

MANIPAL INSTITUTE OF TECHNOLOGY
First Semester B. Tech. In-semester 1 October 2022
Subject: ELE 1071 – Basic Electrical Technology






Thursday, October 20, 2022

Time: 2:30 PM – 3:30 PM




Answer Scheme

Maximum Marks: 15


Part A

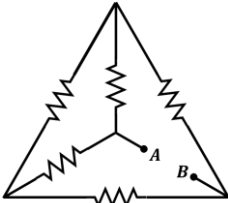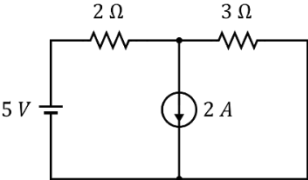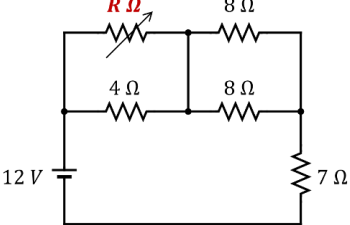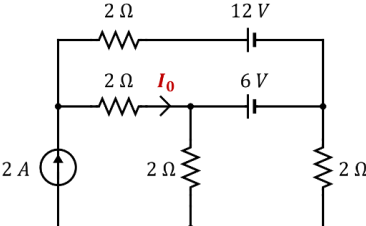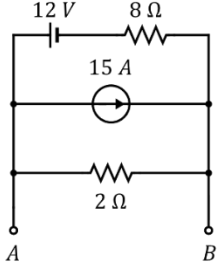Q. No.		Marks	CO	BTL
1	<p>With each resistance being $2\ \Omega$, the equivalent resistance between the terminals A and B is:</p>  <p>a) $2\ \Omega$ b) $4\ \Omega$ c) $8\ \Omega$ d) $1\ \Omega$</p>	1	1	3
2	<p>The 2 A current source is:</p>  <p>a) Delivering 1.2 W b) Absorbing 0.6 W c) Absorbing 1.2 W d) Delivering 0.6 W</p>	1	1	4
3	<p>The value of R so that maximum power dissipation takes place in $7\ \Omega$ resistor is:</p>  <p>a) $12\ \Omega$ b) $0\ \Omega$ c) $7\ \Omega$ d) $2\ \Omega$</p>	1	1	4
4	<p>The current I_0 in the in the circuit when only 6 V source acting alone is:</p>  <p>a) -1.5 A b) 1.5 A c) 3 A d) 1 A</p>	1	1	4
5	<p>A single voltage source in series with a resistance representation between open terminals A & B will be:</p>  <p>a) -21.6 V & $1.6\ \Omega$ c) -26.4 V and $1.6\ \Omega$ b) -30 V & $1.6\ \Omega$ d) 21.6 V & $0\ \Omega$</p>	1	1	3

Part B

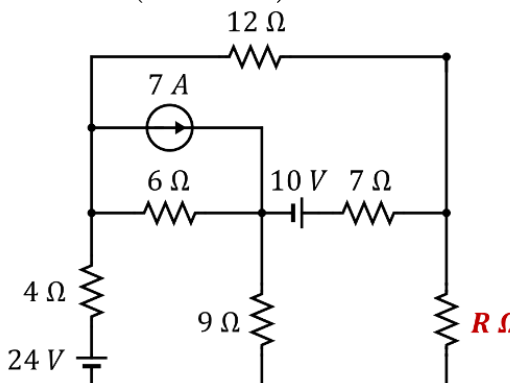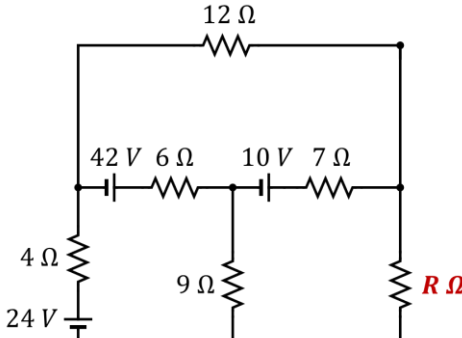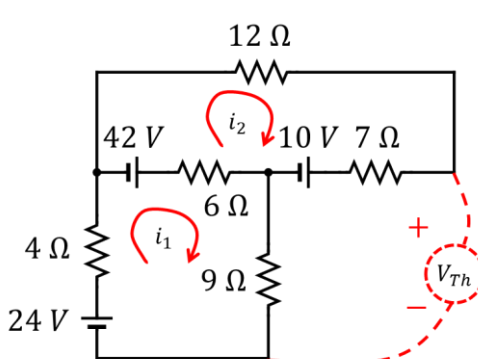Q. No.		Marks	CO	BTL
6	<p>Obtain the value of R so that maximum power is dissipated in it. Also, determine the maximum power. What will be the power transfer efficiency if R is made 1.25 times the source (Thevenin's) resistance.</p> 	4	1	4
Sol	<p>The circuit can be simplified as,</p>  <p style="text-align: right;">----- [0.5M]</p> <p>To find V_{Th}:</p>  <p>Finding i_1 and i_2 using inspection method,</p> $\begin{bmatrix} 19 & -6 \\ -6 & 25 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} 66 \\ -52 \end{bmatrix}$ $i_1 = \frac{1338}{439} = 3.0478 \text{ A} \quad \& \quad i_2 = \frac{-592}{439} = -1.3485 \text{ A}$ <p style="text-align: right;">----- [1M]</p> <p>To find V_{Th}, apply KVL:</p> $(9) \left(\frac{1338}{439} \right) + 10 - (7) \left(\frac{592}{439} \right) - V_{Th} = 0$ $\Rightarrow V_{Th} = 27.9908 \text{ V}$ <p style="text-align: right;">----- [0.5M]</p>			

To find R_{Th} : q

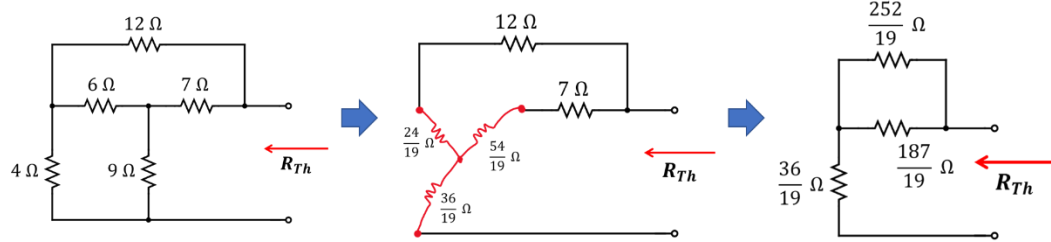

$$\Rightarrow R_{Th} = 7.5444 \Omega$$

----- [1M]

Maximum power dissipated in R will be,

$$P_{\max} = \frac{V_{Th}^2}{4R_{Th}} = 25.9623 \text{ W}$$

----- [0.5M]

If R is made $1.25 R_{Th} = 9.4305 \Omega$, the power dissipated in R will be,

$$P_{R=1.25R_{Th}} = \left(\frac{V_{Th}}{R_{Th} + 1.25R_{Th}} \right)^2 (1.25R_{Th}) = 25.6419 \text{ W}$$

$$P_{\text{Source}, R_{Th}} = \left(\frac{V_{Th}}{R_{Th} + 1.25R_{Th}} \right)^2 (R_{Th}) = 20.51 \text{ W}$$

$$\text{Power transfer efficiency} = \frac{25.6419}{25.6419 + 20.51} \times 100 = 55.559 \%$$


----- [0.5M]

7 Using superposition principle, determine the current I_x as shown.


3

1

3

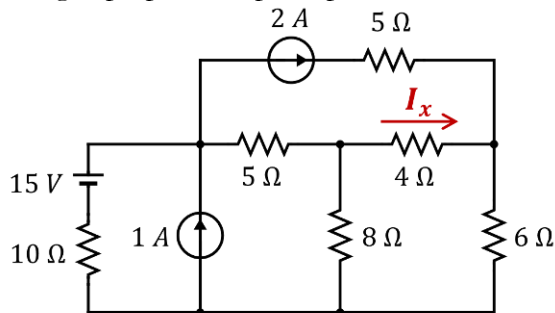

Sol Current I_x due to 15 V source only:

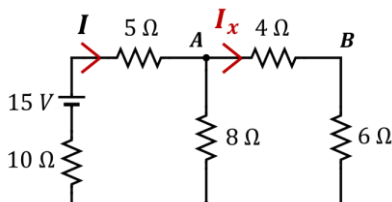


$$R_{eq} = (10 \parallel 8) + 5 + 10 = \frac{175}{9} \Omega$$

$$I = \frac{15}{\left(\frac{175}{9}\right)} = \frac{27}{35} \quad \text{Or} \quad I_x|_{15\text{V}} = \frac{\left(\frac{27}{35}\right)(8)}{8 + 10} = 0.3429 \text{ A (A to B)}$$

----- [1M]


Current I_x due to 1 A source only:

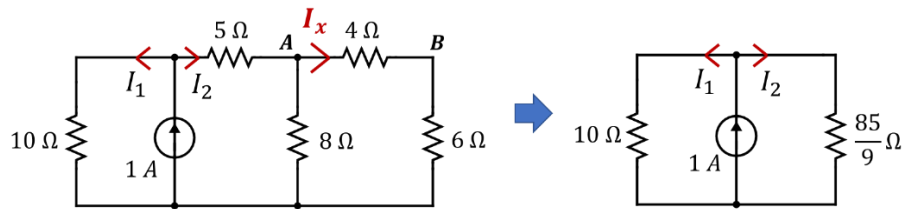

$$I_2 = \frac{1 \times 10}{10 + \frac{85}{9}} = \frac{18}{35} \text{ A} \quad \text{Or} \quad I_x|_{1A} = \frac{(I_2)(8)}{8 + 10} = 0.2286 \text{ A (A to B)}$$

----- [1M]

Current I_x due to 2 A source only:

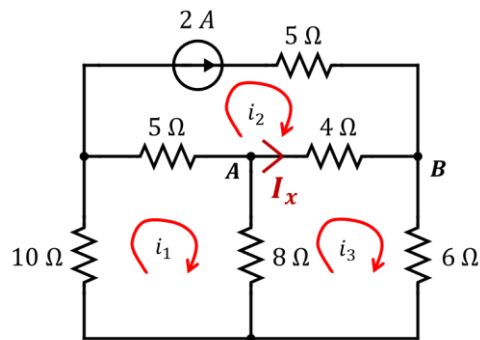

Using mesh analysis to find the mesh currents,

$$i_2 = 2 \quad \dots \text{eq. 1}$$

$$-10i_1 - 5(i_1 - i_2) - 8(i_1 - i_3) = 0$$

$$-23i_1 + 5i_2 + 8i_3 = 0 \quad \dots \text{eq. 2}$$

$$-8(i_3 - i_1) - 4(i_3 - i_2) - 6i_3 = 0$$

$$8i_1 + 4i_2 - 18i_3 = 0 \quad \dots \text{eq. 3}$$

Solving the equations,

$$i_3 = \frac{132}{175} = 0.7542 \text{ A} \quad \text{Or} \quad I_x|_{2A} = i_3 - i_2 = -\frac{218}{175} = -1.2457 \text{ A (A to B)}$$

----- [1M]

As per superposition theorem,

$$I_x = I_x|_{15V} + I_x|_{1A} + I_x|_{2A}$$

$$I_x = \frac{12}{35} + \frac{8}{35} - \frac{218}{175} = -0.6742 \text{ A}$$


8

Find the current through $2\ \Omega$ resistor and power supplied by $3\ \text{A}$ source in the circuit.


3

1


4

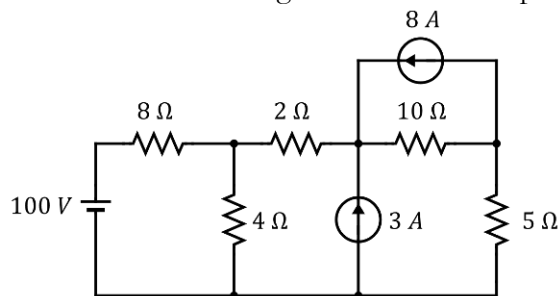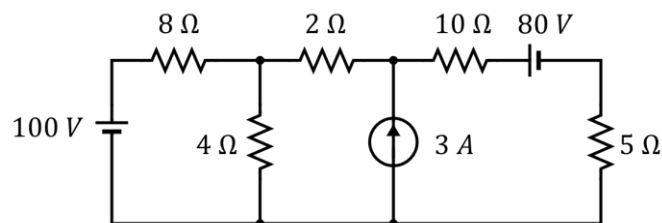**Sol**

Using source transformation, the circuit can be simplified as,



Applying mesh analysis,

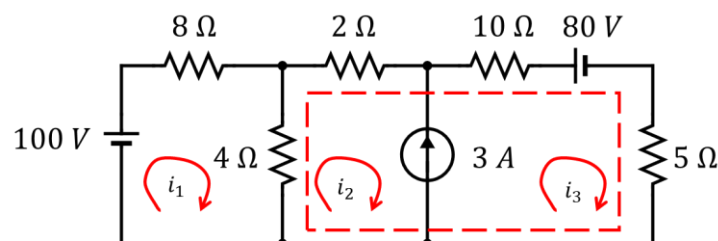

----- [0.5M]

From mesh 1,

$$100 - 8i_1 - 4(i_1 - i_2) = 0 \quad \Rightarrow -12i_1 + 4i_2 = -100 \quad \dots (\text{eq. 1})$$

----- [0.5M]

From Supermesh,

$$-i_2 + i_3 = 3 \quad \dots (\text{eq. 2})$$

----- [0.5M]

$$-4(i_2 - i_1) - 2i_2 - 10i_3 - 80 - 5i_3 = 0 \quad \text{Or} \quad 4i_1 - 6i_2 - 15i_3 = 80 \quad \dots (\text{eq. 3})$$


----- [0.5M]

Solving the three equations,

$$i_1 = \frac{400}{59} = 6.7796\ \text{A} \quad \& \quad i_2 = \frac{-275}{59} = -4.6610\ \text{A} \quad \& \quad i_3 = -\frac{98}{59} = -1.6610\ \text{A}$$

Current through $2\ \Omega$ resistor will be equal to $i_2 \Rightarrow I_{2\Omega} = -4.6610\ \text{A}$

----- [0.5M]

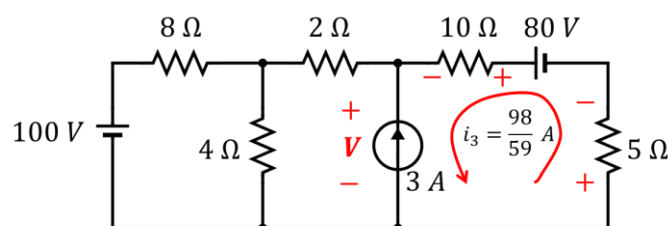To find power supplied by $3\ \text{A}$ source in the circuit, assume a voltage of 'V' across the $3\ \text{A}$ source:

To find the value of 'V', apply KVL in mesh 3:

$$V + (10 + 5)i_3 - 80 = 0 \quad \text{Or} \quad V = 80 - (15)\left(\frac{98}{59}\right) = 55.0847\ \text{V}$$

----- [0.5M]

Power supplied by $3\ \text{A}$ source will be,


$$P_{3A} = 55.0847 \times 3 = 165.2542\ \text{W}$$

Note:

Students may solve the problem using nodal analysis.

The scheme for it will be:

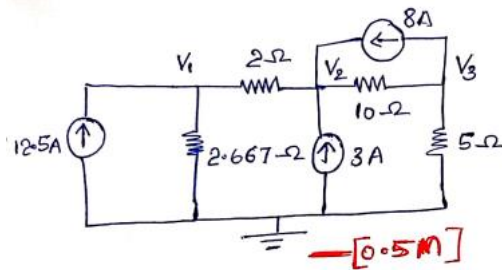- **0.5M** for **100 V** in series with **8 Ω** conversion to **12.5 A** in parallel with **8 Ω**.
- **1.5M** for **writing nodal equations** taking the bottom node as the datum node.
- **0.5M** for calculation of **current through 2 Ω** based on voltages obtained above
- **0.5M** for calculating **power from 3 A** source using **V * I**



Node ①

$$-12.5 + \frac{V_1 - V_2}{2} + \frac{V_1}{2.6667} = 0$$

Node ②

$$-3 - 8 + \frac{V_2 - V_1}{2} + \frac{V_2 - V_3}{10} = 0$$

Node ③

$$8 + \frac{V_3 - V_2}{10} + \frac{V_3}{5} = 0$$

Solving,

$$V_1 = 45.763 \text{ V}$$

$$V_2 = 55.0851 \text{ V}$$

$$V_3 = -8.3049 \text{ V}$$

$$I_{2\Omega} = \frac{V_2 - V_1}{2} = \boxed{4.66105 \text{ A}} \quad \text{from node ② to node ①}$$

$$P_{3A} = V_2 \times 3 = \boxed{165.255 \text{ W}}$$

— [0.5M]

— [0.5M]