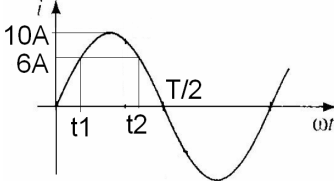
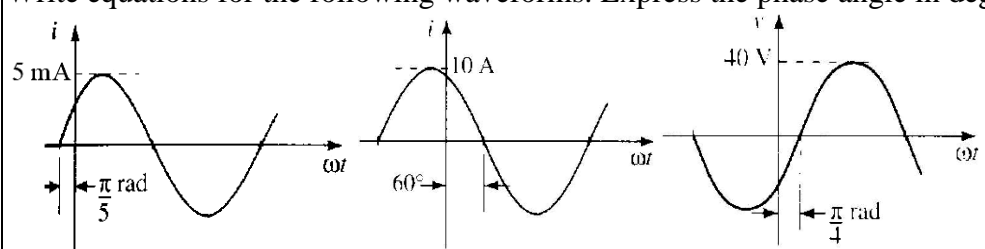
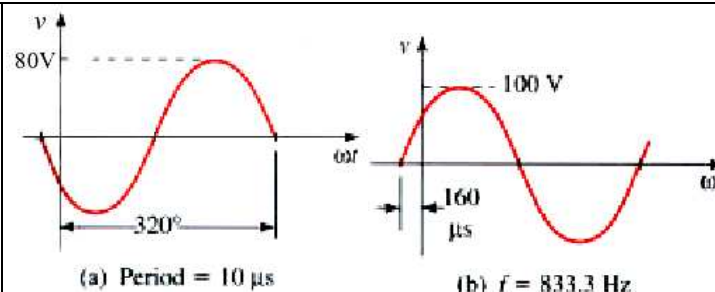
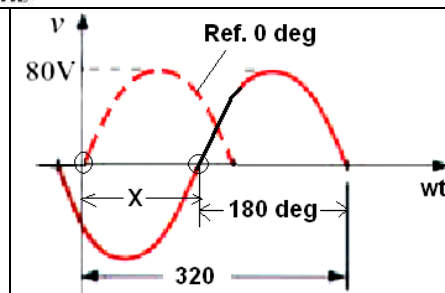
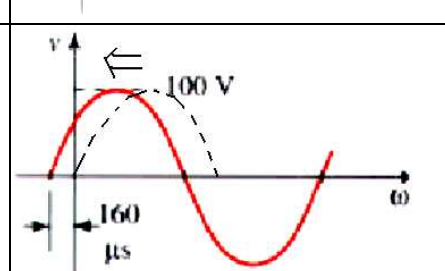
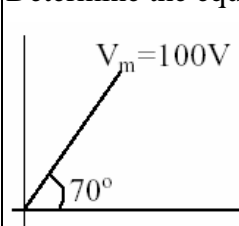
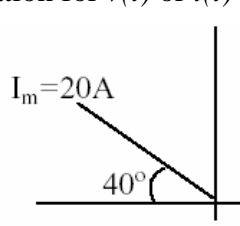
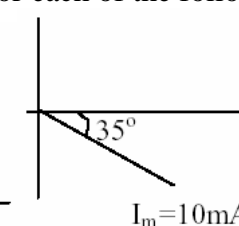
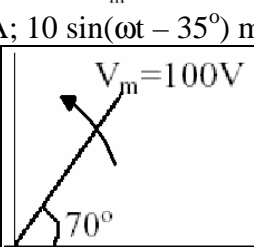
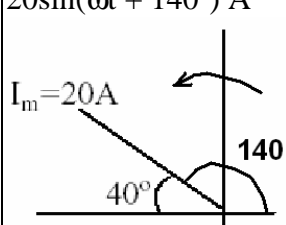
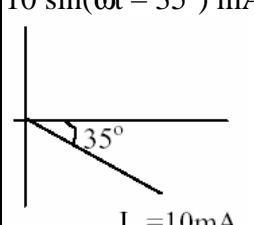
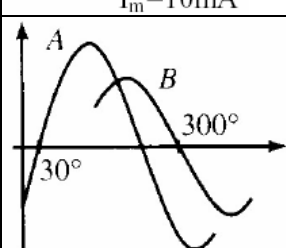
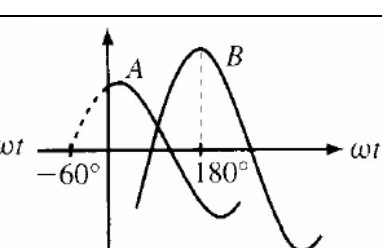
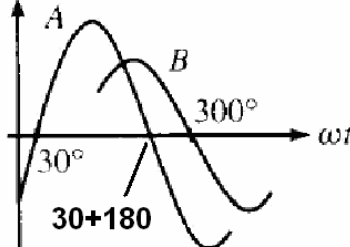
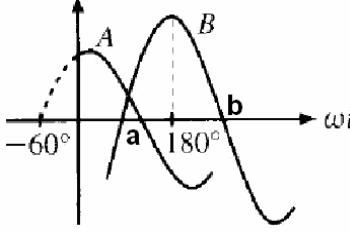
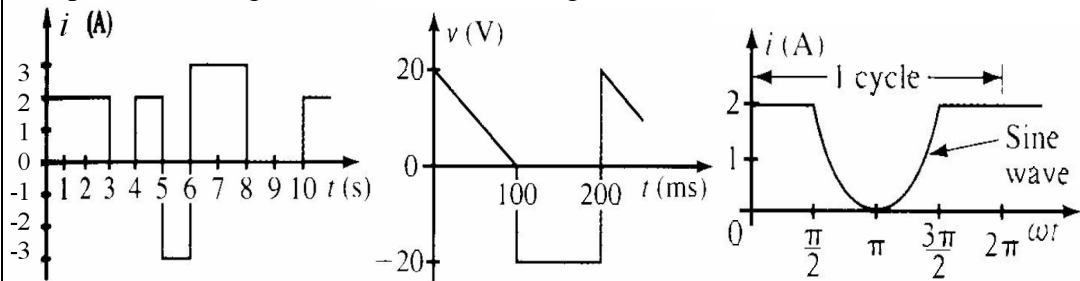
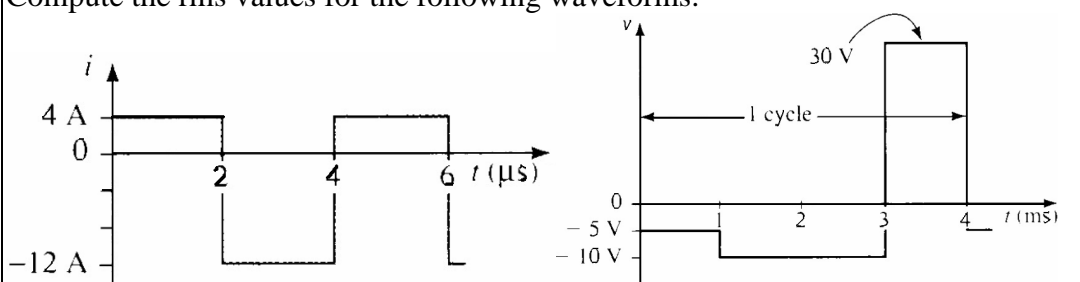


TUTORIAL 1 – AC FUNDAMENTALS


1.	An alternating current i is represented by: $i = 10\sin 942t$ ampere. Determine: (a) the frequency; (b) the period; (c) the time taken from $t=0$ for the current to reach 6 A for a first and second time; [150 Hz; 6.67 ms; 0.68 ms; 2.66 ms]	
1 soln	(a) $942 = \omega = 2\pi f \Rightarrow f = 942 / 2\pi = 150 \text{ Hz}$ (b) $T = 1/f = 1/150 = 6.67 \text{ ms}$ (c) $6 = 10 \sin 942 t_1 \Rightarrow [\sin^{-1} 0.6]/942 = t_1$ $t_1 = 0.68 \text{ ms}$ $t_2 = T/2 - t_1 = 6.67/2 - 0.68 = 2.66 \text{ ms}$	
2.	2. Determine equations for sine waves with the following: (a) $V_m = 170 \text{ V}$, $f = 60 \text{ Hz}$ (b) $I_m = 40 \mu\text{A}$, $T = 10 \text{ ms}$ (c) $T = 120 \mu\text{s}$, $v = 10 \text{ V}$ at $t = 12 \mu\text{s}$ [$v = 170\sin 377t \text{ V}$; $i = 40\sin 628t \mu\text{A}$; $v = 17\sin(52.4 \times 10^3 t) \text{ V}$]	
2 soln	(a) In general $v(t) = V_m \sin \omega t$, $\omega = 2\pi f = 2\pi \times 60 = 377$ $v(t) = 170 \sin 377 t \text{ [V]}$ (b) $i(t) = I_m \sin \omega t$, $\omega = 2\pi f = 2\pi/T = 2\pi / 10 \times 10^{-3} = 628$ $i(t) = 40 \sin 628 t \text{ [\mu A]}$ (c) $\omega = 2\pi f = 2\pi/T = 2\pi / 120 \times 10^{-6} = 52.4 \times 10^3$ $v(t) = V_m \sin \omega t \Rightarrow 10 = V_m \sin 52.4 \times 10^3 \times 12 \times 10^{-6}$ $\Rightarrow 10 = V_m \sin 0.6288 \Rightarrow V_m = 10 / 0.588 = 17$ $\Rightarrow v(t) = 17 \sin 52.4 \times 10^3 t \text{ [V]}$	
3	Determine f , T and amplitude for each of the following: (a) $v = 75\sin 200\pi t$ (b) $i = 8\sin 300t$ [100 Hz, 0.01 s, 75 V; 47.7 Hz, 20.9 ms, 8 A]	
3 soln	(a) Amplitude = 75, $2\pi f = 200\pi \Rightarrow f = 100 \text{ Hz} \Rightarrow T = 1/f = 0.01 \text{ s}$ (b) Amplitude = 8A, $2\pi f = 300 \Rightarrow f = 47.7 \text{ Hz} \Rightarrow T = 1/f = 20.9 \text{ ms}$	
4.	Given $v = 5\sin(\omega t + 45^\circ)$. If $\omega = 20\pi \text{ rad/s}$, what is v at $t = 20, 75$ and 90 ms ? [4.46 V; -3.54 V; 0.782 V]	
4 soln	$45 = \pi/4$ $v(t) = 5\sin(20\pi t + \pi/4)$ At $t=20 \text{ ms}$ $v(20 \text{ ms}) = 5\sin(20\pi \times 20 \times 10^{-3} + \pi/4) = 4.46 \text{ [V]}$ At $t=75 \text{ ms}$ $v(75 \text{ ms}) = 5\sin(20\pi \times 75 \times 10^{-3} + \pi/4) = -3.54 \text{ [V]}$ At $t=90 \text{ ms}$ $v(90 \text{ ms}) = 5\sin(20\pi \times 90 \times 10^{-3} + \pi/4) = 0.782 \text{ [V]}$	
5.	Write equations for the following waveforms. Express the phase angle in degrees.	
		
	(a) $\omega = 1000 \text{ rad/s}$ (b) $T = 50 \text{ ms}$ (c) $f = 900 \text{ Hz}$ [$5\sin(1000t + 36^\circ) \text{ mA}$; $10\sin(40\pi t + 120^\circ) \text{ A}$; $4\sin(1800\pi t - 45^\circ) \text{ V}$]	
5 soln	(a) $i(t) = I_m \sin(\omega t + \phi) \Rightarrow$ The waveform is shift to the left by $\pi/5$ Maximum = 5mA $\Rightarrow I_m = 5$, $\pi/5 \text{ [rad]} = \pi/5 / \pi \times 180 = 36 \text{ [deg]}$ $i(t) = 5 \sin(1000t + 36^\circ)$ (b) $i(t) = I_m \sin(\omega t + \phi) \Rightarrow$ The waveform is shift to the left by $180-60$ $\Rightarrow \phi = 120 \text{ [deg]}$, $\omega = 2\pi f = 2\pi/T = 2\pi / 50 \times 10^{-3} = 40\pi$ Maximum = 10A $\Rightarrow I_m \Rightarrow i(t) = 10 \sin(40\pi t + 120^\circ)$ (c) $v(t) = V_m \sin(\omega t + \phi) \Rightarrow$ The waveform is shift to the right by $\pi/4$ $\Rightarrow \pi/4 = \pi/4 / \pi \times 180 = 45 \text{ [deg]}$, $\omega = 2\pi f = 2\pi \times 900 = 1800\pi$ Maximum = 40V $\Rightarrow V_m = 40 \Rightarrow v(t) = 40 \sin(1800\pi t - 45^\circ)$	
6.	Write equations for the following waveforms. Express the phase angle in degrees. [$80\sin(2 \times 10^5 \pi t - 140^\circ) \text{ V}$; $100\sin(5236t + 48^\circ) \text{ V}$]	


	 <p>(a) Period = $10\ \mu\text{s}$</p> <p>(b) $f = 833.3\ \text{Hz}$</p>	
6(a) soln	<p>(a) Since the curve shift to right hand side by $x=320 - 180 = 140$ Phase lag $140\ \text{deg}$, $T = 10 \times 10^{-6}$, $\omega = 2\pi f = 2\pi/T = 2\pi/10 \times 10^{-6}$ $\omega = 2\pi \times 10^{-5}$ $\Rightarrow v(t) = 80 \sin(2\pi \times 10^{-5}t - 140^\circ)$</p>	 <p>Ref. 0 deg</p>
6(b) soln	<p>(b) The curve is shift to the left by $160\ \mu\text{s}$ $f = 833.3\ \text{Hz}$, $\omega = 2\pi f = 5236$, $T = 1/f = 1200\ \mu\text{s}$ Phase lead = $160\ \mu\text{s} / 1200\ \mu\text{s} \times 360 = 48\ \text{deg}$ $\Rightarrow v(t) = 100 \sin(5236t + 48^\circ)$</p>	
7.	<p>Determine the equation for $v(t)$ or $i(t)$ for each of the following phasor.</p> <div style="display: flex; justify-content: space-around; align-items: flex-end;"> <div style="text-align: center;">  <p>$V_m = 100\text{V}$</p> </div> <div style="text-align: center;">  <p>$I_m = 20\text{A}$</p> </div> <div style="text-align: center;">  <p>$I_m = 10\text{mA}$</p> </div> </div> <p>$[100\sin(\omega t + 70^\circ)\ \text{V}; 20\sin(\omega t + 140^\circ)\ \text{mA}; 10 \sin(\omega t - 35^\circ)\ \text{mA}]$</p>	
7 soln	<p>Rotating vector rotates in anti-clockwise direction, all phase angle measure with respect to the horizontal x-axis At time $t=0$, initial phase angle = 70 Magnitude is 100V, $\Rightarrow v(t) = 100 \sin(\omega t + 70^\circ)$</p>	 <p>$V_m = 100\text{V}$</p>
7 soln	<p>At time $t = 0$, initial phase angle = $180 - 40 = 140$ Magnitude = 20A $20\sin(\omega t + 140^\circ)\ \text{A}$</p>	<p>At time $t = 0$, initial phase angle = -35 Magnitude = 10mA $10 \sin(\omega t - 35^\circ)\ \text{mA}$</p>
	 <p>$I_m = 20\text{A}$</p>	 <p>$I_m = 10\text{mA}$</p>
8.	<p>For the following waveforms, determine the phase differences. Which waveform leads?</p> <div style="display: flex; justify-content: space-around;"> <div style="text-align: center;">  <p>(a)</p> </div> <div style="text-align: center;">  <p>(b)</p> </div> </div>	

8 soln	<p>(a) B is lagging with respect to A $300 - (30 + 180) = 90$</p> 	<p>(b) B is lagging with respect to A Point a $= 180 - 60 = 120$ Point b $= 180 + 90 = 270$ $270 - 120 = 150$</p> 
9.	<p>Compute the average values of the following waveforms. [1.1 A; -5 V; 1.36 A]</p> 	
9	<p>(a) Total Area Under the Curve = A $A = (2 \times 3) + (1 \times 2) - (1 \times 3) + (2 \times 3) = 11$ Average Voltage = A / 10 = 11/10 = 1.1</p> <p>(b) Period = T = 200 Total Area under the curve from 0 to 200 $A = (100 \times 20 / 2) - (100 \times 20) = -1000$ Average Voltage = -1000/200 = -5V</p>	<p>(c) Period = T = 2π A = Area under the curve = 2 × 2π - A₁ A₁ = Area under a sine wave for half cycle Average Value of a half cycle sine wave is 0.637 x Max Value $A_1 = 2 \times 0.637 \times \pi = 1.274\pi$ $A = 4\pi - 1.274\pi = 2.726\pi$ Average = 2.726π / (2π) = 1.363</p>
10.	<p>Determine the rms values of each for the following.</p> <p>(a) A 12V battery (b) $-24\sin(\omega t + 73^\circ)$ mA (c) $10 + 24\sin\omega t$ V (d) $45 - 27\cos 2\omega t$ V [12 V; 17 mA; 19.7 V; 48.9 V]</p>	
10	<p>(a) DC voltage 12V, RMS = 12 (b) AC Amplitude = -24 ⇒ RMS = 24/√2 = 16.9mA (c) DC component = 10, AC Amplitude = 24 Average Square = 10² + 24²/2 = 388 ⇒ RMS = √388 = 19.7V (d) DC component = 45, AC Amplitude = 27 Average Square = 45² + 27²/2 = 2389.5 ⇒ RMS = √2389.5 = 48.9V</p>	
11.	<p>Compute the rms values for the following waveforms.</p> 	
11 Soln	<p>(a) A = Total Area Under the (Current)² Curve $A = (4)^2 \times 2 + (-12)^2 \times 2 = 320$ Mean Square = 320/4 = 80 Root Mean Square = √80 = 8.94</p> <p>(b) A = Total Area Under the V² Curve $A = (-5)^2 \times 1 + (-10)^2 \times 2 + (30)^2 \times 1 = 1125$ Mean Square = 1125/4 = 281.25 Root Mean Square = √281.25 = 16.8</p>	

TUTORIAL 2 – AC SINGLE PHASE




1.	Determine the resistance and the series connected inductance or capacitance for each of the following impedances (a) $12 + j5$, (b) $-j40$ and (c) $30 \angle 60^\circ$. Assume a frequency of 50 Hz.
1. Soln	<p>(a) $Z = R + jX_L$ Hence, $12 + j5$ shows that the resistance is 12 ohms and the inductive reactance is 5 ohms. $X_L = 2\pi fL$, $L = \frac{X_L}{2\pi f} = \frac{5}{2\pi(50)} = 0.016 \text{ H}$ i.e. the inductance is 16 mH.</p> <p>$X_L = \omega L = 2\pi f L$</p> <p>(b) $Z = R - jX_C$ Hence, $0 - j40$ shows that the resistance is zero and the capacitive reactance is 40 ohms. $X_C = \frac{1}{2\pi fC}$, $C = \frac{1}{2\pi fX_C} = \frac{10^6}{2\pi(50)(40)} \mu F = 79.6 \mu F$ i.e. the capacitance is 79.6 μF.</p> <p>$X_C = 1/[\omega C] = 1/[2\pi f C]$</p> <p>(c) $30 \angle 60^\circ = 30 (\cos 60^\circ + j \sin 60^\circ) = 15 + j25.98$. From equation (4), $15 + j25.98$ shows that the resistance is 15 ohms and the inductive reactance is 25.98 ohms. $X_L = 2\pi fL$, $L = \frac{X_L}{2\pi f} = \frac{25.98}{2\pi(50)} = 0.0827 \text{ H}$ i.e. the inductance is 82.7 mH</p> <p>$Z = R + Xj$ if $X > 0 \Rightarrow$ Inductive $\Rightarrow X = 2\pi f L$ if $X < 0 \Rightarrow$ Capacitive $\Rightarrow X_C = 1/[2\pi f C]$</p>
2.	The impedance of an electrical circuit is $30 - j50$ ohms. Determine (a) the resistance, (b) the capacitance, (c) the modulus of the impedance and (d) the current flowing, when the circuit is connected to a 240 V, 50 Hz supply.
2. Soln	<p>Modulus (Magnitude) = Z $Z = Z \angle \tan^{-1}(X/R)$</p> <p>(a) Since $Z = R - jX_C$, the resistance is 30 ohms.</p> <p>(b) Since $Z = R - jX_C$, the capacitive reactance is 50 ohms. $X_C = \frac{1}{2\pi fC}$, $C = \frac{1}{2\pi fX_C} = \frac{10^6}{2\pi(50)(50)} \mu F = 63.7 \mu F$ i.e. the capacitance is 63.7 μF.</p> <p>(c) The modulus of the impedance $Z = \sqrt{R^2 + X_C^2} = \sqrt{30^2 + (-50)^2} = \underline{\underline{58.31 \text{ ohms}}}$</p> <p>(d) The circuit phase angle $\phi = \arctan\left(\frac{X_C}{R}\right) = \arctan\left(\frac{50}{30}\right) = 59^\circ 2'$ Since $Z = R - jX_C$, this angle is in the fourth quadrant, i.e. $-59^\circ 2'$. Thus an alternative way of expressing the impedance is $Z = 58.31 \angle -59^\circ 2'$ The current flowing, $I = \frac{V}{Z} = \frac{240 \angle 0^\circ}{58.31 \angle -59^\circ 2'} = \underline{\underline{4.116 \angle 59^\circ 2'}}$ <i>(Since the voltage is 240 volts, it is $240 + j0$ volts in rectangular form, and $240 \angle 0^\circ$ in polar form.)</i></p>

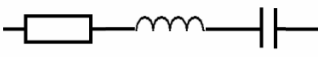3.	A series connected electrical circuit has a resistance of 32 ohms and an inductance of 0.15H. It is connected to a 200V, 50Hz supply. Determine (a) the inductive reactance, (b) the impedance in rectangular and polar forms, (c) the current and the circuit phase angle, (d) the voltage drop across the resistor and (e) the voltage drop across the inductor.
3. Soln	<p>(a) Inductive resistance $X_L = 2\pi fL = 2\pi(50)(0.15) = \underline{47.1 \text{ ohms}}$</p> <p>(b) Impedance $Z = R + jX_L$ i.e. $Z = 32 + j47.1$ Thus, $Z = \sqrt{32^2 + 47.1^2} = 57 \text{ ohms}$ and the circuit phase angle $\phi = \arctan\left(\frac{47.1}{32}\right) = 55^\circ 48'$ Thus $Z = 57 \angle 55^\circ 48'$ ohms, in polar form.</p> <p>(c) Current $I = \frac{V}{Z} = \frac{200 \angle 0^\circ}{57 \angle 55^\circ 48'} = \underline{3.51 \angle -55^\circ 48'}$ i.e. the current is 3.51 A, lagging V by $55^\circ 48'$</p> <p>(d) The voltage drop across the 32 ohm resistor, $V_R = IR = (3.51 \angle -55^\circ 48')(32) = \underline{112.3 \angle -55^\circ 48' \text{ volts}}$</p> <p>(e) The voltage drop across the 0.15 H inductor, $V_L = IX_L = (3.51 \angle -55^\circ 48')(47.1 \angle 90^\circ) = \underline{165.3 \angle 34^\circ 12' \text{ volts}}$</p>
4.	A 240 V, 50 Hz voltage is applied across a series connected circuit having a resistance of 12 ohm, an inductance of 0.10 H and a capacitance of 120 μ F. Determine the current flowing in the circuit.
4. Soln	 <p>$R + jX_L - jX_C$ $R + j(2\pi fL) - j/(2\pi fC)$</p> <p>Inductive resistance $X_L = 2\pi fL = 2\pi(50)(0.10) = 31.4 \Omega$</p> <p>Capacitive reactance $X_C = \frac{1}{2\pi fC} = \frac{10^6}{2\pi(50)(120)} = 26.5 \Omega$</p> <p>Impedance $Z = R + j(X_L - X_C) = 12 + j(31.4 - 26.5) = 12 + j4.9$</p> <p>In polar form, $Z = \sqrt{12^2 + 4.9^2} \arctan\left(\frac{4.9}{12}\right) = 13 \angle 22^\circ 13' \text{ ohms}$</p> <p>Hence, current $I = \frac{V}{Z} = \frac{240 \angle 0^\circ}{13 \angle 22^\circ 13'} = 18.5 \angle -22^\circ 13' \text{ amperes}$ i.e. the current flowing is 18.5 amperes, lagging the voltage by $22^\circ 13'$.</p>
5.	Determine the resistance R and series inductance L (or capacitance C) for each of the following impedances, assuming the frequency to be 50 Hz. (a) $4 + j7$ (b) $3 - j2$ (c) $j10$ (d) $-j200$ (e) $15 \angle \pi/3$ (f) $6 \angle -45^\circ$ [(a) $R = 4 \Omega$, $L = 22.3 \text{ mH}$ (b) $R = 3 \Omega$, $C = 1592 \mu\text{F}$ (c) $R = 0$, $L = 31.8 \text{ mH}$ (d) $R = 0$, $C = 15.92 \mu\text{F}$ (e) $R = 7.5 \Omega$, $L = 41.3 \text{ mH}$ (f) 4.243Ω , $C = 750.3 \mu\text{F}$]
5 Soln	<p>(a) $4 + j7 = R + jX \Rightarrow R = 4$, $X > 0 \Rightarrow$ Inductive, $X = L\omega = L 2\pi f = L 100\pi$ $\Rightarrow L = 7 / (100\pi) = 0.0223 = 22.3 \text{ mH}$</p> <p>(b) $3 - j2 = R + jX \Rightarrow R = 3$, $X < 0 \Rightarrow$ Capacitive, $X = 1/(C\omega) = 1/(C 2\pi f) = 1/(C 100\pi)$ $\Rightarrow C = 1 / (2 \times 100\pi) = 0.00159 \text{ F} = 1592 \mu\text{F}$</p> <p>(c) $10j = R + jX \Rightarrow R = 0$, $X > 0 \Rightarrow$ Inductive, $X = L\omega = L 2\pi f = L 100\pi$ $\Rightarrow L = 10 / (100\pi) = 31.8 \text{ mH}$</p> <p>(d) $-j200$, $X < 0 \Rightarrow$ Capacitive, $X = 1/(C\omega) = 1/(C 2\pi f) = 1/(C 100\pi)$</p>



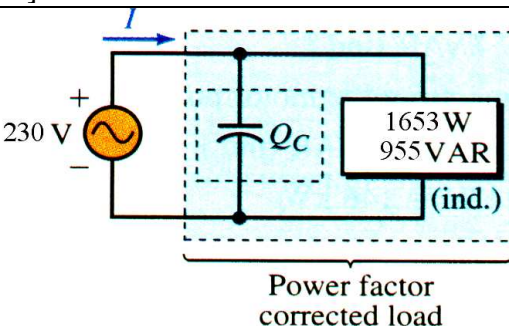
	$\Rightarrow C = 1 / (200 \times 100\pi) = 15.92 \mu\text{F}$ (e) $15 \angle \pi/3 = 15 \cos(\pi/3) + j 15 \sin(\pi/3) = 7.5 + j13 \Rightarrow R = 7.5$ $X = L\omega = L 2\pi f = L 100\pi \Rightarrow L = 13 / (100\pi) = 41.3 \text{mH}$ (f) $6 \angle -45^\circ = 6 \cos(-45) + j 6 \sin(-45) = 4.24 - j4.24j$ $R = 4.24 \Omega, X = 1/(C\omega) = 1/(C 2\pi f) = 1/(C 100\pi) \Rightarrow C = 1 / (4.24 \times 100\pi) = 750.3 \mu\text{F}$	
6.	An alternating voltage of 100 V, 50 Hz is applied across an impedance of $(20 - j30)\Omega$. Calculate: (a) the resistance, (b) the capacitance, (c) the current, and (d) the phase angle between current and voltage. [(a) 20 . (b) 106.1 μF (c) 2.774 A (d) $56^\circ 19'$]	
7.	Two voltages are represented by $(15 + j10)$ and $(12 - j4)$ volts. Determine the magnitude of the resultant voltage when these voltages are added. [27.66 V]	
8.	Two impedances, $Z_1 = (2 + j6)\Omega$ and $Z_2 = (5 - j2)\Omega$, are connected in series to a supply voltage of 100V. Find the magnitude of the current and its phase angle relative to the voltage. [12.40A; $29^\circ 45'$ lag]	
9.	A resistance of 45 ohms is connected in series with a capacitor of 42 μF . If the applied voltage is 250V, 50Hz determine: (a) the capacitive reactance; (b) the impedance; (c) the current, and its phase relative to the applied voltage; (d) the voltage across the resistance; and (e) the voltage across the capacitance. [(a) 75.79 . (b) 88.14 . (c) 2.836 A at $59^\circ 18'$ leading (d) 127.6 V (e) 214.9 V]	
10	A single –phase motor takes 8.3A at a power factor of 0.866 lagging when connected to a 230V, 50Hz supply. Two similar capacitors are connected in parallel with each other to form a capacitance bank. This capacitance bank is now connected in parallel with the motor to raise the power factor to unity. Determines the capacitance of each capacitor. [28.7 μF]	
10. Soln	$\text{VA} = 230 \times 8.3 = 1909 \text{ VA}$ $\text{Real Power} = 1909 \times 0.866 = 1653.2 \text{ W}$ $\text{Phase angle} = \cos^{-1} 0.866 = 30$ $\text{Reactive Power} = 1909 \times \sin 30 = 954.6 \text{ VAR}$ $\text{For Unity Power Factor}$ $Q_c = 954.6 = V^2 / X_c \Rightarrow 230^2 / 954.6 = X_c$ $X_c = 55.42 \Omega = 1 / (2\pi f C) = 1 / (2\pi 50 C)$ $\text{Capacitance of Cap. Bank} = 57.44 \mu\text{F}$ $\text{Capacitance of Each Capacitor} = 57.44 / 2 = 28.7 \mu\text{F}$	
11	(a) A single-phase load of 5kW operates at a power factor of 0.6 lagging. It is proposed to improve this power factor to 0.95 lagging by connecting a capacitor across the load. Calculate the kVA rating of the capacitor. [5.02kVA] (b) Give reasons why it is to a consumer's economic advantage to improve his power factor with respect to the supply, and explain the fact that the improvement is rarely made to unity in practice.	
12	A 25kVA single-phase has a power factor of 0.8 lag. A 10kVA capacitor is connected for power-factor correction. Calculate the input apparent power in kVA taken from the mains and its power factor when the motor is (a) on half load; (b) on full load. Sketch a phasor diagram for each case. [10.3 kVA, 0.97 leading; 20.6kVA, 0.97 lagging]	
13	A single-phase motor takes 50A at a power factor of 0.6 lagging from a 250V, 50Hz supply. What value of capacitance must be a shunting capacitor have to raise the overall power factor to 0.9 lagging ? How does the installation of the capacitor affect the line and motor currents? [324 μF]	
14	A 240V, single-phase supply feeds the following loads (a) incandescent lamps taking a current of 8A at unity power factor, (b) fluorescent lamps taking a current of 5A at 0.8 leading power factor (c) motor taking a current of 7A at 0.75 lagging power factor. Sketch the phasor diagram and determine the total current, active power and reactive power taken from the supply and the overall power factor. [17.35A, 4140W, 390 var, 0.996 lagging]	
15	The load taken from an ac supply consists of (a) a heating load of 15kW (b) a motor load of 40kVA at 0.6 power factor lagging (c) a load of 20kW at 0.8 power factor lagging. Calculate the total load from the supply (in kW and kVA) and its power factor. What would be the kvar rating of a capacitor to bring the power factor to unity and how would the capacitor be connected. [59kW, 75.5kVA, 0.78 lagging; 47kvar in parallel]	
16	A cable is required to supply a welding set taking a current of 225A at 110V alternating current, the average power factor being 0.5 lagging. An available cable has a rating of 175A and it is decided to use this cable by installing a capacitor across the terminal of the welding set. Find (a) the required capacitor	

current and reactive power to limit the cable current to 175A (b) the overall power factor with the capacitor in circuit. [60.8A, 6.7 kvar, 0.643 lag]

TUTORIAL 3 – AC THREE PHASE
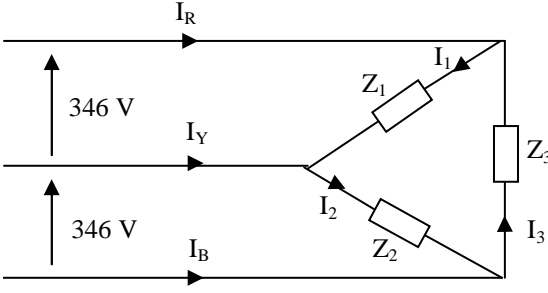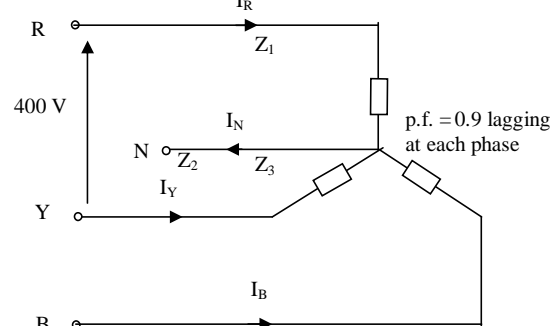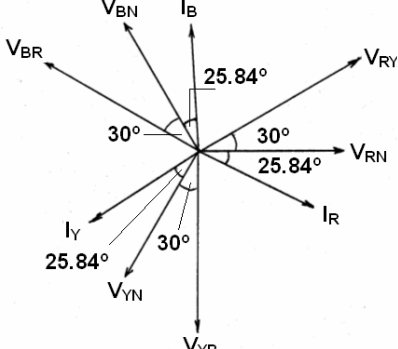
<p>1. A delta load is connected as shown in fig. 1. Calculate I_P and I_L of the circuit. $Z_1 = 100 \angle 0^\circ \Omega$ $Z_2 = 20 + j60 \Omega$ $Z_3 = -j106 \Omega$ I_P : Phase Current I_1, I_2, I_3 I_L : Line Current I_R, I_Y, I_B</p>	 <p style="text-align: right;">Fig. 1</p>
<p>1. Soln Take V_{RY} as reference. Phase currents: $I_1 = \frac{V_{RY}}{Z_1} = 346 \angle 0^\circ / 100 \angle 0^\circ = 3.46 \angle 0^\circ \text{ A}$ $I_2 = \frac{V_{YB}}{Z_2} = 346 \angle -120^\circ / (20 + j60) = 5.47 \angle -(120 + 71.57)^\circ = 5.47 \angle 168.43^\circ \text{ A} \text{ (-191.57}^\circ = 168.43^\circ)$ $I_3 = \frac{V_{BR}}{Z_3} = 346 \angle -240^\circ / -j106 = 346 \angle 120^\circ / 106 \angle 270^\circ = 3.26 \angle -150^\circ \text{ A}$ Line currents: $I_R = I_1 - I_3 = 3.46 \angle 0^\circ - 3.26 \angle -150^\circ = 6.5 \angle 14.54^\circ \text{ A}$ $I_Y = I_2 - I_1 = 5.47 \angle 168.43^\circ - 3.46 \angle 0^\circ = 8.89 \angle 173^\circ \text{ A}$ $I_B = I_3 - I_2 = 3.26 \angle -150^\circ - 5.47 \angle 168.43^\circ = 3.72 \angle -47.08^\circ \text{ A}$</p>	
<p>2. A factory has the following load with power factor of 0.9 lagging in each phase. Red phase 40 A, yellow phase 50 A and blue phase 60 A. If the supply is 400V, three-phase, four-wire, calculate the current in the neutral and the total power. Draw a phasor diagram for phase and line quantities.</p>	
<p>2 Soln $I_R = 40 \text{ A}$ $I_Y = 50 \text{ A}$ $I_B = 60 \text{ A}$ Find I_N and $P_{3\phi}$, $(400/\sqrt{3}) = 230.9$ Take V_{RN} as reference, $V_{RN} = 230.9 \angle 0^\circ \text{ V}$, $V_{YN} = 230.9 \angle -120^\circ \text{ V}$, $V_{BN} = 230.9 \angle 120^\circ \text{ V}$ Power angle at each phase, $\phi = \cos^{-1} 0.9 = 25.84^\circ$</p>	
<p>Therefore, $I_R = 40 \angle -25.84^\circ \text{ A}$, $I_Y = 50 \angle -145.84^\circ \text{ A}$, $I_B = 60 \angle 94.16^\circ \text{ A}$ $I_N = 40 \angle -25.84^\circ + 50 \angle -145.84^\circ + 60 \angle 94.16^\circ$ $= 17.31 \angle 124.16^\circ \text{ A} \quad \#$ $P_{3\phi} = P_R + P_Y + P_B = V_R I_R \cos \phi_R + V_Y I_Y \cos \phi_Y + V_B I_B \cos \phi_B$ $= V_P (I_R + I_Y + I_B) \cos \phi_P = (400/\sqrt{3}) \times (40 + 50 + 60) \times (0.9)$ $= 31.18 \text{ kW}$</p>	

TUTORIAL 4 – AC THREE PHASE

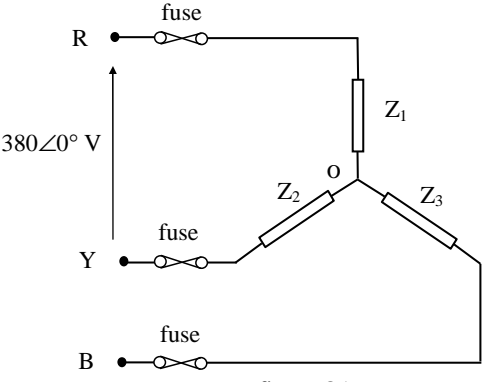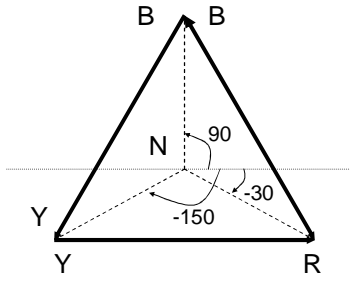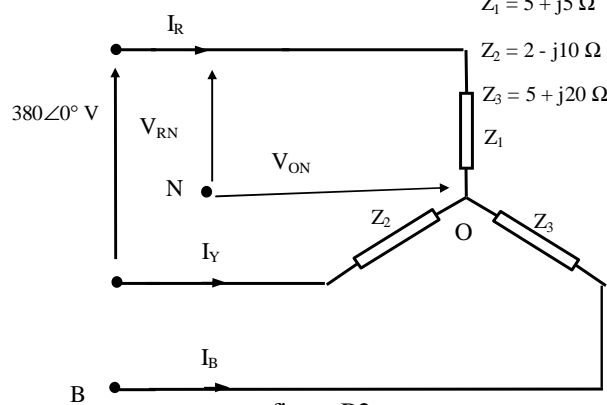1	<p>A 380V 3-phase power supply with phase sequence RYB is supplying power to an unbalance 3-phase star load as shown in fig Q1.</p> <p>Given $Z_1=5+j5$ $Z_2=2-j10$ $Z_3=5+j20$.</p> <p>Take V_{RY} as reference. Determine:</p> <p>(a) the magnitude and phase angle of the voltage at the star point;</p> <p>(b) the magnitudes and phase angles of the three line currents;</p> <p>(c) the total active and reactive powers of the load;</p> <p>(d) the overall power factor of the load; and,</p> <p>(e) draw the phasor diagram of the three-phase load.</p>	 <p>figure Q1</p>
1 Soln	<p>Take V_{RY} as reference.</p> <p>$V_{RY} = 380\angle 0^\circ \text{ V}$</p> <p>$V_{YB} = 380\angle -120^\circ \text{ V}$</p> <p>$V_{BR} = 380\angle 120^\circ \text{ V}$</p> <p>$V_{RN} = 219.4\angle -30^\circ \text{ V}$</p> <p>$V_{YN} = 219.4\angle -150^\circ \text{ V}$</p> <p>$V_{BN} = 219.4\angle 90^\circ \text{ V}$</p> <p>By Millman's Therom</p> $V_{on} = \frac{V_{RN} Y_1 + V_{YN} Y_2 + V_{BN} Y_3}{Y_1 + Y_2 + Y_3} \text{ where:}$ 	 <p>figure B2</p>
	$Y_1 = \frac{1}{Z_1} = \frac{1}{5+j5} = 0.1414\angle -45^\circ \text{ s}$ $Y_2 = \frac{1}{Z_2} = \frac{1}{2-j10} = 0.0981\angle 78.7^\circ \text{ s}$ $Y_3 = \frac{1}{Z_3} = \frac{1}{5+j20} = 0.0485\angle -76.0^\circ \text{ s}$ $V_{on} = \frac{(219.4\angle -30^\circ)(0.1414\angle -45^\circ) + (219.4\angle -150^\circ)(0.0981\angle 78.7^\circ) + (219.4\angle 90^\circ)(0.0485\angle -76.0^\circ)}{0.1414\angle -45^\circ + 0.0981\angle 78.7^\circ + 0.0485\angle -76.0^\circ}$	
	$\therefore I_R = (V_{RN} - V_{on}).Y_1 = (219.4\angle -30^\circ - 384.46\angle -40.9^\circ)(0.1414\angle -45^\circ) \text{ A} = 24.61\angle 80.3^\circ \text{ A}$ $I_Y = (V_{YN} - V_{on}).Y_2 = (219.4\angle -150^\circ - 384.46\angle -40.9^\circ)(0.0981\angle 78.7^\circ) \text{ A} = 49.14\angle -117.8^\circ \text{ A}$ $I_B = (V_{BN} - V_{on}).Y_3 = (219.4\angle 90^\circ - 384.46\angle -40.9^\circ)(0.0485\angle -76.0^\circ) \text{ A} = 26.85\angle 45.7^\circ \text{ A}$	
	<p>Total active power, $P_T = I_R ^2.R_{Z_1} + I_Y ^2.R_{Z_2} + I_B ^2.R_{Z_3}$</p> $= (24.61)^2.(5) + (49.14)^2.(2) + (26.85)^2.(5) \text{ W} = 11.46 \text{ kW} \#$ <p>Total reactive power, $Q_T = I_R ^2.X_{Z_1} + I_Y ^2.X_{Z_2} + I_B ^2.X_{Z_3}$</p> $= (24.61)^2.(+5) + (49.14)^2.(-10) + (26.85)^2.(+20) \text{ Var} = -6.7 \text{ kVar (capacitive)} \#$	
	<p>The overall power factor, $p.f. = \frac{P_T}{\sqrt{P_T^2 + Q_T^2}} = \frac{11.46}{\sqrt{(11.46)^2 + (6.7)^2}} = 0.863 \text{ leading}$</p>	
2	<p>Referred to figure Q1, if the fuse in the Yellow line is blown, determine the new values of:</p> <p>(a) the voltage at the star point; and,</p>	

	(b) the three line currents.
2 Soln	<p>If fuse on Yellow is blown, the star point voltage is: (Z_2 becomes OPEN Circuit, $Z_2=\infty$, $Y_2=0$)</p> $V_{on} = \frac{V_{RN}Y_1 + V_{YN}Y_2 + V_{BN}Y_3}{Y_1 + Y_2 + Y_3} = \frac{(219.4\angle -30^\circ)(0.1414\angle -45^\circ) + (219.4\angle -150^\circ)(0) + (219.4\angle 90^\circ)(0.0485\angle -76.0^\circ)}{0.1414\angle -45^\circ + 0 + 0.0485\angle -76.0^\circ}$ $V_{on} = 178.5\angle -3.41^\circ \text{ V}$
	<p>If fuse on Yellow is blown, $I_Y = 0 \text{ A}$, and $I_B = -I_R$</p> $I_R = \frac{V_{RB}}{Z_1 + Z_3} = \frac{(380\angle -60^\circ)}{(5 + j5) + (5 + j20)} \text{ A}$ $I_R = 14.1\angle -128.1^\circ \text{ A} \# ; I_Y = 0 \text{ A} \# ; I_B = -I_R = 14.1\angle 51.9^\circ \text{ A} \#$ $I_B = -14.1\angle -128.1^\circ \text{ A} = 14.1\angle (180^\circ - 128.1^\circ) \text{ A} = 14.1\angle 51.9^\circ \text{ A}$ $-1 = 1\angle 180^\circ$

TUTORIAL 5 – INTRODUCTION TO ELECTRICAL MACHINES, TRANSFORMER

1	(i) State two advantages and two disadvantages of using auto-transformer compared with the two-winding transformer.
1 Soln	<p><u>Advantages of auto-transformer</u></p> <ol style="list-style-type: none"> 1. Less copper is used, when compared with 2 winding transformer. 2. The weight and volume of transformer is less. 3. The auto-transformer has a higher efficiency. 4. The auto-transformer suffers less voltage variation. 5. The auto-transformer provides continuously variable output voltage. <p><u>Disadvantages of auto-transformer</u></p> <ol style="list-style-type: none"> 1. The auto-transformer primary and secondary have a common neutral connection, so it cannot be used as an isolation transformer. 2. The secondary short-circuit current will be larger. 3. A break in the secondary winding stops the transformer action and the full primary voltage will be applied to the secondary circuit.
2	<p>(i) State the losses associated with the iron core of a transformer.</p> <p>(ii) Explain the method(s) used to reduce the losses you stated in part (a)(i)</p>
2 Soln	<p>(1) There are hysteresis and eddy current losses.</p> <p>(2) Hysteresis loss can be reduced by using material with small remanent flux or narrow hysteresis loop, since the area of the hysteresis represent losses per cycle of magnetization.</p> <p>Eddy current can be reduced by using laminated iron core. Induced emf is reduced to $1/N$ of the total if N metal sheets are used. At the same time, the resistance path is increased N times due to the reduction in the thickness.</p>
3	A 200kVA, 6600/400V, 50Hz single-phase transformer has 80 turns on the secondary. Calculate (a) the approximate values of the primary and secondary currents; (b) the approximate number of primary turns; (c) the maximum value of the flux. (30.3A, 1320 turns, 0.0225 Wb)
3 Soln	$V_1/V_2 = N_1/N_2 \Rightarrow 6600/400 = N_1/80$ $\Rightarrow N_1 = 6600 / 400 \times 80 = 1320$ $I_1 = 200 \times 1000 / V_1 = 200 \times 1000 / 6600 = 30.3 \text{ A}$ $I_2 = 200 \times 1000 / V_2 = 200 \times 1000 / 400 = 500 \text{ A}$ $V_1 = 4.44 N_1 f \Phi \Rightarrow \Phi = 6600 / (4.44 \times 50 \times 1320) = 22.5 \text{ mWb}$
4	The primary winding of a single-phase transformer is connected to a 230V, 50Hz supply. The secondary winding has 1500 turns. If the maximum value of core flux is 0.00207Wb, determine : (a) the number of turns on the primary winding; (b) the secondary induced voltage; (c) the net cross-sectional core area if the flux density has a maximum value of 0.465 Tesla. (500, 690V, 4450mm ²)
4. Soln	<p>(a) $V_1 = 4.44 N_1 f \Phi \Rightarrow N_1 = V_1 / (4.44 f \Phi) = 230 / (4.44 \times 50 \times 0.00207) = 500 \text{ turns}$</p> <p>(b) $V_2 = 4.44 N_2 f \Phi = 4.44 \times 1500 \times 50 \times 0.00207 = 689 \text{ V}$</p> <p>(c) $0.00207 = B A = 0.465 \times A \Rightarrow A = 4451 \text{ mm}^2$</p>
5	The primary of a transformer has 500 turns and is supplied at a voltage of 2000V r.m.s. at a frequency of 50Hz. Estimate the maximum value of the flux through the core. (0.018Wb)

5.	2000 r.m.s
Soln	$2000 = 4.44 \times N_1 \times f \times \Phi = 4.44 \times 500 \times 50 \times \Phi$ $\Rightarrow \Phi = 0.018$
6	The primary of a transformer has 1000 turns and produces a maximum flux of 0.03Wb alternating at 50Hz in the iron core. The secondary winding has 35 turns. Estimate the r.m.s. values of primary and secondary e.m.f.'s on the assumption that the flux change is sinusoidal. (6660V, 233V)
6.	$V_1 = 4.44 N_1 f \Phi = 4.44 \times 1000 \times 50 \times 0.03 = 6660$
Soln	$V_2 = 4.44 N_2 f \Phi = 4.44 \times 35 \times 50 \times 0.03 = 233V$
7	A single-phase transformer has a primary voltage of 2000V, a secondary voltage of 440V and a full load output of 20kVA. The secondary winding has 130 turns. Calculate the number of primary turns and the primary and secondary full load currents, neglecting losses. (591, 10A, 45.5A)
7.	$I_1 = 20 \times 1000 / 440 = 45.45A$
Soln	$I_2 = 20 \times 1000 / 2000 = 10A$ $V_1 / V_2 = N_1 / N_2 \Rightarrow N_1 = V_1 / V_2 \times N_2 = 2000 / 440 \times 130 = 591$
8	A 4-pole, 3-phase induction motor is energized from a 60Hz supply, and is running at a load condition for which the slip is 0.03. Determine (a) the speed of the rotation field; (b) the rotor speed; (c) the rotor frequency. [Ans (a) 1800 r.p.m (b) 1746 r.p.m. (c) 1.8 Hz]
8.	(a) Speed of Rotating Field = Frequency / pole-pair = $60 / 2 = 30 \text{ rev/s} = 1800 \text{ rpm}$
Soln	(b) Rotor Speed = $N_r = (1-s) N_s = (1-0.03) \times 1800 = 1746 \text{ rpm}$ (c) Rotor frequency = slip x stator frequency = $s f = 0.03 \times 60 = 1.8\text{Hz}$
9	The frequency of the e.m.f. induced in the rotor of an 3-phase, 6-pole induction motor is found to have 180 cycles/min. The motor is connected to a 50Hz, 440V supply, calculate (a) the speed of the motor; (b) the percentage slip of the motor. [Ans (a) 940 r.p.m(b) 0.06]
9.	(a) $180 \text{ cycles/min} = 3 \text{ cycles / sec} \Rightarrow \text{Rotor frequency} = f_r = 3\text{Hz}$
Soln	$3 = s \times \text{stator frequency} = s 50 \Rightarrow s = 0.06$ (b) $N_s = f / p = 50 / 3 = 16.67 \text{ rev/s} = 1000 \text{ rpm}$ Speed of the rotor = $(1-s) \times N_s = 1000 \times (1-0.06) = 940 \text{ rpm}$