

# Basic Electrical Technology

[ELE 105 I]


---

## ***CHAPTER 3 - SINGLE PHASE AC CIRCUITS***

***(3.5)***

# Power associated in RL load

For RL load:

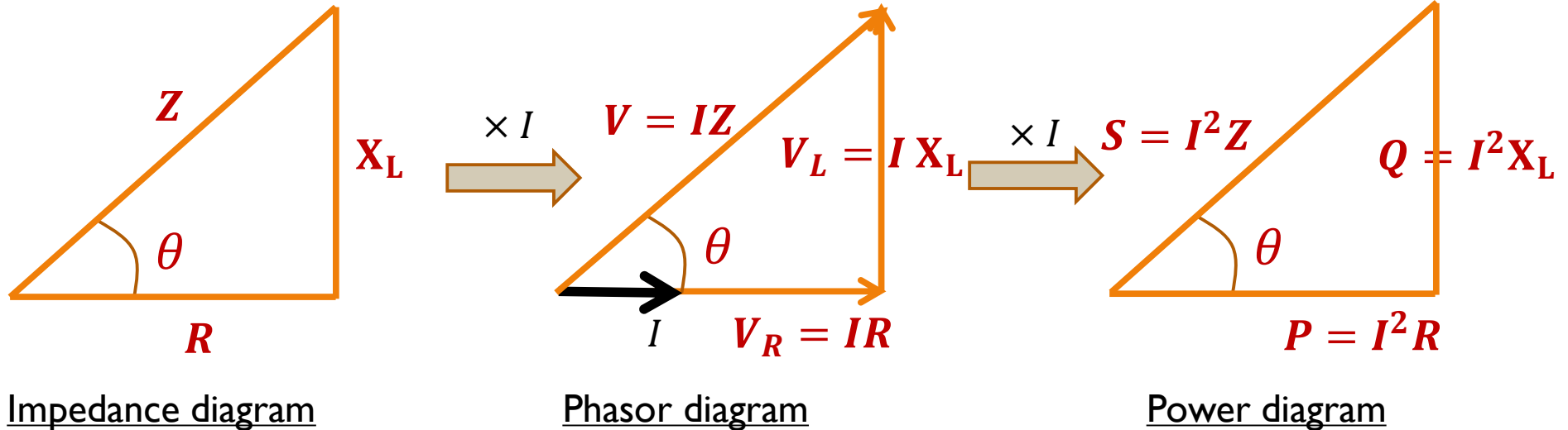

$$S = P + jQ$$

where,

$S$  = Apparent Power (VA)

$P$  = Active Power (W)

$Q$  = Reactive Power (var)


$$S = |V||I|$$

$$P = VI \cos \phi$$

$$Q = VI \sin \phi$$

# Power associated in RC load

For RC load:

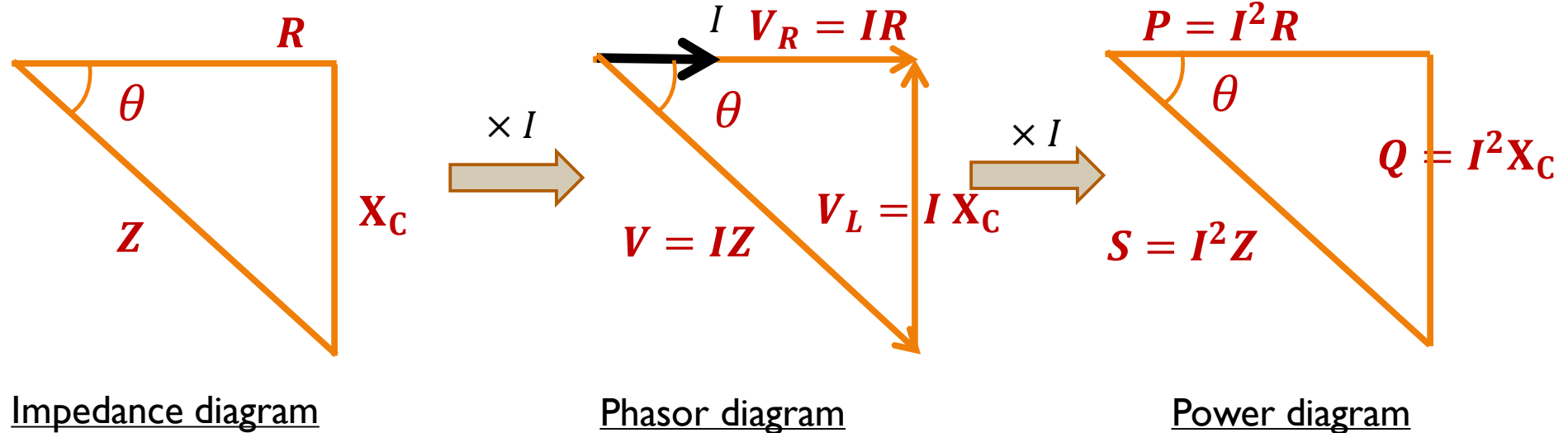

$$S = P - jQ$$

Where,

$S$  = Apparent Power (VA)

$P$  = Active Power (W)

$Q$  = Reactive Power (var)

$$S = |V||I|$$

$$P = VI \cos \phi$$

$$Q = VI \sin \phi$$

# Power in AC circuits

Power in AC circuit can be written as,

$$S = (\bar{V})(\bar{I}^*)$$

**For RL Load**


$$\begin{aligned} Z &= |Z|\angle\phi \\ \text{if } \bar{V} &= |V|\angle 0^\circ \\ \bar{I} &= |I|\angle -\phi \\ I^* &= |I|\angle\phi \end{aligned}$$

$$S = VI(\cos\phi + j\sin\phi)$$

$$S = P + jQ$$

$$P = V_{rms}I_{rms}\cos\phi$$

$$Q = V_{rms}I_{rms}\sin\phi$$

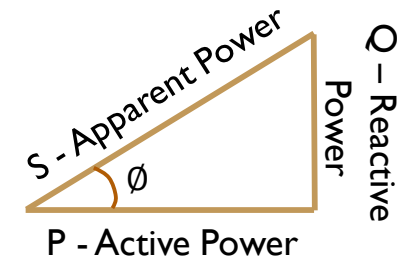

**For RC Load**


$$\begin{aligned} Z &= |Z|\angle -\phi \\ \text{if } \bar{V} &= |V|\angle 0^\circ \\ \bar{I} &= |I|\angle\phi \\ I^* &= |I|\angle -\phi \end{aligned}$$

$$S = VI(\cos\phi - j\sin\phi)$$

$$S = P - jQ$$

$$P = V_{rms}I_{rms}\cos\phi$$

$$Q = V_{rms}I_{rms}\sin\phi$$

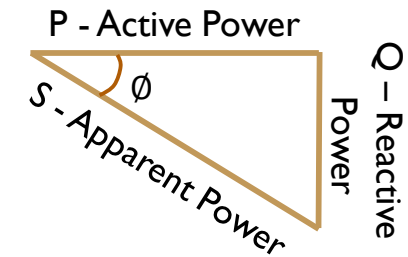

Units:

Apparent Power(S)

**VA**

Active Power(P)

**W**

Reactive Power(Q)

**var**

# Power Factor

$$\text{Power Factor} = \frac{\text{Active Power } P \text{ in watts}}{\text{Apparent Power } S \text{ in voltamperes}}$$

$$\cos \theta = \frac{P}{S} = \frac{P}{VI}$$

- For an impedance  $Z$ ,

$$\cos \theta = \frac{IR}{V} = \frac{IR}{IZ} = \frac{\text{resistance}}{\text{impedance}}$$

- Power factor is *lagging* when the *current lags the supply voltage*
- Power factor is *leading* when the *current leads the supply voltage*
- For a resistive load, power factor is Unity

# Disadvantages of Low Power Factor

- Under utilisation of power system network
- Increased transmission losses
- Hence bulk consumers are advised to maintain the power factor close to unity by power utilities



## Remedial Measures

- Reactive power demand of Inductive loads can be compensated with capacitive loads
- It is possible to localise reactive power requirement by connecting parallel capacitors across the load


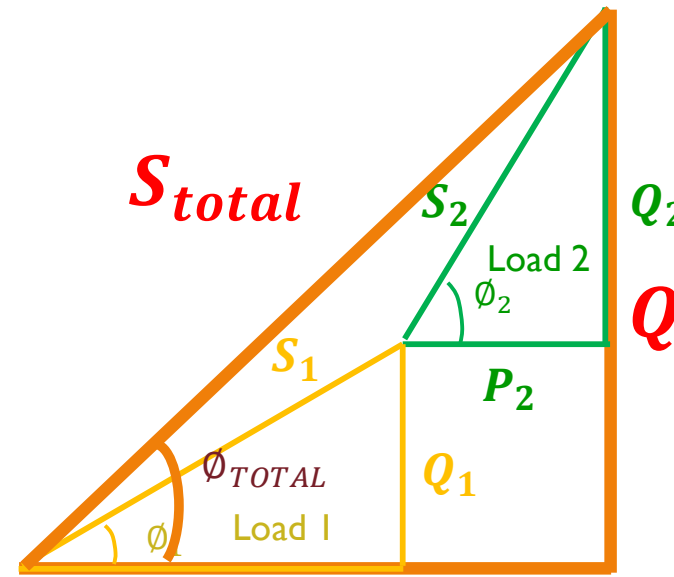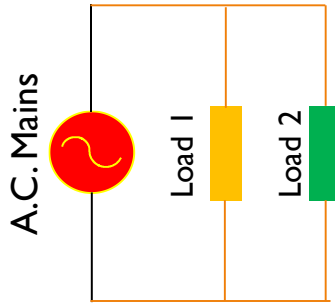
# Power Triangle

- Practically, loads are in connected parallel
- Majority of the loads are inductive in nature



$$Q_{total} = Q_1 + Q_2$$


$$S_{total} = P_{total} + jQ_{total}$$

$$P_{total} = P_1 + P_2$$

<http://www.kptcl.com/save.htm>
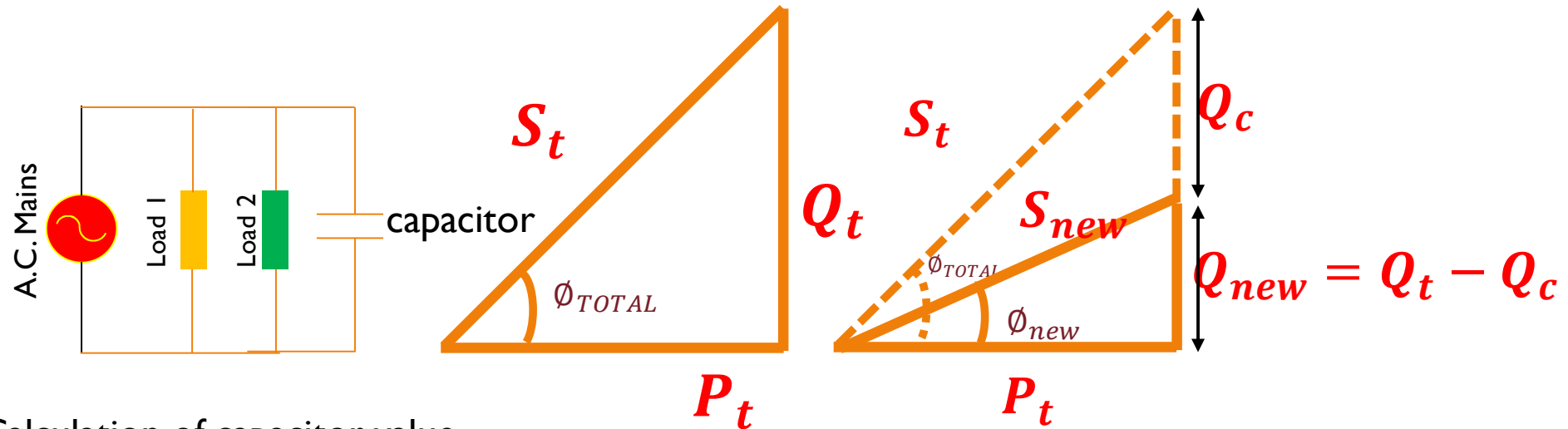
# Power Factor Improvement

- Connect capacitor parallel to the load
- Energy stored by the capacitor provides the required reactive power by the load



## Calculation of capacitor value

- Calculate  $Q_c$  needed to improve power factor to  $\cos\phi_{new}$
- Calculate  $X_c = \frac{V^2}{Q_c}$  &  $C = \frac{1}{2\pi f X_c}$



# Illustration I

---

A single-phase motor takes **8.3 A** at a power factor of **0.866 lagging** when connected to a **230 V, 50 Hz supply**. Capacitance bank is now connected in parallel with the motor to raise the power factor to **unity**. Determine the capacitance value

$$C = 57.43\mu F$$

# Illustration 2

---

A single-phase load of **5 kW** operates at a power factor of **0.6 lagging**. It is proposed to improve this power factor to **0.95 lagging** by connecting a capacitor across the load. Calculate the kvar rating of the capacitor

$$Q_c = 5.023 \text{ kVAR}$$

# Illustration 3

---

Obtain the complete power triangle for three parallel-connected loads:

- (a) 250VA, 0.5 p.f lagging
- (b) 180W, 0.8 p.f leading
- (c) 300VA, 100 var (inductive)

Ans

$$P_{TOTAL} = 587.8W$$

$$Q_{TOTAL} = 181.5var \text{ (inductive)}$$

$$S_{TOTAL} = 615.2VA$$

0.955 lagging



**Thank You!**