



MANIPAL INSTITUTE OF TECHNOLOGY

MANIPAL

(A constituent institution of MAHE, Manipal)



Basic Electrical Technology

[ELE 105 I]

4. Three Phase AC Circuits


L2 I – Generation & Representation of three phase supply

Topics Covered



- ➡ *Generation of Three Phase Supply*
- ➡ *Representation of Three Phase Excitation*
- ➡ *Relationship between Phase and Line Voltages*
- ➡ *3 Phase Supply & Loads*


Generation of Three Phase

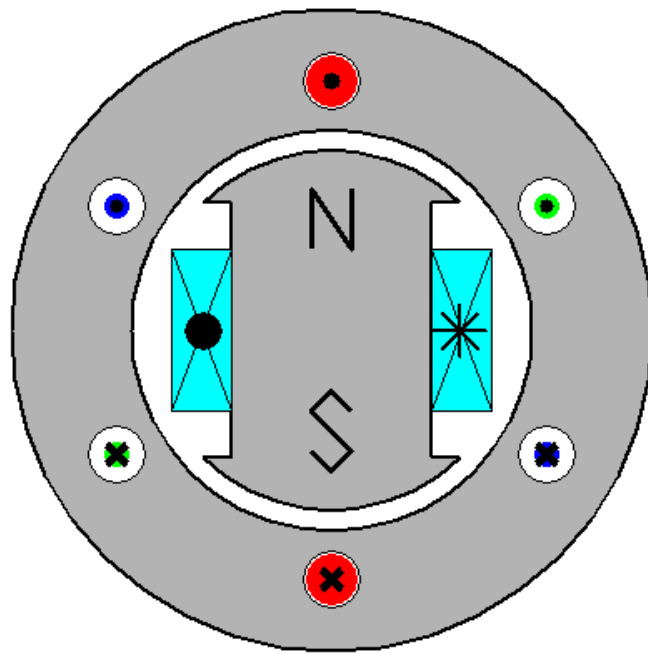

Phase A

Phase B

Phase C

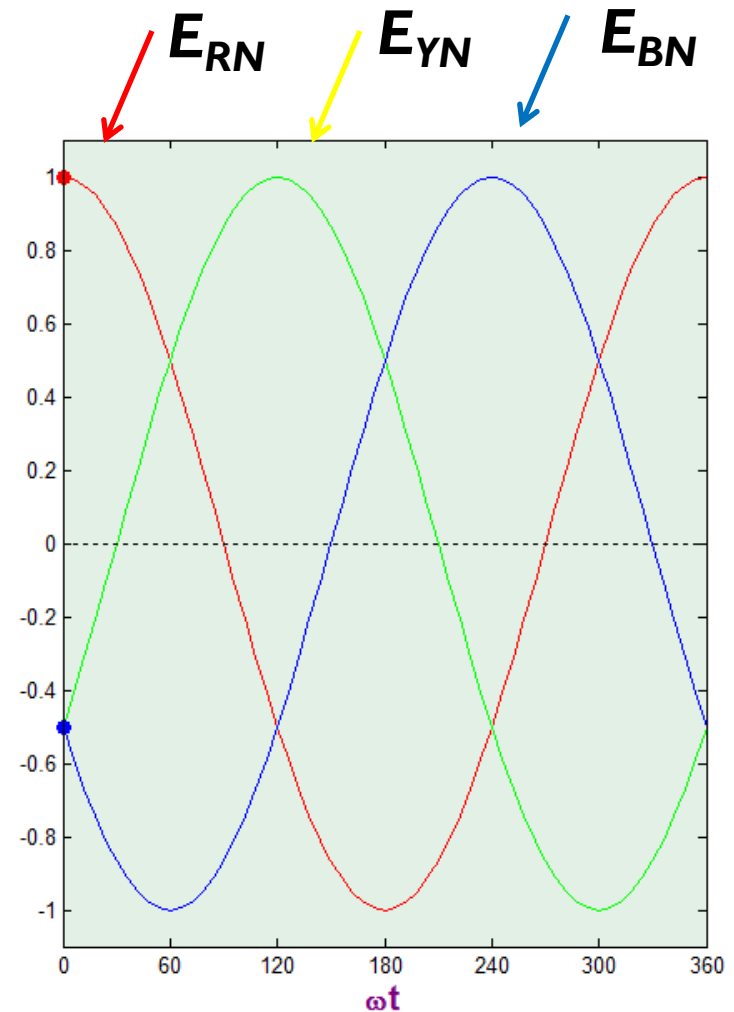

Courtesy : www.ece.umn.edu

3 Phase Excitation (Phase Voltages)





Phase Voltages,

$$\hat{V}_{RN} = V_m \sin(\omega t)$$

$$\hat{V}_{YN} = V_m \sin(\omega t - 120^\circ)$$
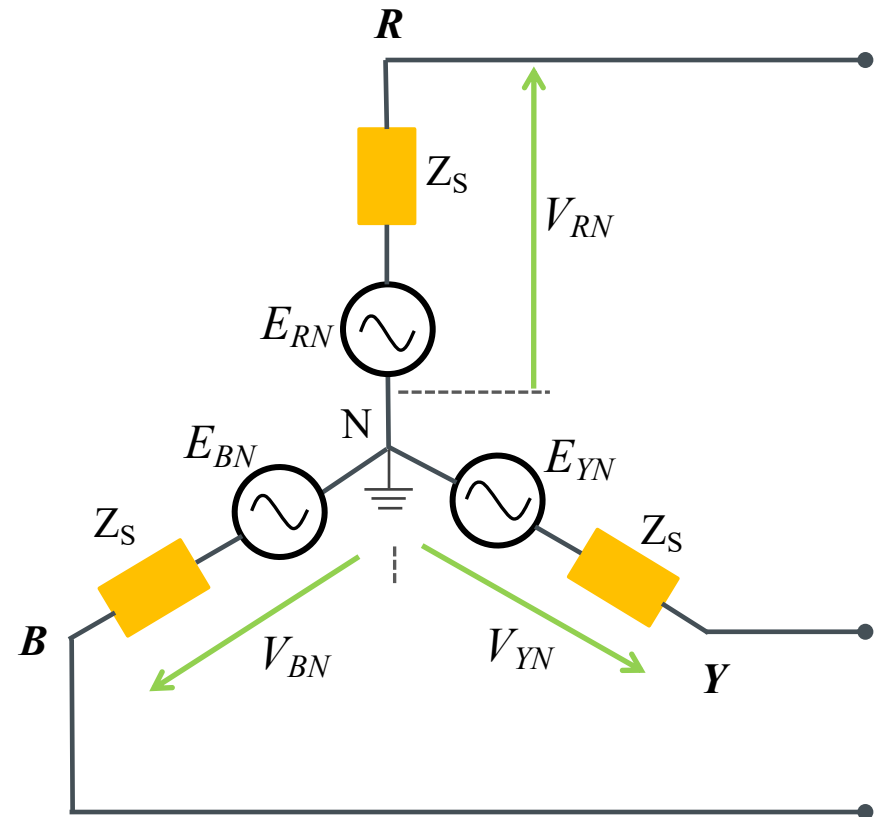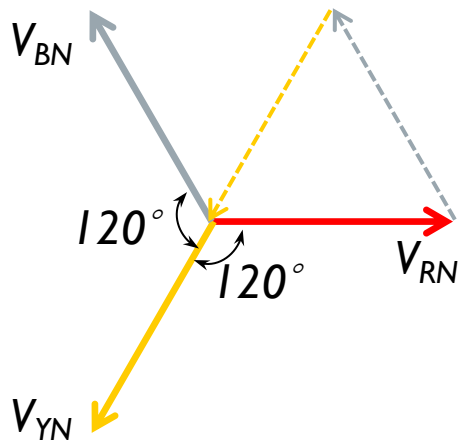
$$\hat{V}_{BN} = V_m \sin(\omega t - 240^\circ)$$






Three Phase Source


Summing up the phase voltages,

$$\hat{V}_{RN} + \hat{V}_{YN} + \hat{V}_{BN} = 0$$

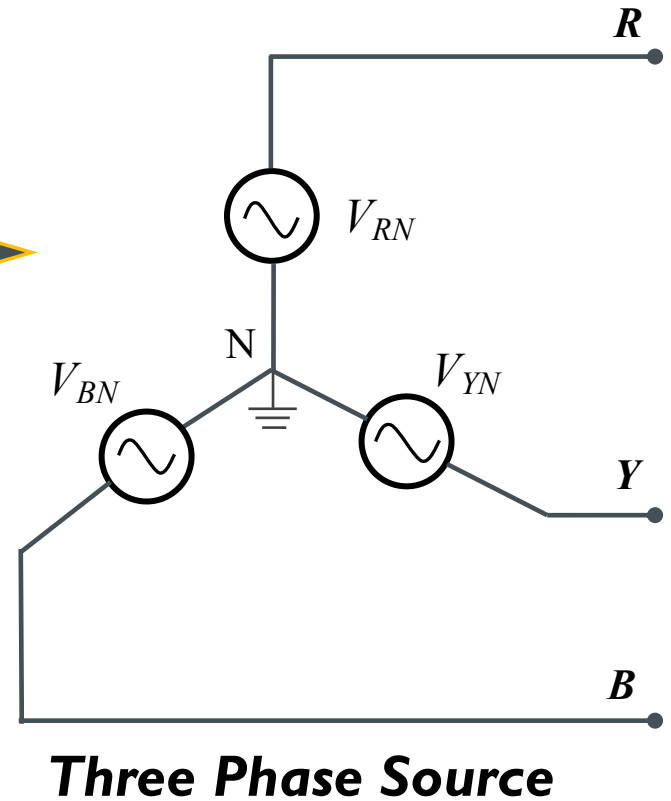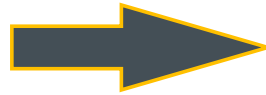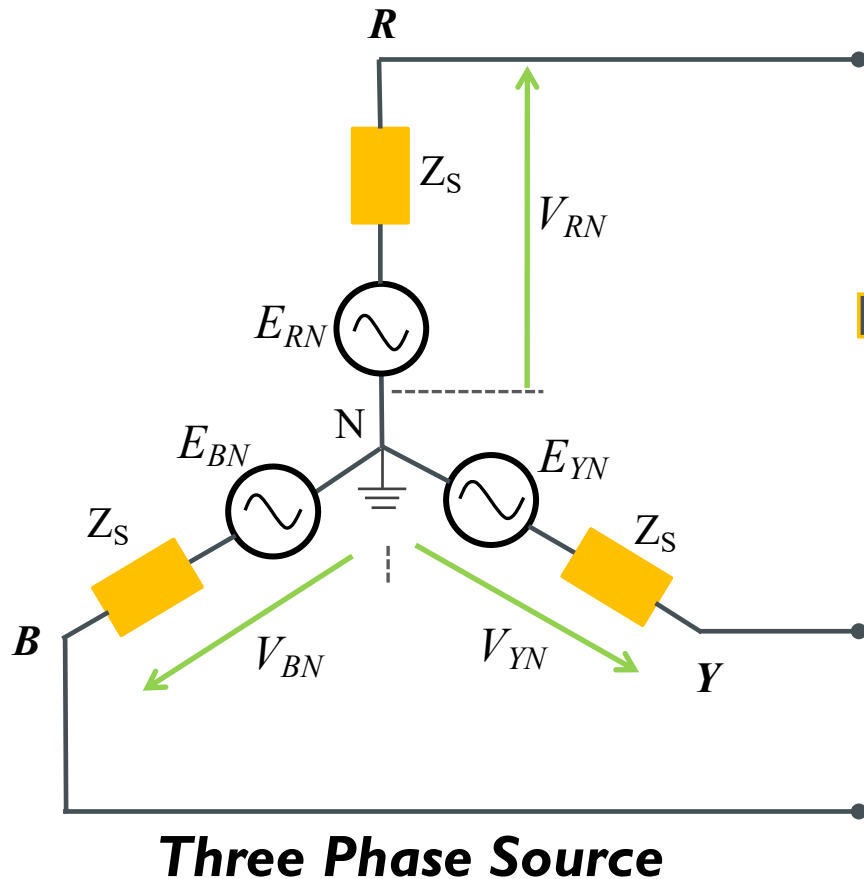
3 Phase Excitation (Phase Voltages).. ---



3 Phase Excitation (Line Voltages)

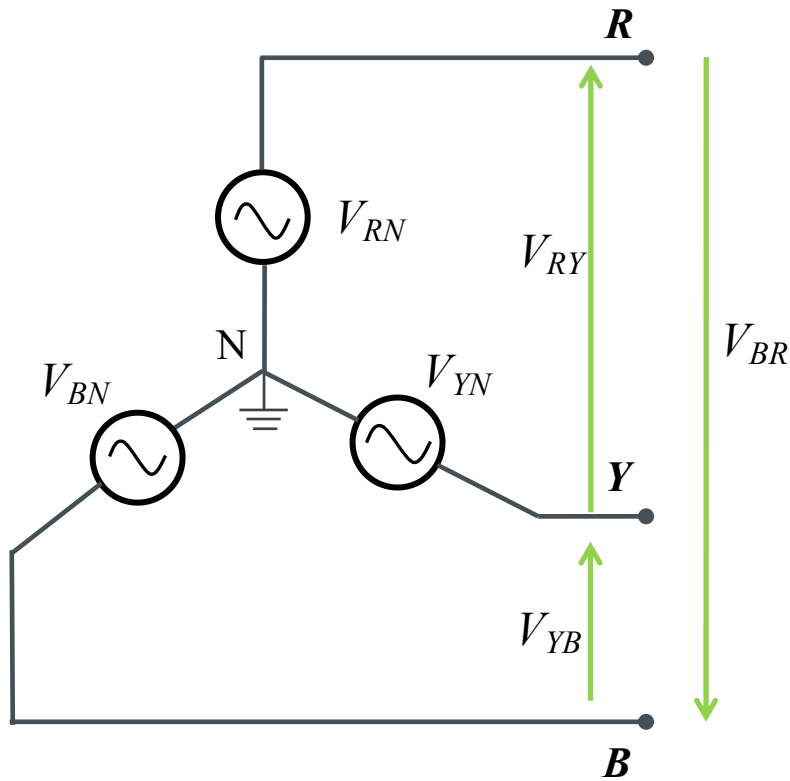

Three Phase Source

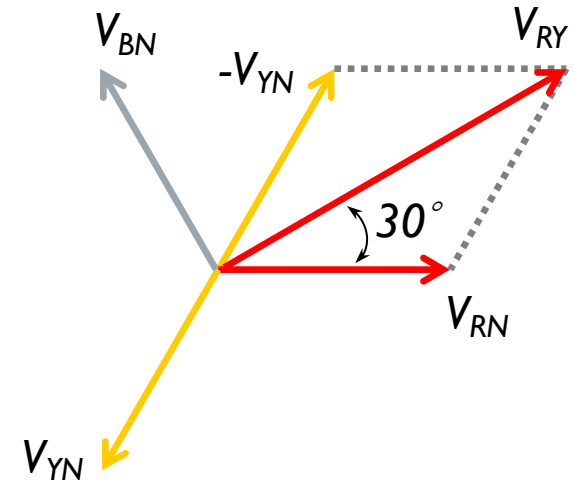

Line Voltages,

$$\begin{aligned}\hat{V}_{RY} &= \hat{V}_{RN} - \hat{V}_{YN} \\ &= V_m \sin(\omega t) - V_m \sin(\omega t - 120^\circ) \\ &= \sqrt{3} \times V_m \sin(\omega t + 30)\end{aligned}$$

3 Phase Excitation (Line Voltages)...



Similarly,


$$\begin{aligned}\hat{V}_{YB} &= \hat{V}_{YN} - \hat{V}_{BN} \\ &= V_m \sin(\omega t - 120) - V_m \sin(\omega t - 240^\circ) \\ &= \sqrt{3} \times V_m \sin(\omega t - 90) \\ &= V_{RY} \sin(\omega t - 120)\end{aligned}$$

$$\begin{aligned}\hat{V}_{BR} &= \hat{V}_{BN} - \hat{V}_{RN} \\ &= V_{RY} \sin(\omega t + 120)\end{aligned}$$

Summing up the Line voltages,

$$\hat{V}_{RY} + \hat{V}_{YB} + \hat{V}_{BR} = 0$$

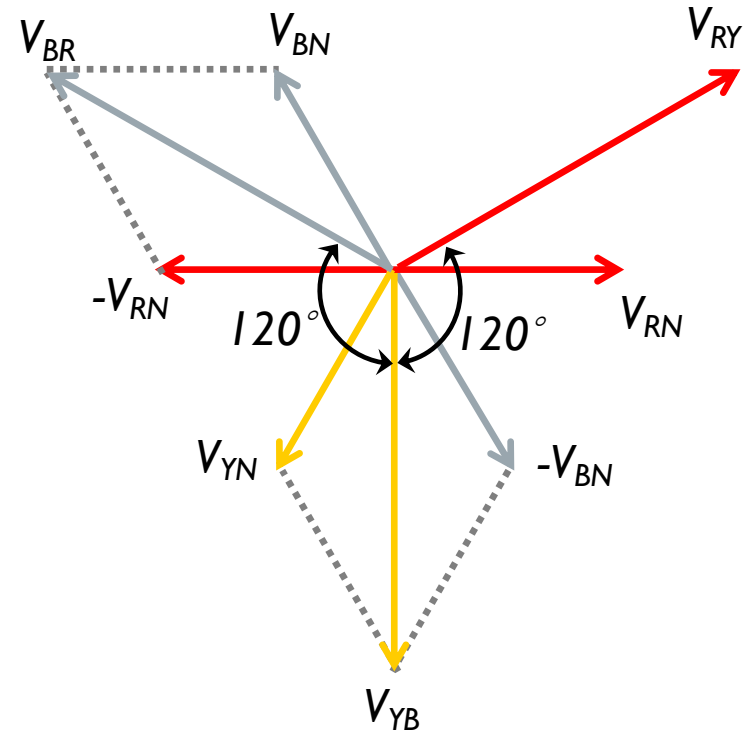In a Three Phase balanced Supply, the summation of Phase voltages and summation of Line Voltages is zero.



Relation b/w Phase & Line Voltages



Phase Voltages

$$\hat{V}_{RN} = V_m \sin(\omega t)$$

$$\hat{V}_{YN} = V_m \sin(\omega t - 120^\circ)$$


$$\hat{V}_{BN} = V_m \sin(\omega t - 240^\circ)$$

Line Voltages

$$\hat{V}_{RY} = \sqrt{3} \times V_m \sin(\omega t + 30^\circ)$$

$$\hat{V}_{YB} = \sqrt{3} \times V_m \sin(\omega t - 90^\circ)$$
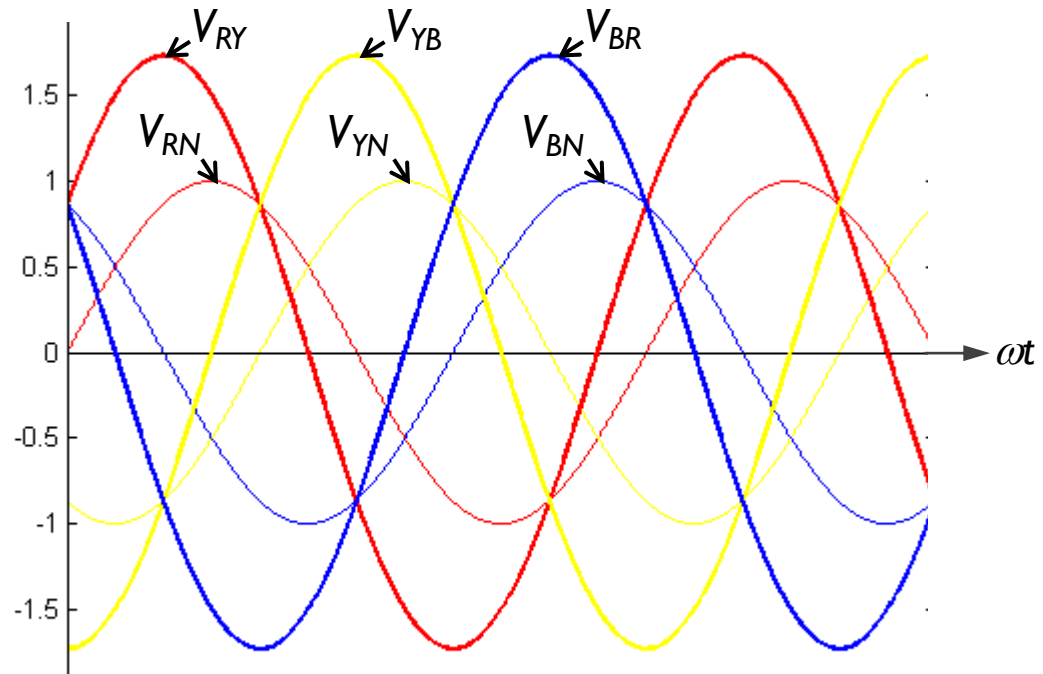
$$\hat{V}_{BR} = \sqrt{3} \times V_m \sin(\omega t + 150^\circ)$$




$$|V_{Line}| = \sqrt{3} |V_{Phase}|$$


Phase Sequence



1. RYB

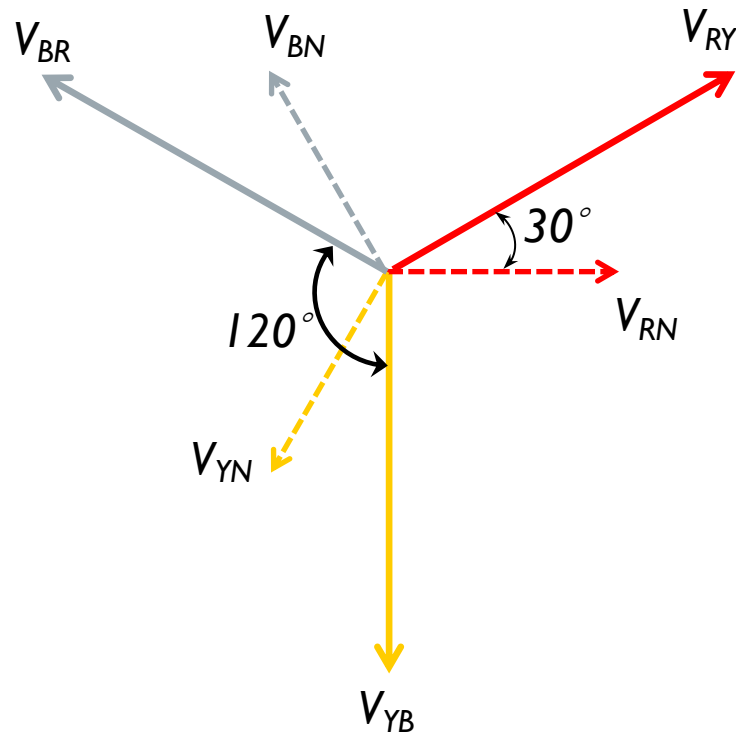

2. RBY

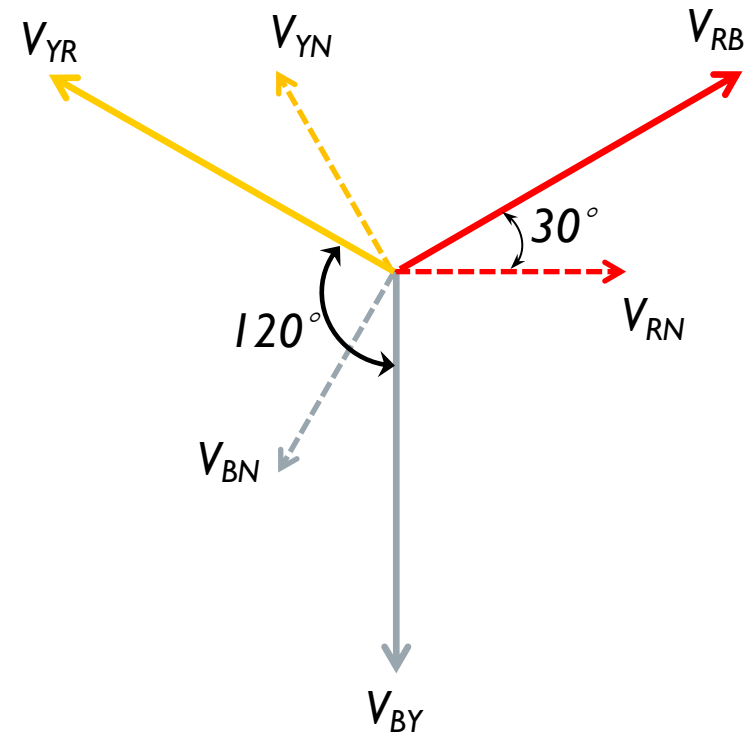

Phase Sequence is the order in which three phases attain their peak or maximum values

Exercise- I



Given the phase voltage V_{RN} of a 3 phase balanced RYB system as 240V, express the phase and line voltages mathematically. Also sketch the phasor diagram.

Solution:

Phase Voltages:

$$\hat{V}_{RN} = 240 \times \sqrt{2} \times \sin(\omega t)$$

$$\hat{V}_{YN} = 240 \times \sqrt{2} \times \sin(\omega t - 120^\circ)$$


$$\hat{V}_{BN} = 240 \times \sqrt{2} \times \sin(\omega t - 240^\circ)$$

Line Voltages:

$$\hat{V}_{RY} = \sqrt{3} \times 240 \times \sqrt{2} \times \sin(\omega t + 30^\circ)$$

$$\hat{V}_{YB} = \sqrt{3} \times 240 \times \sqrt{2} \times \sin(\omega t - 90^\circ)$$

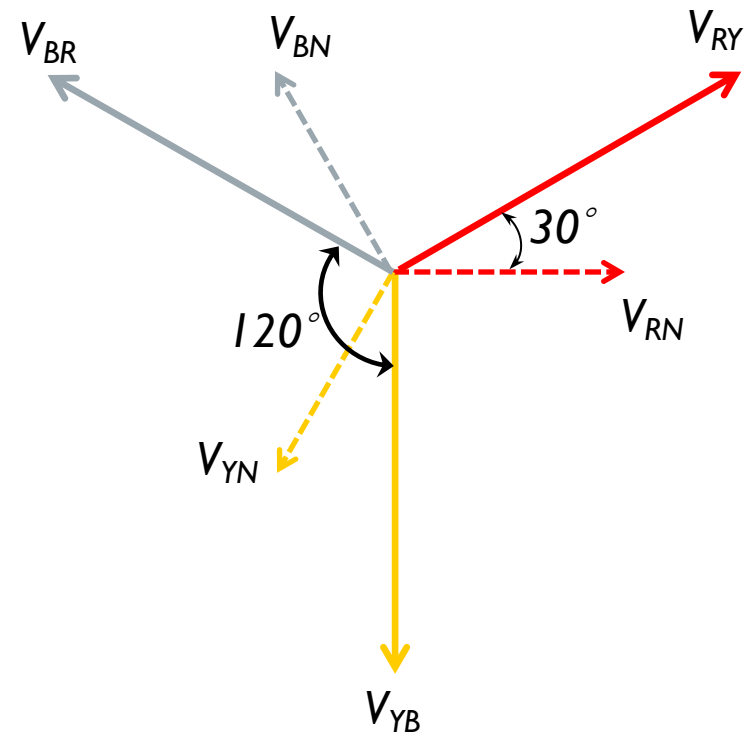
$$\hat{V}_{BR} = \sqrt{3} \times 240 \times \sqrt{2} \times \sin(\omega t + 150^\circ)$$




3 Phase 3 Wire & 4 Wire Supply



3 Phase 3 Wire Supply

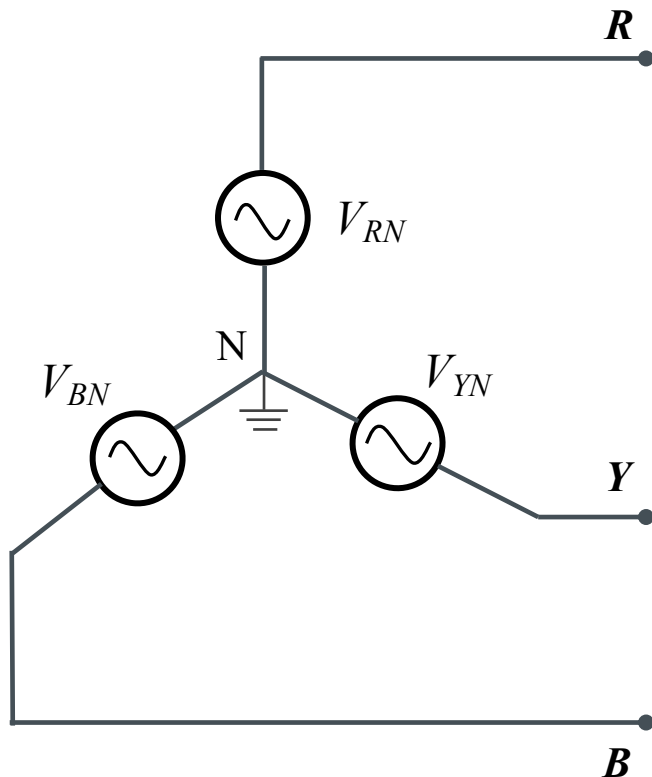


3 Phase 4 Wire Supply

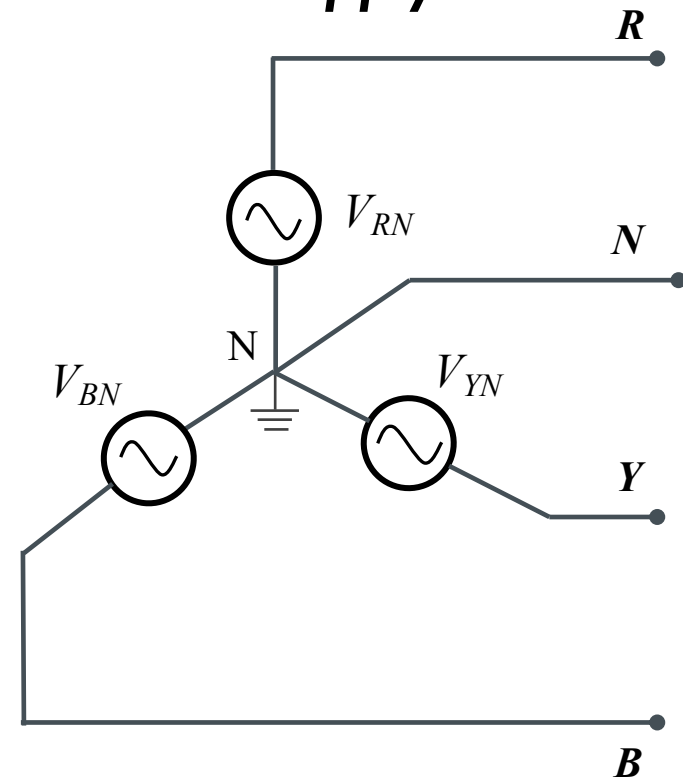

3 Phase Load

- Star Connected Load
- Delta Connected Load

Star Connected Load

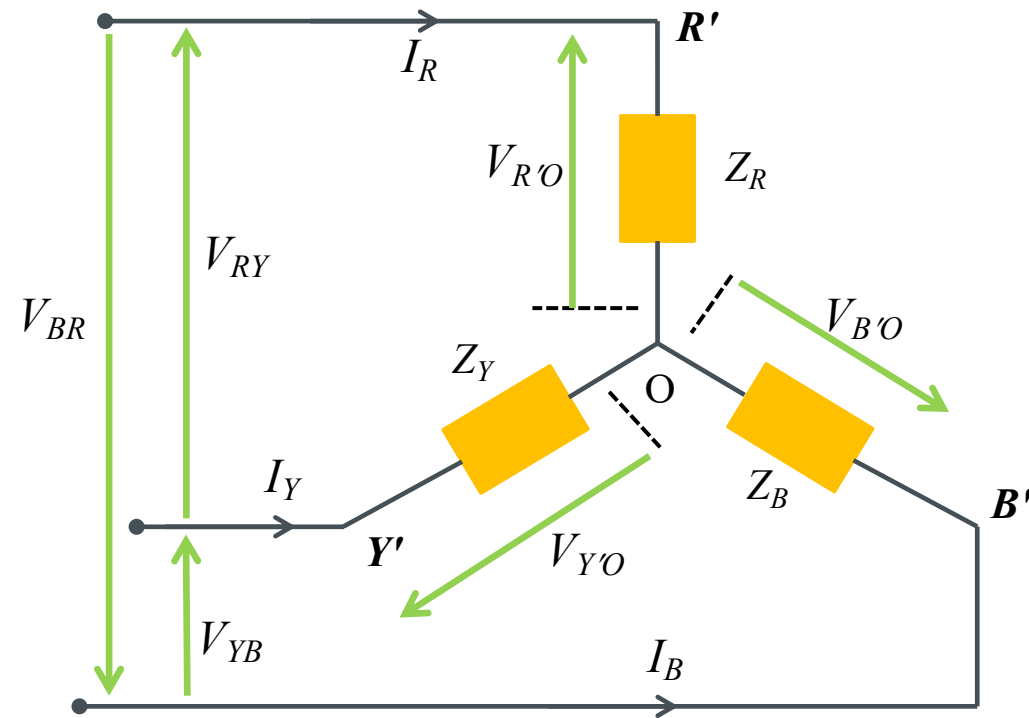


Phase Voltages: $V_{R'O}, V_{Y'O}, V_{B'O}$

Line Voltages:

$$\hat{V}_{RY} = \hat{V}_{R'O} - \hat{V}_{Y'O}$$


$$\hat{V}_{YB} = \hat{V}_{Y'O} - \hat{V}_{B'O}$$
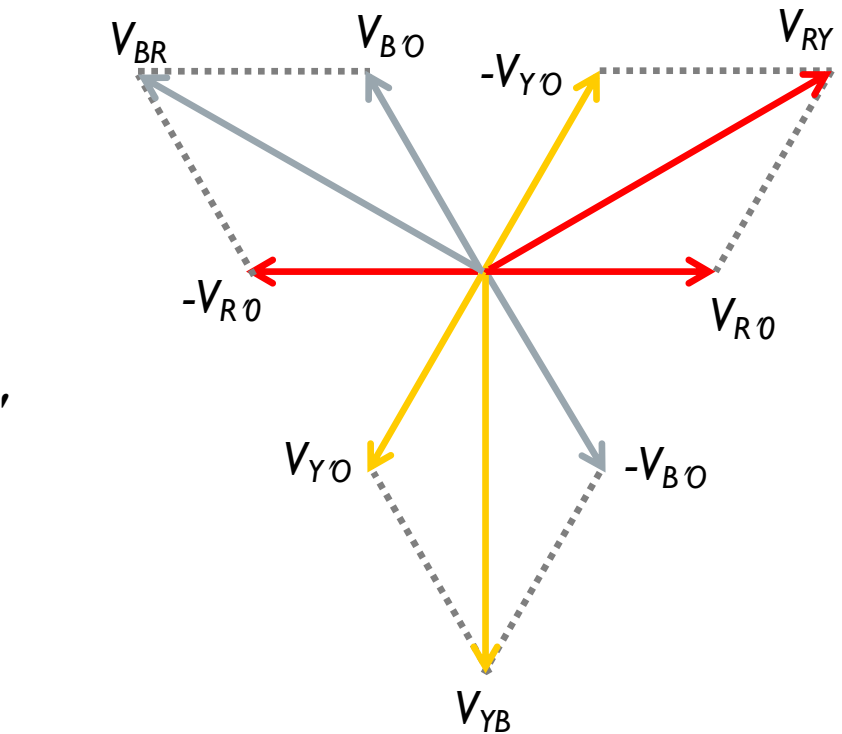
$$\hat{V}_{BR} = \hat{V}_{B'O} - \hat{V}_{R'O}$$


Line Currents = Phase Currents

For Balanced load,
Line Voltage = $\sqrt{3}$ X Phase Voltage

Delta Connected Load

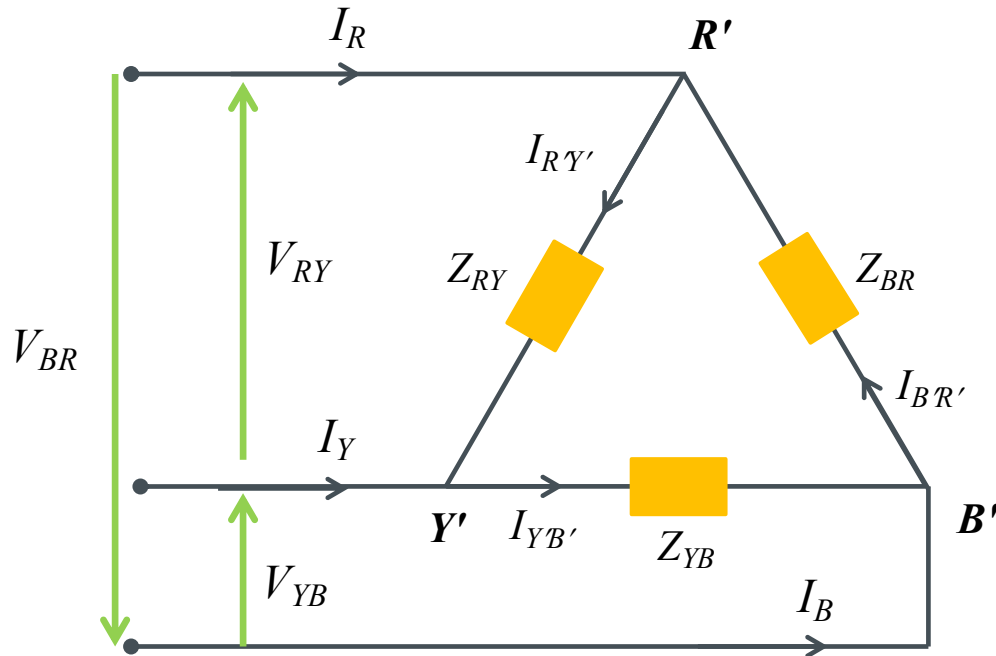


Phase Currents: $I_{RY'}, I_{YB'}, I_{BR'}$

Line Currents: $\hat{I}_R = \hat{I}_{R'Y'} - \hat{I}_{B'R'}$

$\hat{I}_Y = \hat{I}_{Y'B'} - \hat{I}_{R'Y'}$

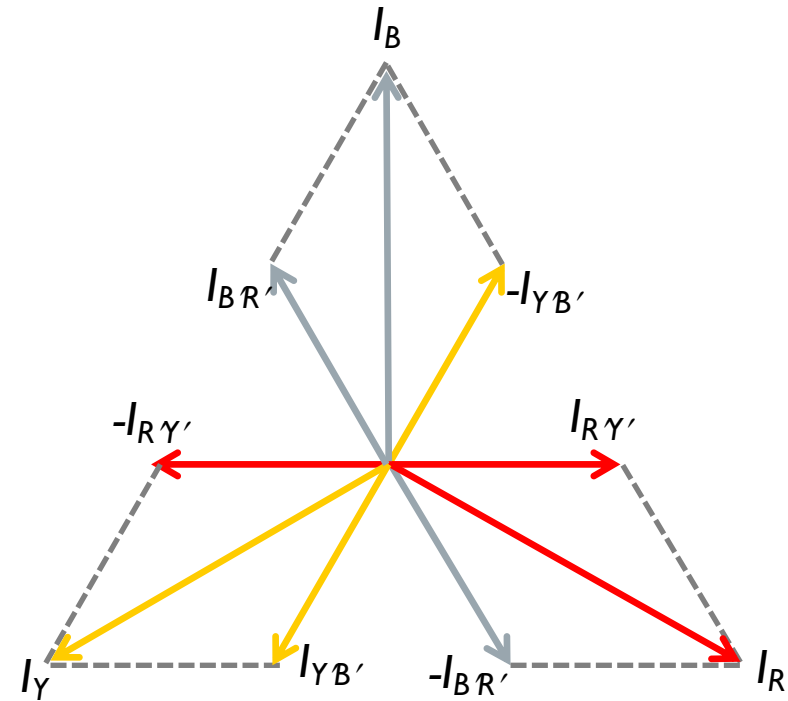
$\hat{I}_B = \hat{I}_{B'R'} - \hat{I}_{Y'B'}$




Phase Voltages = Line Voltages

For Balanced load,
Line Current = $\sqrt{3}$ X Phase Current

3 Phase 4 Wire System

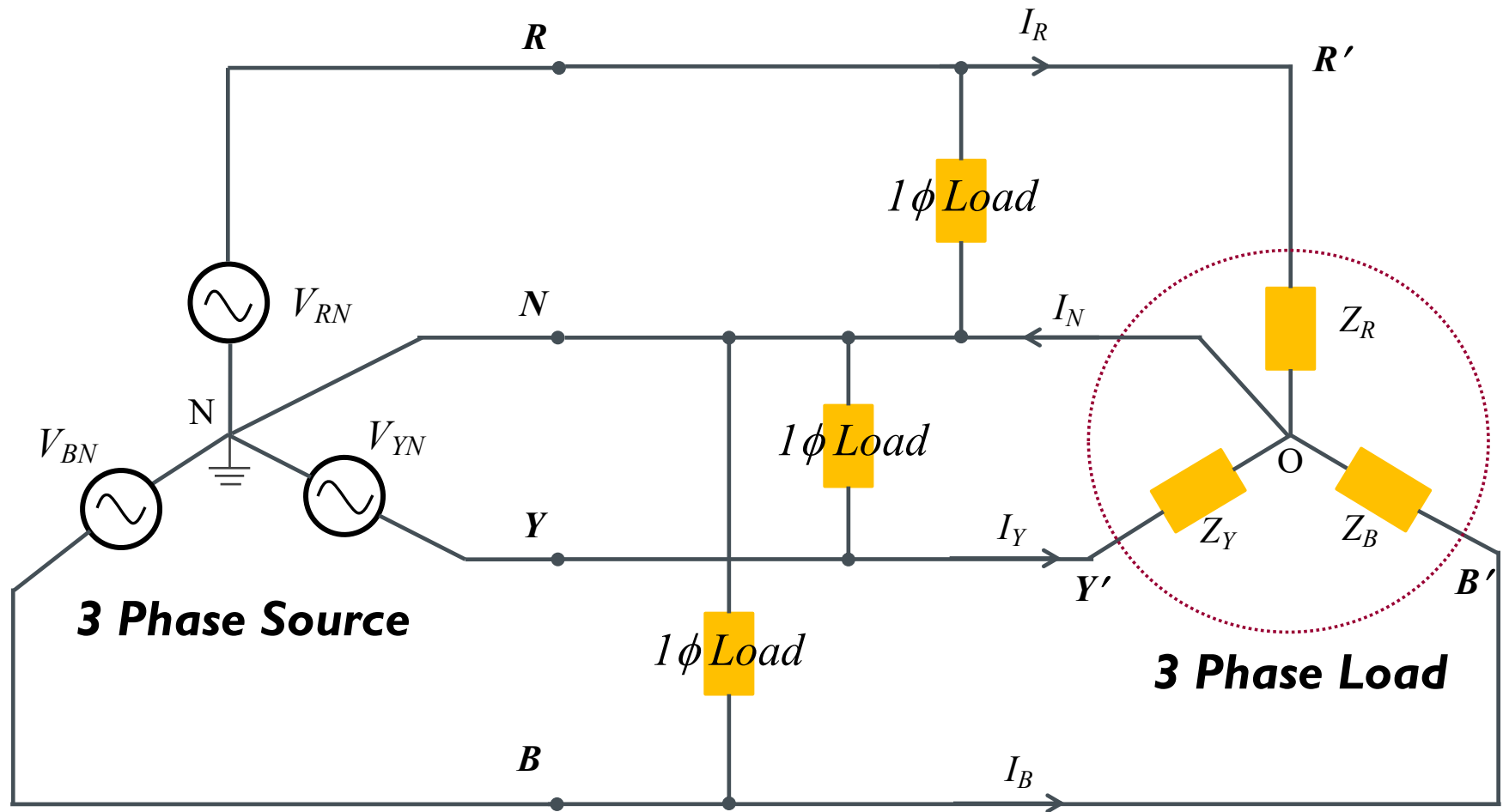

3 Phase 3 wire System

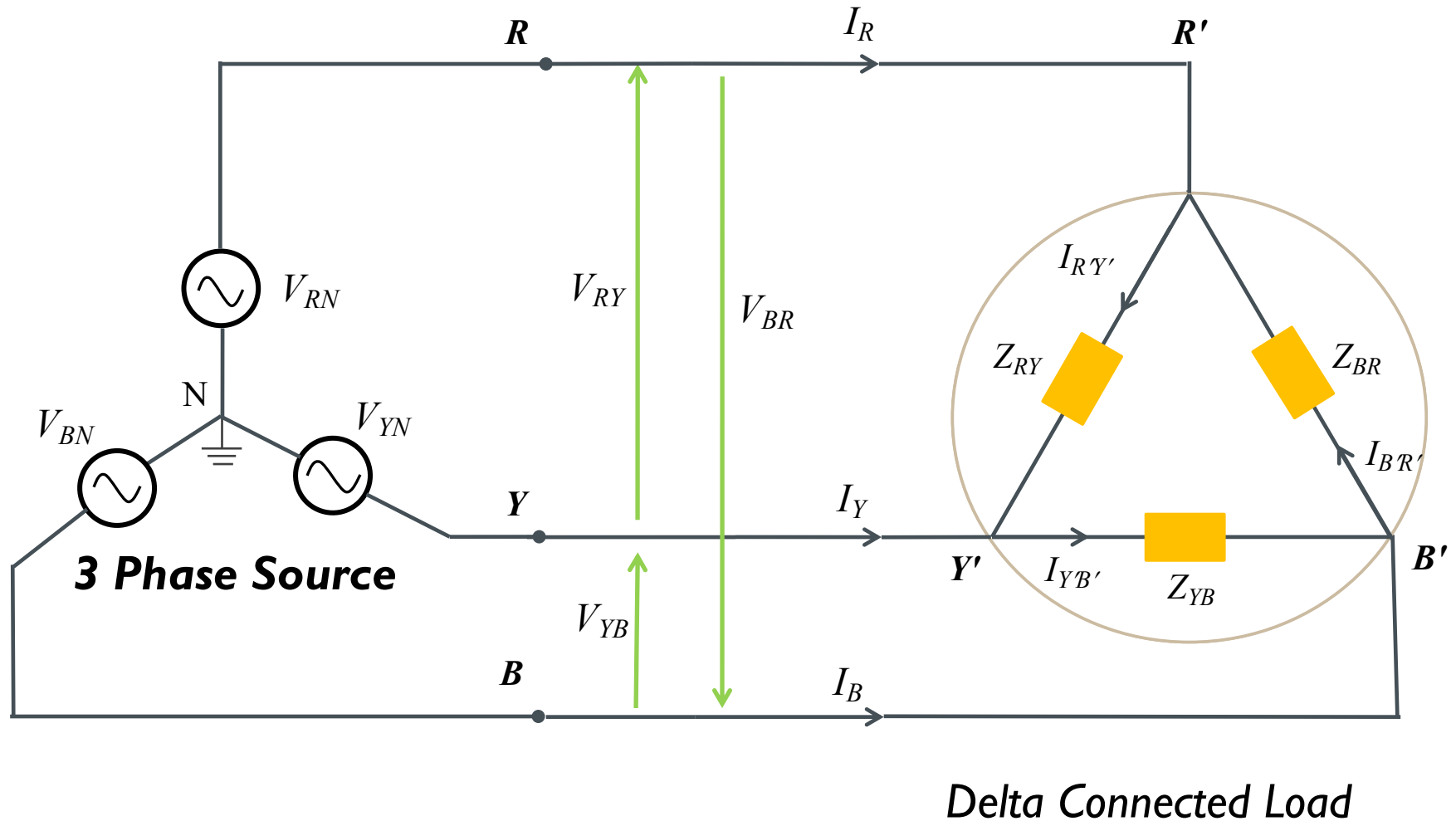

Summary



In a three phase balanced supply,

- ✓ *Summation of phase voltages = zero*
- ✓ *Summation of Line voltages = zero*
- ✓ *Line voltage is $\sqrt{3}$ x Phase Voltage*
- ✓ *In an RYB sequence, V_{RY} leads V_{RN} by 30°*
- ✓ *Power transmission is generally through 3 phase 3 wire network and distribution is through 3 phase 4 wire network.*
- ✓ *For Balanced Star connected load, the line voltage = $\sqrt{3}$ x phase voltage.*
- ✓ *For Balanced Delta connected load, the line current = $\sqrt{3}$ x phase current*