

# Basic Electrical Technology


[ELE 105 I]

---

## ***CHAPTER 3 - SINGLE PHASE AC CIRCUITS***

***(3.3)***

# RL circuit analysis

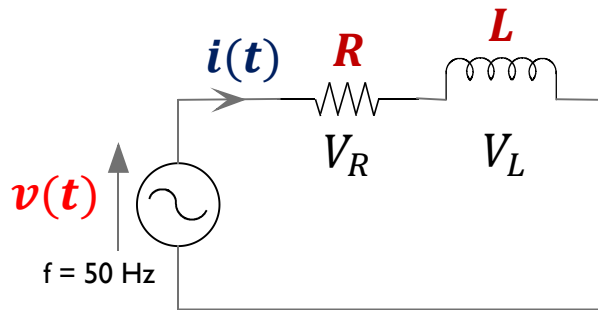

Let  $\bar{I}$  be along the reference

$$\bar{V}_R = \bar{I}R$$

$$\bar{V}_L = j\bar{I}X_L$$

$$\bar{V} = \bar{V}_R + \bar{V}_L = |V|\angle\phi$$


## Mathematical Representation

$$i(t) = I_m \sin(\omega t)$$


$$v(t) = V_m \sin(\omega t + \phi)$$

$\phi$  – Phase Angle

## Graphical Representation

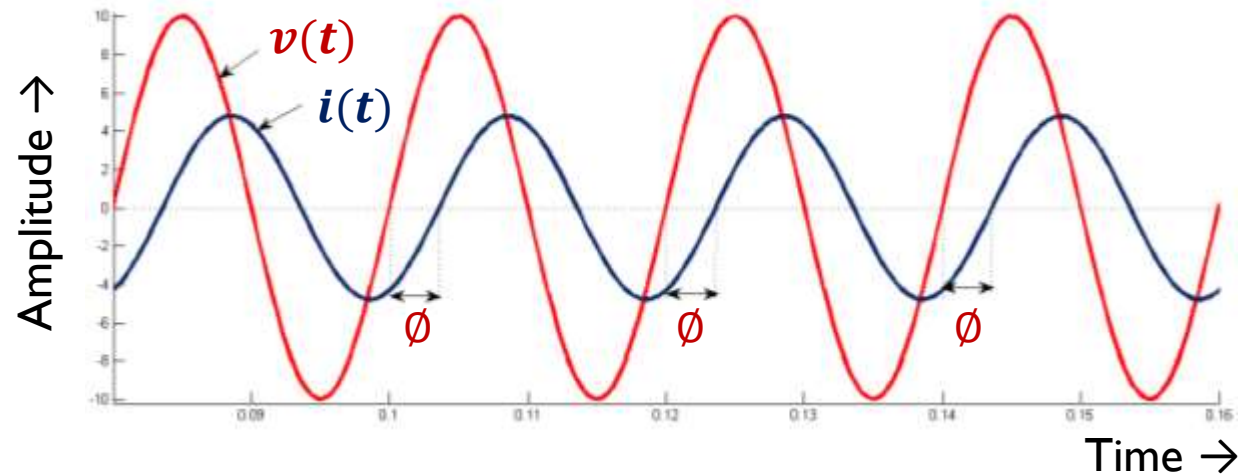

## Phasor Representation

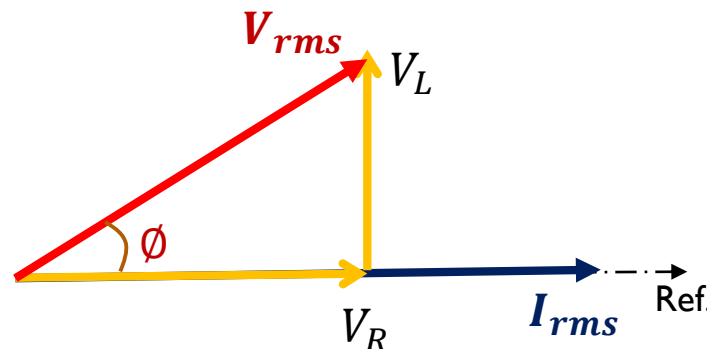

## Impedance


$$\frac{\bar{V}}{\bar{I}} = \frac{\bar{I}(R + jX_L)}{\bar{I}} = R + jX_L = |Z|\angle\phi$$

$Z$  – Impedance of the circuit

$$\therefore R = |Z| \cos \phi \quad X_L = |Z| \sin \phi$$

$$|Z| = \sqrt{R^2 + X_L^2} \quad \phi = \tan^{-1} \frac{X_L}{R}$$

# Power associated - RL circuit

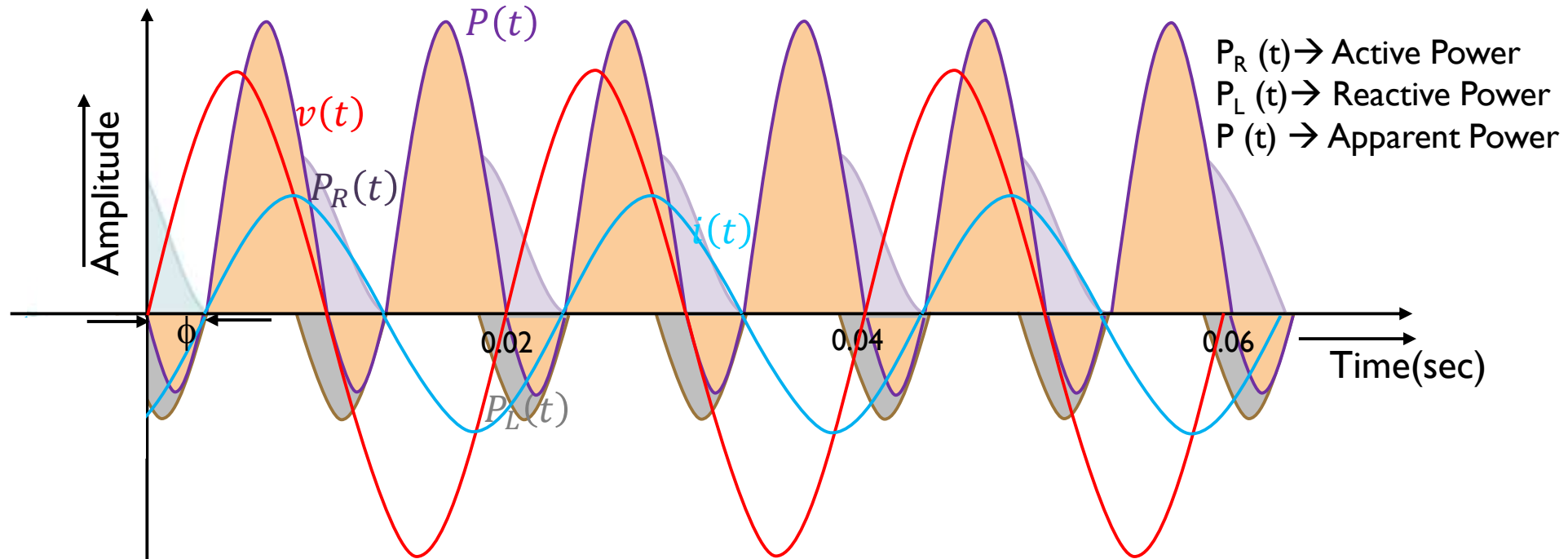

Instantaneous power,

$$p(t) = v(t) \cdot i(t)$$

$$= V_m I_m \sin \omega t \cdot \sin(\omega t + \phi)$$


$$= V_{rms} I_{rms} [\cos \phi - \cos(2\omega t + \phi)]$$

$$\text{Average Power, } P = \frac{1}{T} \int_0^T p(t) dt = \frac{V_m I_m}{2} \cos \phi$$

$$\boxed{P_{avg} = V_{rms} I_{rms} \cos \phi}$$

$\cos \phi$  is called the **Power Factor**

# RC circuit analysis

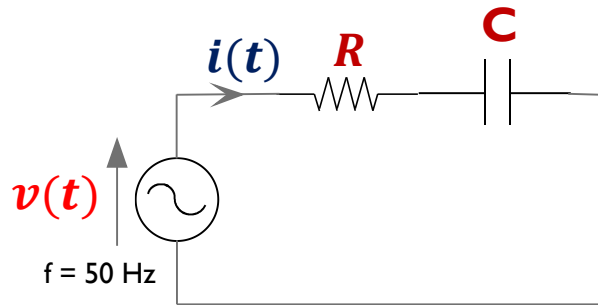

Let  $\bar{I}$  be along the reference

$$\bar{V}_R = \bar{I}R$$

$$\bar{V}_C = -j\bar{I}X_C$$

$$\bar{V} = \bar{V}_R + \bar{V}_C = |V|\angle -\phi$$


Mathematical Representation

$$i(t) = I_m \sin(\omega t)$$


$$v(t) = V_m \sin(\omega t - \phi)$$

$\phi$  – Phase Angle

Graphical Representation

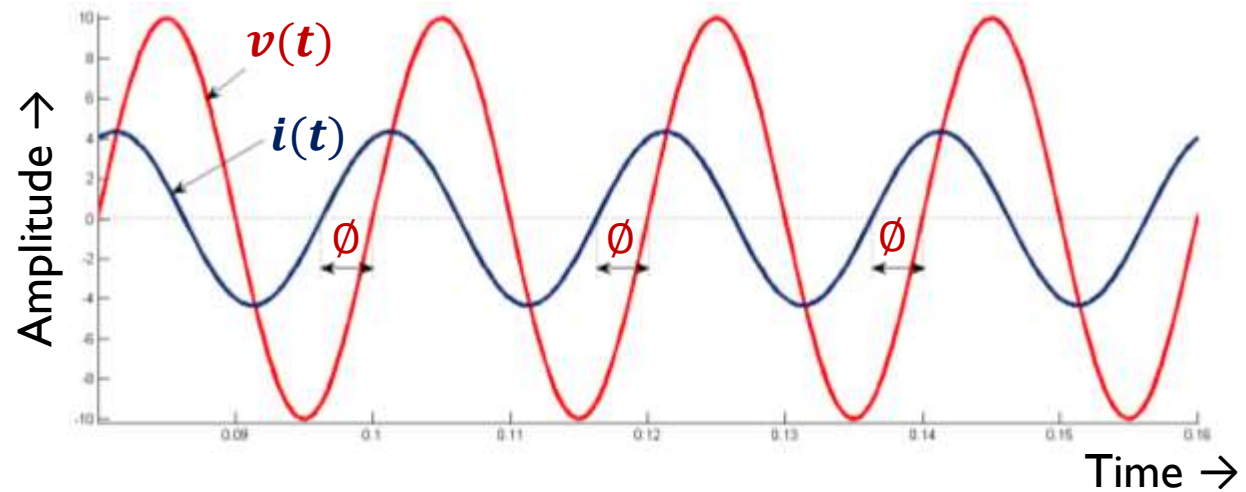

Phasor Representation

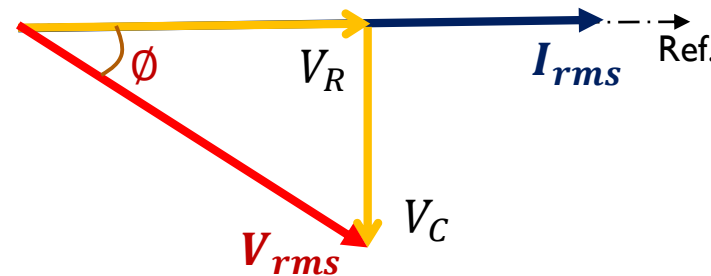

Impedance


$$\frac{\bar{V}}{\bar{I}} = \frac{\bar{I}(R - jX_C)}{\bar{I}} = R - jX_C = |Z|\angle -\phi$$

$Z$  – Impedance of the circuit

$$\therefore R = |Z| \cos \phi \quad X_C = |Z| \sin \phi$$

$$|Z| = \sqrt{R^2 + X_C^2} \quad \phi = \tan^{-1} \frac{X_C}{R}$$

# Power associated - RC circuit

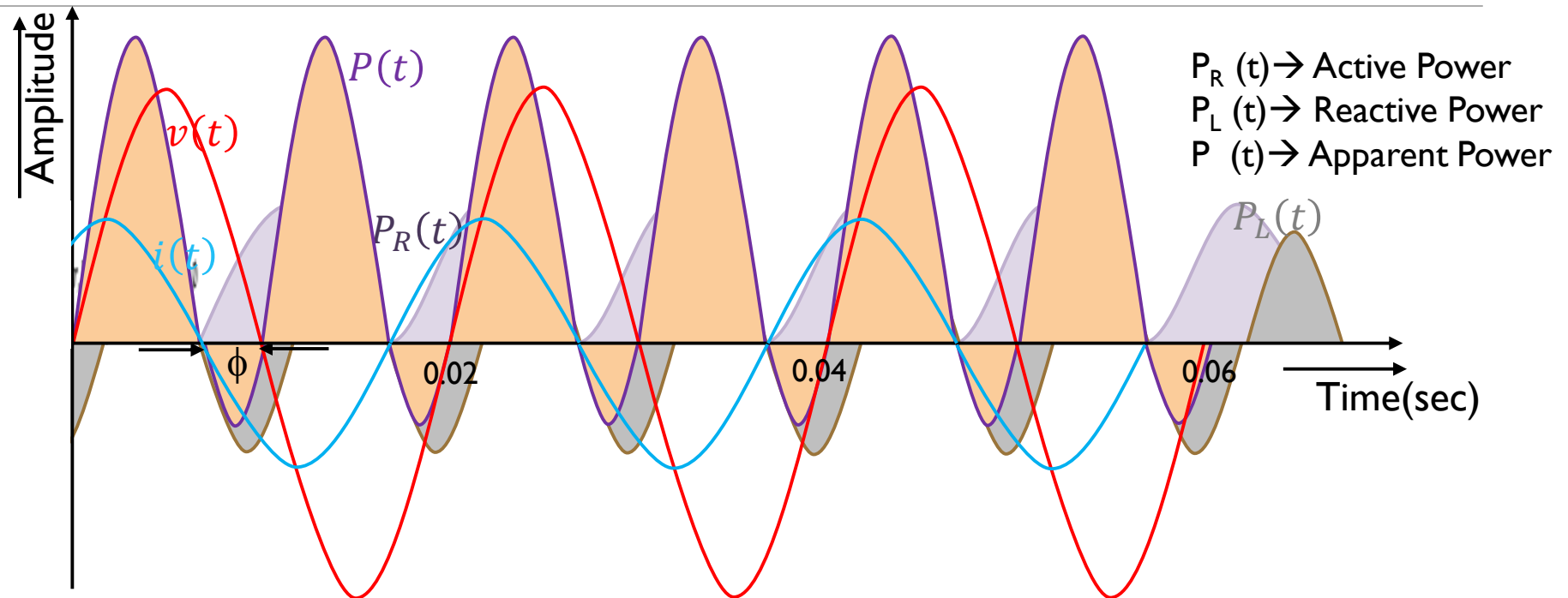


Instantaneous power,

$$\begin{aligned}
 p(t) &= v(t) \cdot i(t) \\
 &= V_m I_m \sin \omega t \cdot \sin(\omega t - \phi) \\
 &= V_{rms} I_{rms} [\cos \phi - \cos(2\omega t - \phi)]
 \end{aligned}$$

$$\text{Average Power, } P = \frac{1}{T} \int_0^T p(t) dt = \frac{V_m I_m}{2} \cos \phi$$

$$\boxed{P_{avg} = V_{rms} I_{rms} \cos \phi}$$

# RLC circuit

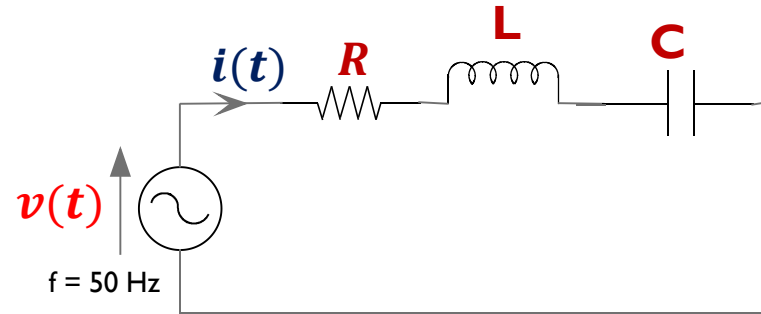

Let  $i(t)$  be the reference

**Impedance,  $Z = R + j(X_L \sim X_C)$**



$\text{if } X_L = X_C$	$\Rightarrow$	Resistive circuit (Resonance condition)
$\text{if } X_L > X_C$	$\Rightarrow$	RL series circuit
$\text{if } X_L < X_C$	$\Rightarrow$	RC series circuit

# Illustration I

A resistance of  $50\Omega$  is connected in series with an inductance of  $200\text{mH}$  and capacitance of  $101.321\mu\text{F}$  across a  $230\text{V}, 50\text{ Hz}$ , single phase AC supply. Obtain,


- a) Impedance of the circuit
- b) Current drawn
- c) Power factor
- d) Power consumed
- e) Phasor diagram

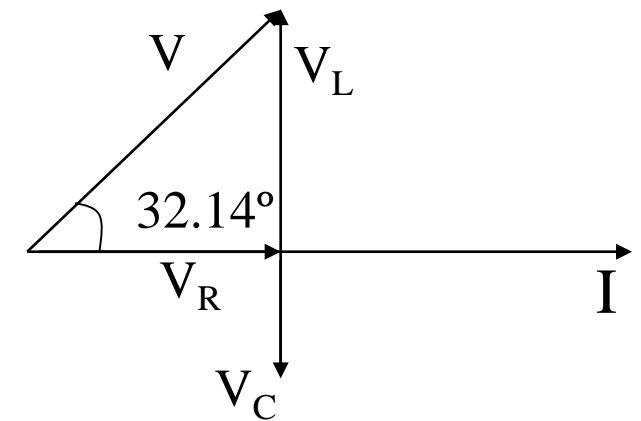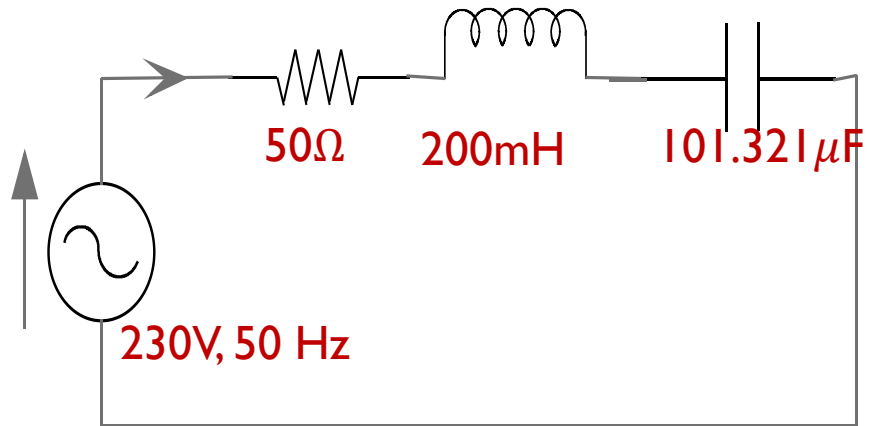- a)  $Z = 50 + j31.4156\Omega = 59.050\angle 32.14^\circ \Omega$
- b)  $I = 3.898\angle -32.14^\circ \text{ A}$
- c)  $PF = 0.846 \text{ lag}$
- d)  $P = 759.15\text{ W}$


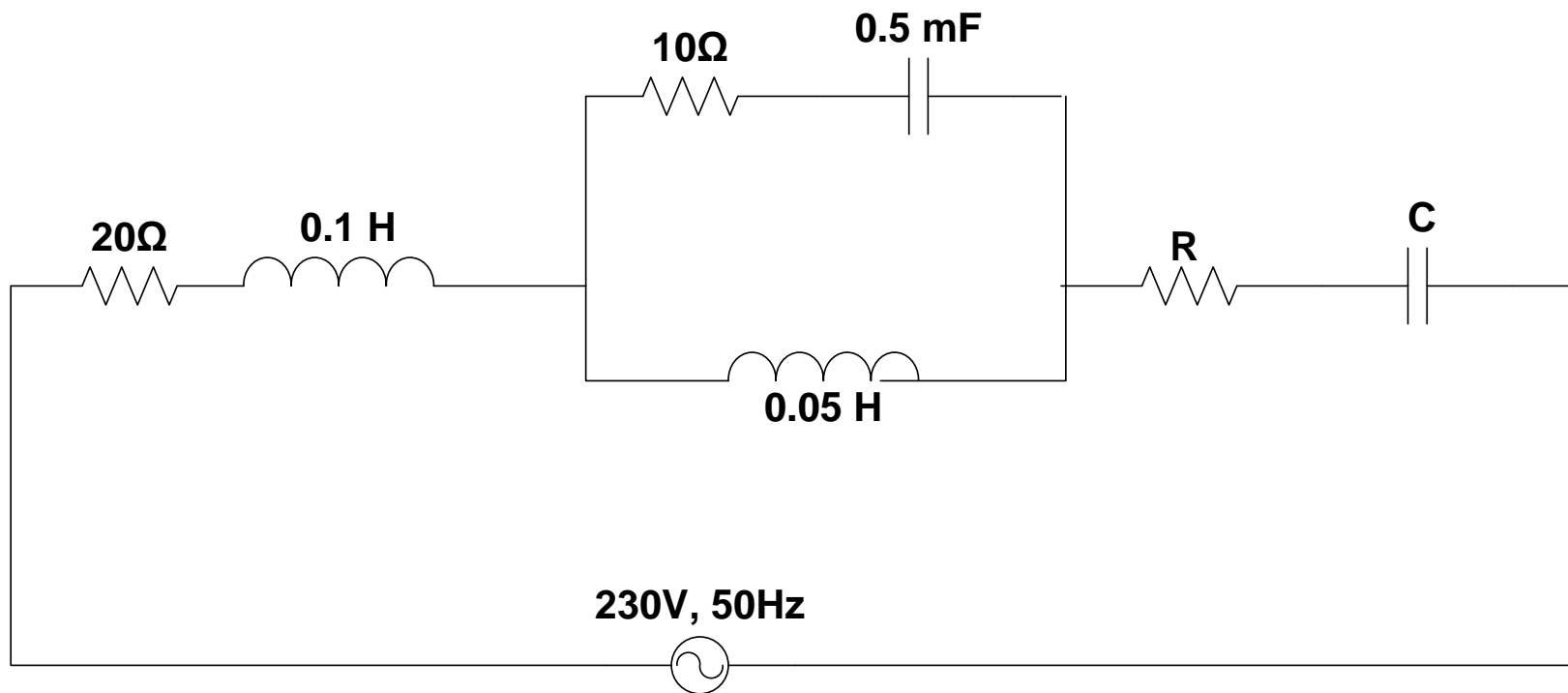
# Illustration 2

The circuit shown below has a source of 230V, 50 Hz. If the current through 0.05H inductor is  $3.5 \angle -80^\circ$  A, find the value of 'R' and 'C'.



$$R = 23.58\ \Omega$$
$$C = 0.104\text{ mF}$$





# Thank You!