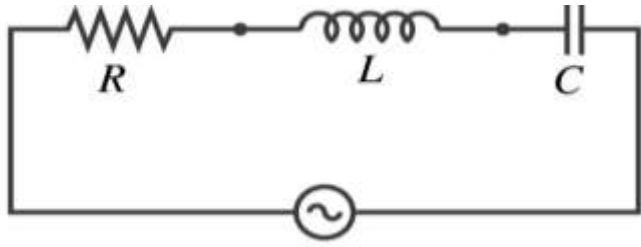


Basic Electrical Technology

[ELE 105 I]

CHAPTER 3 - RESONANCE


Series Resonance



$v(t)$, variable frequency

$$Z = R + j(X_L \sim X_C)$$

$$|Z| = \sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}$$

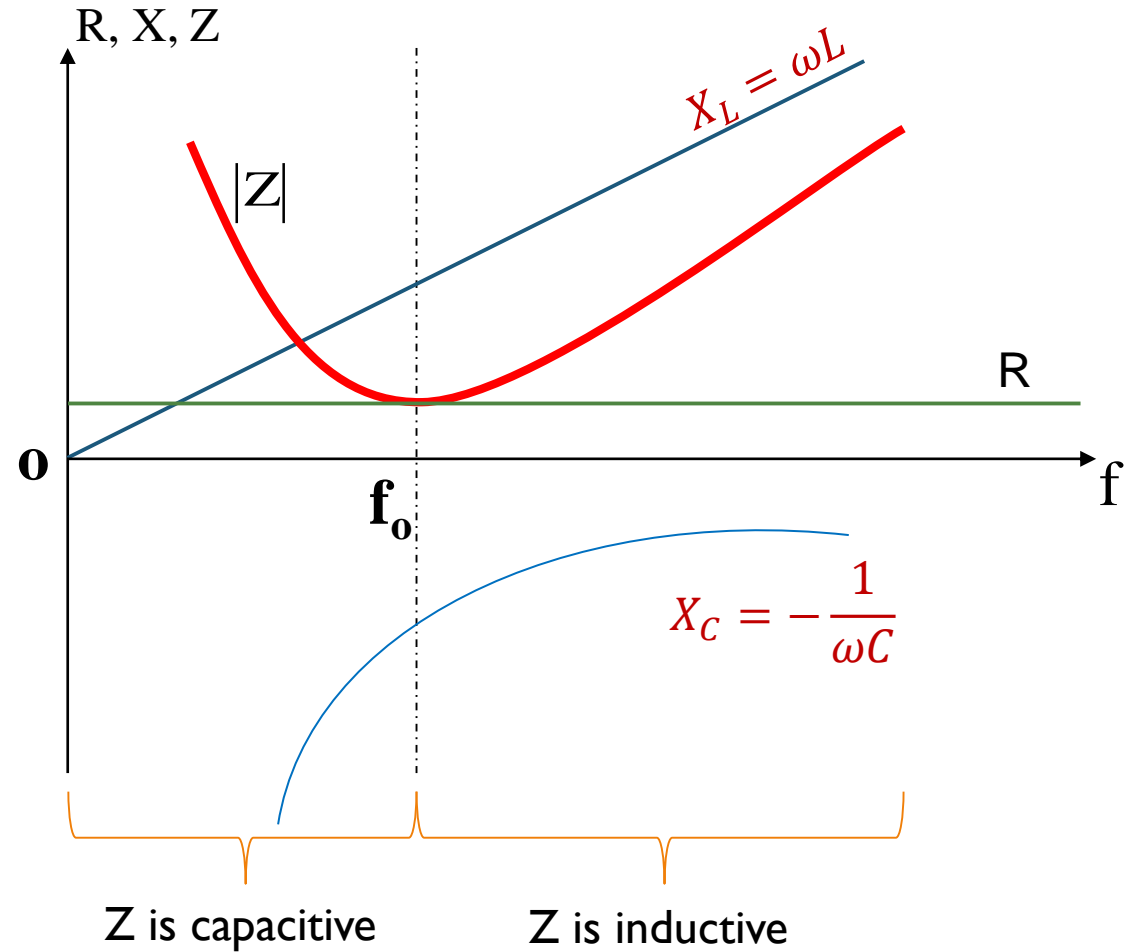

' f_0 is called the resonant frequency'

Series Resonance

- **When series RLC circuit is at resonance,**

- Current is in phase with voltage
- Circuit power factor is unity
- $X_L = X_C$
- $Z = R$


- **Resonant frequency for a series RLC circuit is obtained as follows:**

Imaginary part of $Z_{eq} = 0$

$$X_L = X_C$$

$$\omega_0 L = \frac{1}{\omega_0 C}$$
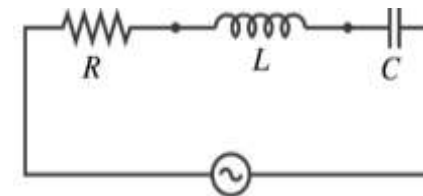
$$f_0 = \frac{1}{2\pi\sqrt{LC}} \text{ hertz}$$




$v(t)$, variable frequency

$$Z = R + j(X_L \sim X_C)$$

Current vs. Frequency in RLC Series Circuit

Variation of current with frequency

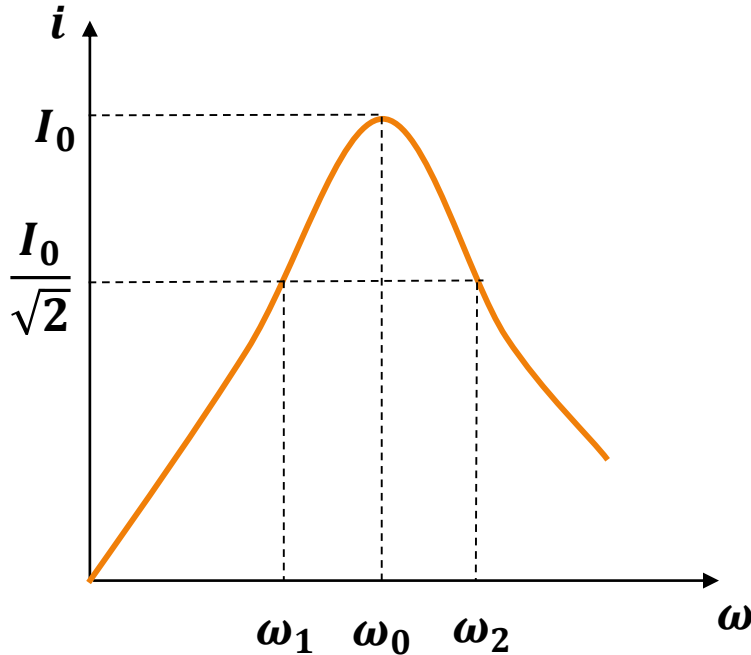

$$I_0 = I_{max} = \frac{V_{rms}}{R}$$

- **Half Power Frequency**

‘Frequency at which the power is half of the power at resonant frequency’

$$Power = \frac{1}{2} I_0^2 R = \left(\frac{I_0}{\sqrt{2}} \right)^2 R$$

$$\text{At } \omega_1 \text{ and } \omega_2, I = \frac{I_0}{\sqrt{2}}$$

ω_1 = Lower half power frequency

ω_2 = Upper half power frequency

$$\text{Bandwidth} = \omega_2 - \omega_1$$

In practice the curve of $|I|$ against ω is not symmetrical about the resonant frequency

Half Power Frequency

$$\text{Impedance at } \omega_1 \text{ and } \omega_2, |Z| = \frac{V_0}{\frac{I_0}{\sqrt{2}}} = \sqrt{2}R$$

Below Resonant frequency ω_0 , $|X_C| > |X_L|$

At ω_1 ,

$$\sqrt{R^2 + (X_C - X_L)^2} = \sqrt{2}R$$

$$X_C - X_L = R$$

$$\frac{1}{\omega_1 C} - \omega_1 L = R$$

$$\omega_1 = \frac{-R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}}$$

Above Resonant frequency ω_0 , $|X_L| > |X_C|$

At ω_2 ,

$$\sqrt{R^2 + (X_L - X_C)^2} = \sqrt{2}R$$

$$X_L - X_C = R$$

$$\omega_2 L - \frac{1}{\omega_2 C} = R$$

$$\omega_2 = \frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}}$$

$$\omega_2 \omega_1 = \frac{1}{LC} = \omega_0^2$$

$$\omega_2 - \omega_1 = \frac{R}{L}$$

Quality Factor for series circuit

- At resonance, V_C and V_L can be very much greater than applied voltage

$$|V_C| = |I|X_C = \frac{V \cdot X_C}{\sqrt{R^2 + (X_L - X_C)^2}}$$

At resonance, $X_L = X_C$

$$V_C = \frac{V}{R} X_C$$

$$V_C = \frac{V}{\omega_0 CR} = QV$$

Q is termed the Q factor or voltage magnification

- High value of Q can lead to component damage
- Careful design necessary
- Larger the value of Q, more symmetrical the curve appears about the resonant frequency

$$Q = \frac{1}{\omega_0 CR} = \frac{\omega_0 L}{R} = \frac{1}{R} \sqrt{\frac{L}{C}}$$

$$Q = \frac{\text{Resonant frequency}}{\text{Bandwidth}}$$

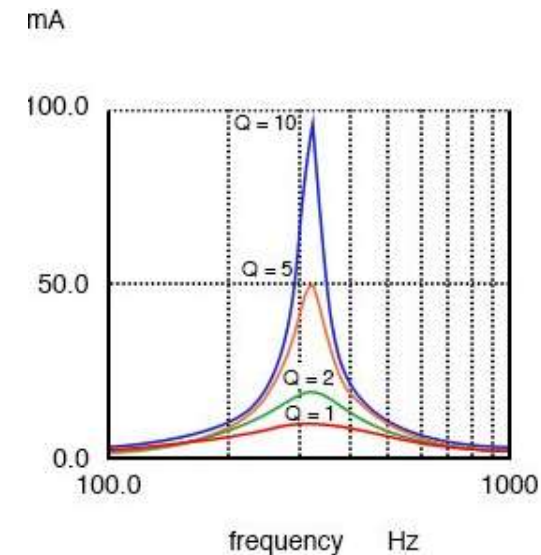


Illustration I

A circuit having a resistance of 4Ω and inductance of $0.5H$ and a variable capacitance in series, is connected across a $100V, 50Hz$ supply. Calculate:

- a) The capacitance to give resonance
- b) The voltages across the inductor and the capacitor
- c) The Q factor of the circuit


$$\begin{aligned} \text{a) } C &= 20.26\mu F \\ \text{b) } V_C &= 3926.99 \text{ V} \\ \text{c) } Q\text{-factor} &= 39.26 \end{aligned}$$

Illustration 2

The bandwidth of a series resonant circuit is **500 Hz**. If the resonant frequency is **6000 Hz**, what is the value of Q ? If **$R = 10 \Omega$** , what is the value of the inductive reactance at resonance? Calculate the inductance and capacitance of the circuit

$$C = 0.22 \mu F$$

Resonance in parallel circuits

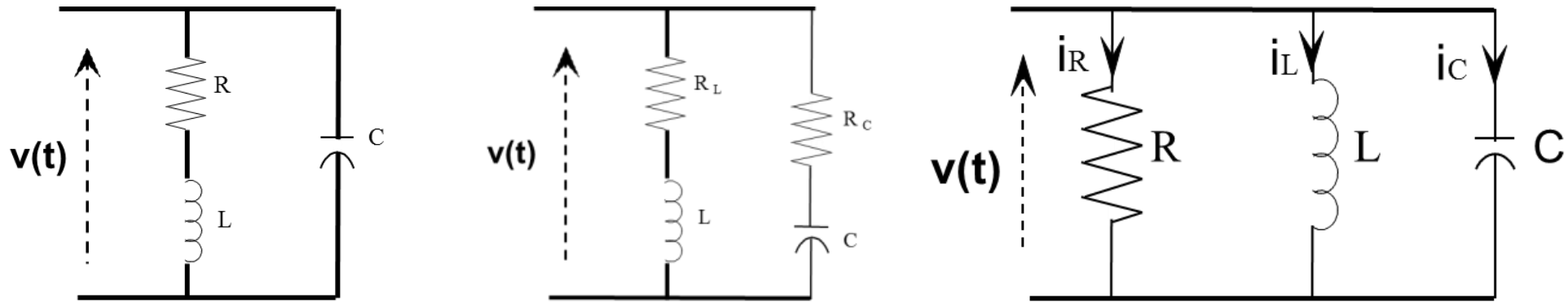


Steps to obtain the expression of resonant frequency in parallel circuits

- Obtain the net admittance of the circuit ; $Y_{eq} = y_1 + y_2 + \dots$
 $Y_{eq} = G_{eq} \pm jB_{eq}$
- Equate the imaginary part (susceptance) to zero; $B_{eq} = 0$ and obtain the expression of ω_r


The expression for resonant frequency depends on circuit configuration

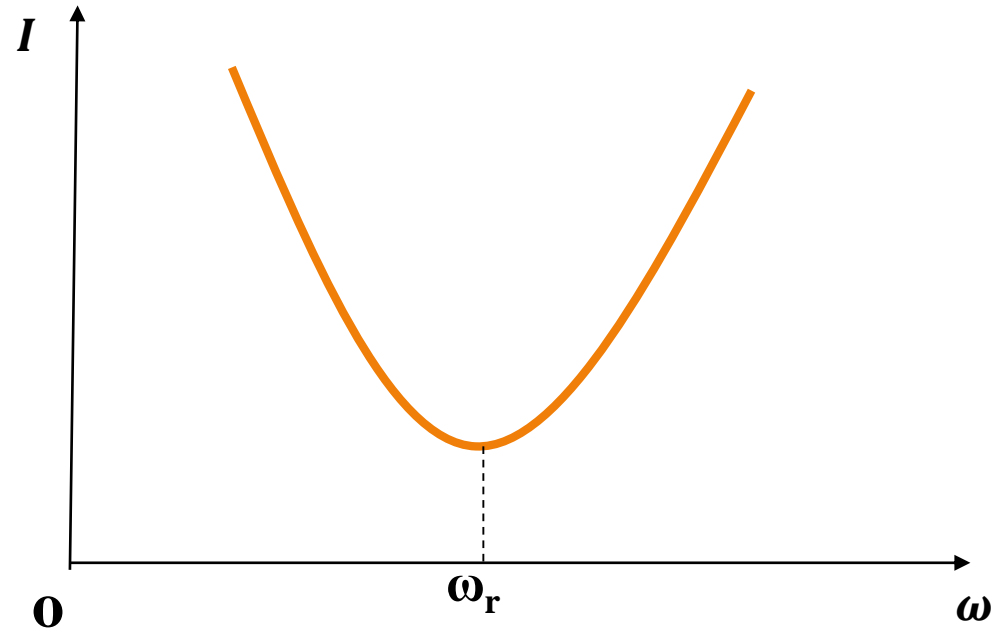Current vs. Frequency in parallel Circuits



- At resonance
 - Impedance is maximum
 - Resultant current minimum

Parallel resonance circuits

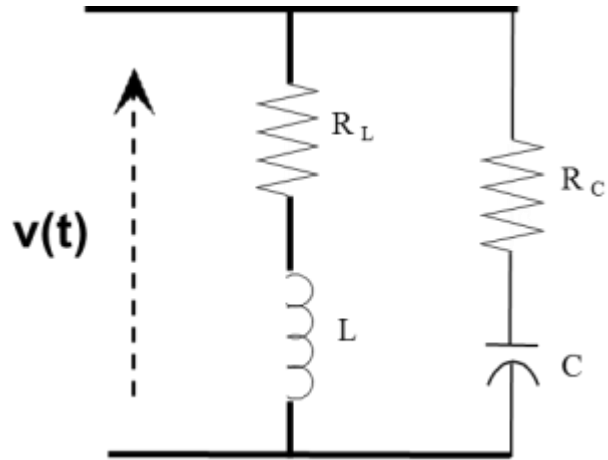

$$y_{eq} = \frac{1}{R_L + jX_L} + \frac{1}{R_C - jX_C}$$

$$y_{eq} = \frac{R_C - jX_C + R_L + jX_L}{(R_L R_C + X_L X_C) - j(R_L X_C - X_L R_C)}$$

Rationalizing ;

$$y_{eq} = \frac{((R_L R_C + X_L X_C) + j(R_L X_C - X_L R_C))(R_C - jX_C + R_L + jX_L)}{(R_L R_C + X_L X_C)^2 + (R_L X_C - X_L R_C)^2}$$

Separating the real & imaginary terms ;

$$y_{eq} = \frac{1}{(R_L R_C + X_L X_C)^2 + (R_L X_C - X_L R_C)^2} (R_L^2 R_C + R_L R_C^2 - R_L X_C^2 - X_L^2 R_C) + j(R_L^2 X_C + X_C X_L^2 - X_L R_C^2 - X_C^2 X_L)$$

Parallel resonance circuits

Equating the imaginary part to zero;

$$B_{eq} = 0 ;$$

$$R_L^2 X_C + X_C X_L^2 - X_L R_C^2 - X_C^2 X_L = 0$$

Solving for ω_0 ;

$$\omega_0 = \frac{1}{\sqrt{LC}} \sqrt{\frac{R_L^2 C - L}{R_C^2 C - L}}$$

If $R_L = R_C$:

$$f_0 = \frac{1}{2\pi\sqrt{LC}}$$

Exercise I


A parallel circuit with an RL series branch ($R = 20 \, \Omega$ and $L = 50 \, \text{mH}$) and an RC series branch ($R = 10 \, \Omega$ and $C = 100 \, \mu\text{F}$) are connected to a variable frequency voltage source. Find at what frequency the circuit will resonate?

Ans:

$$\omega_c = \frac{1}{\sqrt{LC}} \sqrt{\frac{R_L^2 C - L}{R_C^2 C - L}} = 223.6067 \, \text{rad/sec} = 35.58 \, \text{Hz}$$

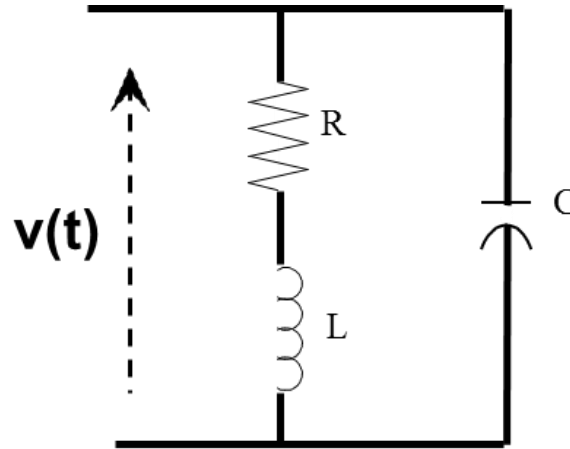Exercise 2

Obtain the expression for resonant frequency for the given parallel circuit





Thank You!