



ARIHA...



Prateek Jain [...]



KASHY...



SHASH...




RIT KH...




NAVEE...




NIKHIL ...

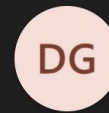

DRISHY...

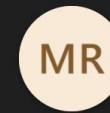


MARA...

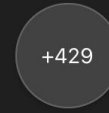

+429



SG

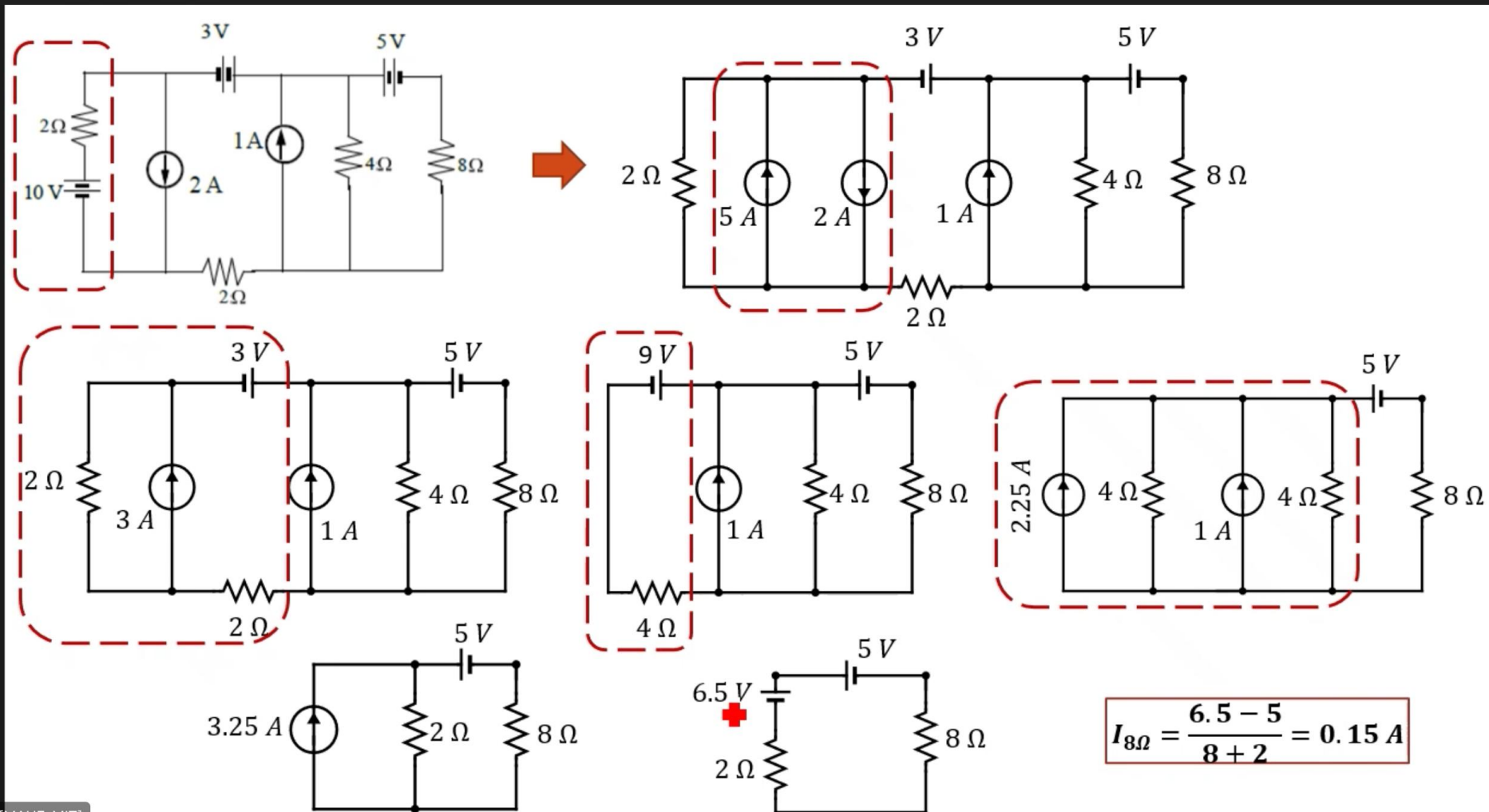


$$I_{8\Omega} = \frac{6.5 - 5}{8 + 2} = 0.15 A$$



MALLE...



Prateek Jain [...]

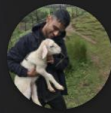

KUNAL...



ARNAV...



ADI - 1...



ARIHA...




SHASH...



RIT KH...







SRISHT...

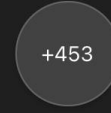



+453



SG

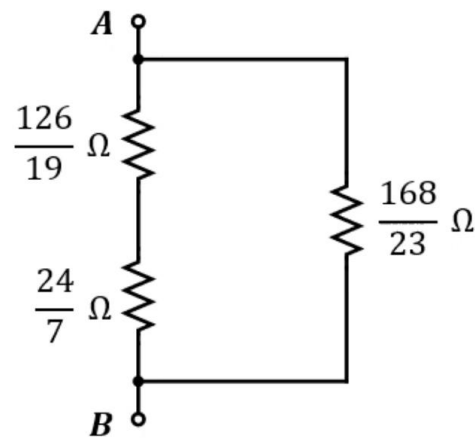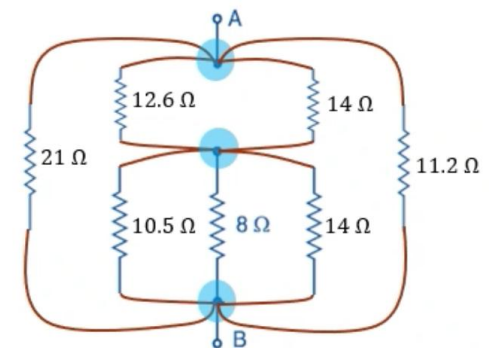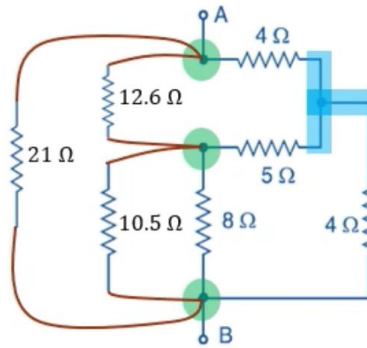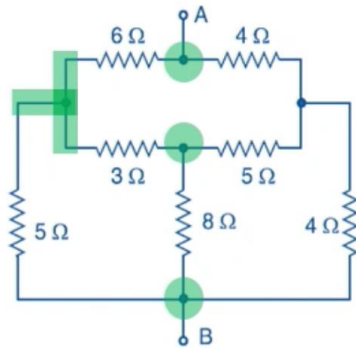

$$R_{AB} = 4.2317 \Omega$$

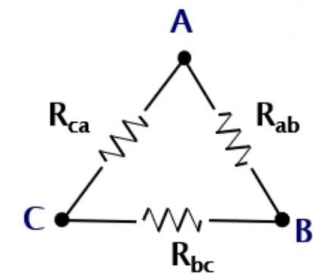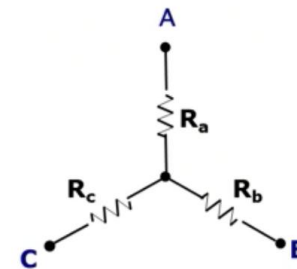

$$R_{ab} = R_a + R_b + \frac{R_a R_b}{R_c}$$


$$R_{bc} = R_b + R_c + \frac{R_b R_c}{R_a}$$

$$R_{ca} = R_c + R_a + \frac{R_a R_c}{R_b}$$




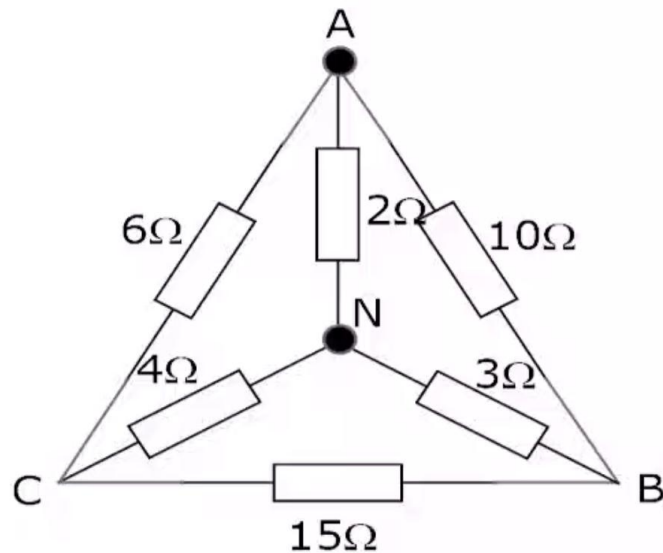
## Self-Practice 2: Star-Delta Transformation

Calculate the equivalent resistance across the terminals **A** and **N** of the given network.



Ans:  $R_{AN} = 1.4741 \Omega$

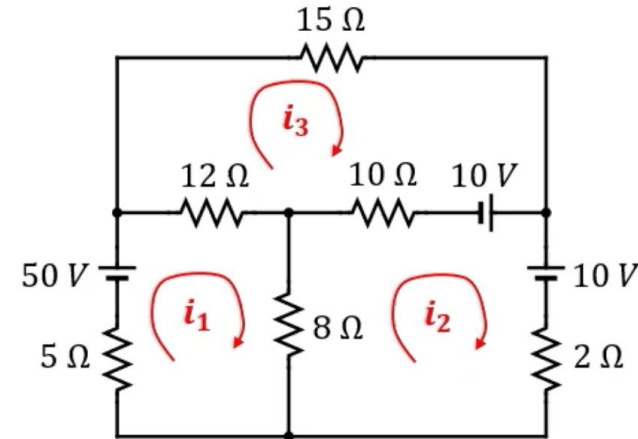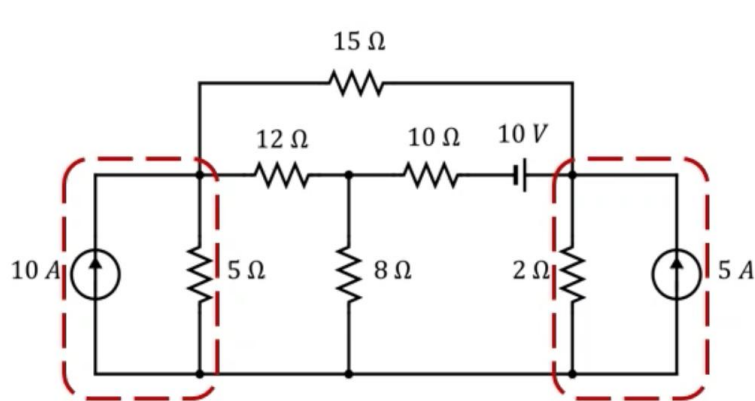

$$\begin{bmatrix} 25 & -8 & -12 \\ -8 & 20 & -10 \\ -12 & -10 & 37 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} = \begin{bmatrix} 50 \\ 0 \\ -10 \end{bmatrix}$$

$$i_1 = 3.2608 \text{ A}$$

$$i_2 = 1.9633 \text{ A}$$

$$i_3 = 1.3179 \text{ A}$$

$$I_{8\Omega} = i_1 - i_2 = 1.2975 \text{ A}$$

$$P_{8\Omega} = I_{8\Omega}^2 \times 8 = 13.4680 \text{ W}$$



Prateek Jain [...]



KABIER...



AISHW...



KUNAL...



ARNAV JA...



UDITA ...




SHAURYA ...



SRISHT...





BAIBHA...

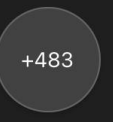

+483



SG

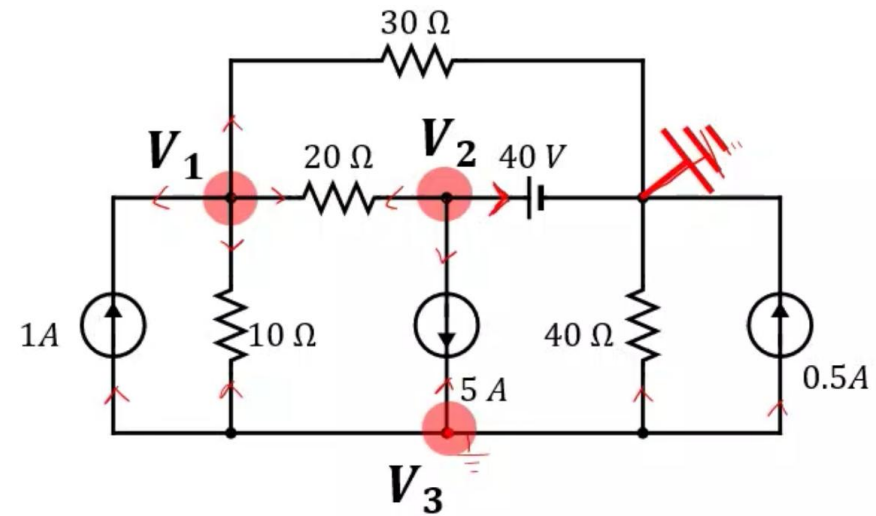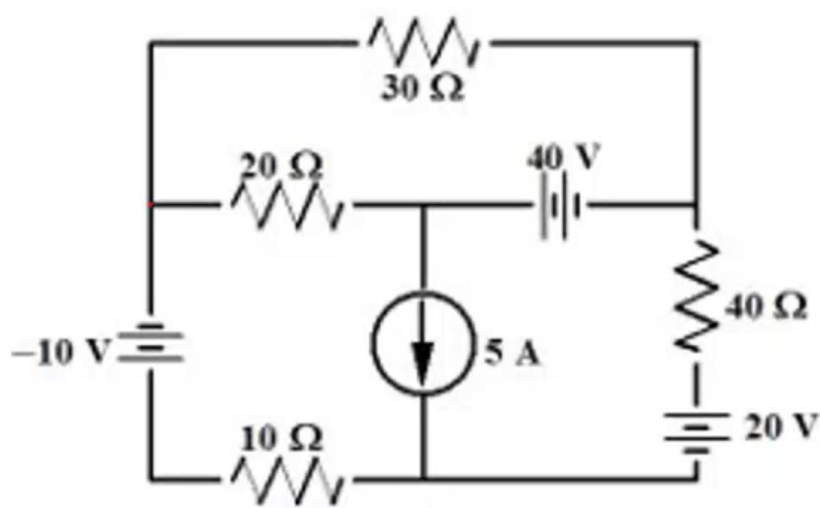


$$V_2 = 40 \text{ V}$$

$$\frac{V_1 - V_2}{20} + \frac{V_1 - V_3}{10} + \frac{V_1}{30} - 1 = 0$$

KCL at node 1

$$\frac{V_3 - V_1}{10} + \frac{V_3}{40} - 5 + 1 + 0.5 = 0$$

KCL at node 3

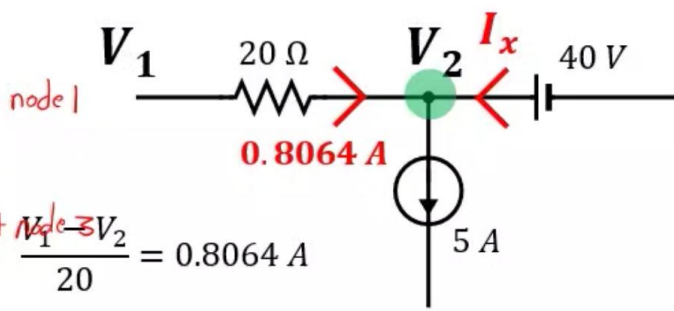

$$\frac{V_1 - V_2}{20} = 0.8064 \text{ A}$$

$$0.8064 + I_x = 5$$

$$I_x = 4.1936 \text{ A}$$

40 V battery is **discharging**

$$V_1 = 56.1290 \text{ V}$$


$$V_3 = 72.9032 \text{ V}$$


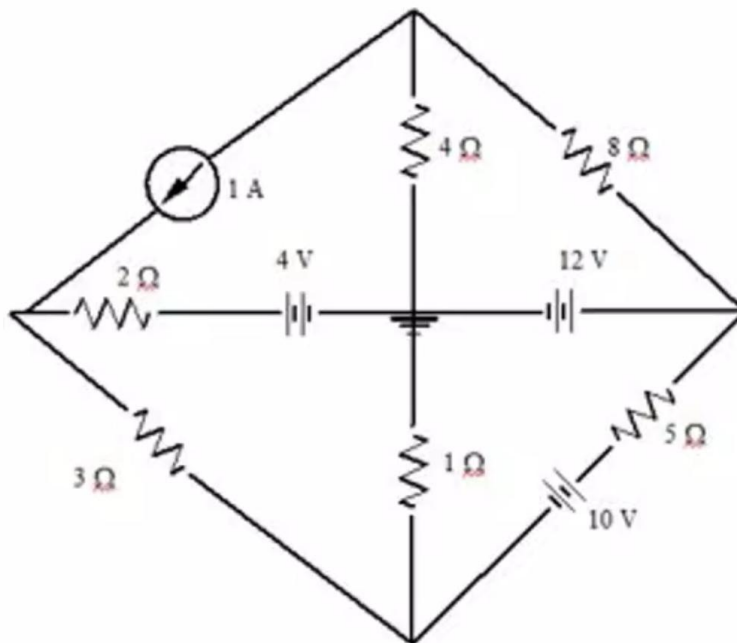
# Self-Practice 4: Node Voltage Analysis




Find the voltage of **all nodes** using node voltage analysis.





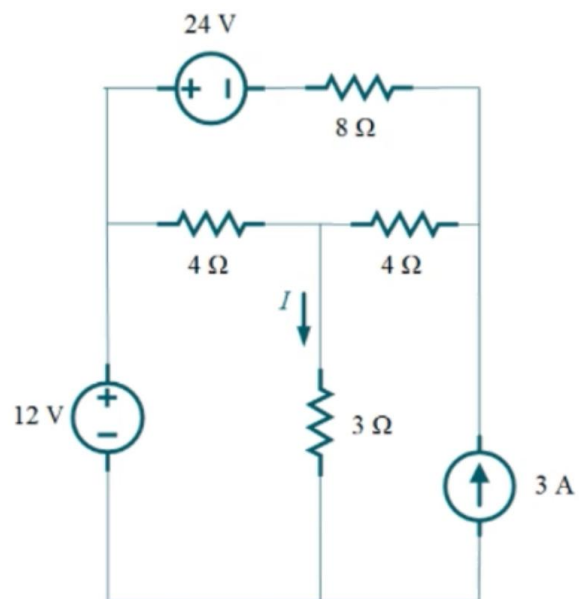
# Self-Practice 5: Superposition Principle


Find the current  $I$  using **superposition** theorem.



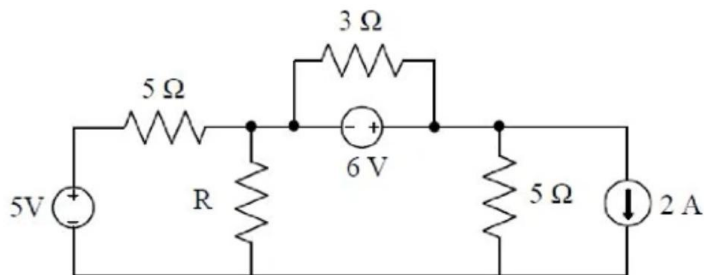Ans:  
 Due to source 24 V: - 1 A  
 Due to source 12 V: 2 A  
 Due to source 3 A: 1 A  
 Total: 2 A



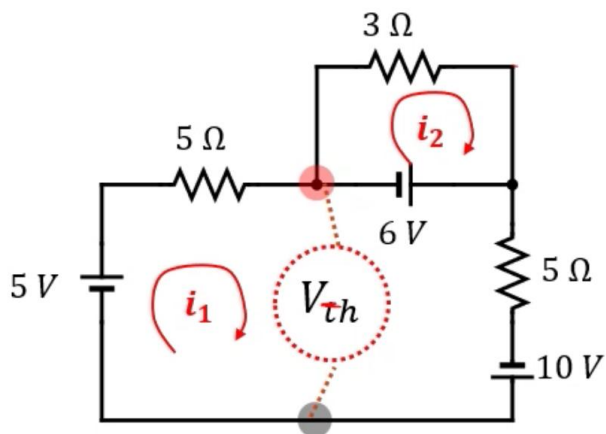To find  $V_{th}$  across load resistance  $R$ ,



$$5 - (5)(i_1) + 6 - 5(i_1) + 10 = 0$$

$$i_1 = 2.1 \text{ A}$$

$$-3i_2 - 6 = 0$$


$$i_2 = -2 \text{ A}$$

Applying KVL,

$$5 - 5(2.1) - V_{th} = 0$$

$$V_{th} = -5.5 \text{ V}$$

To find  $R_{th}$ ,

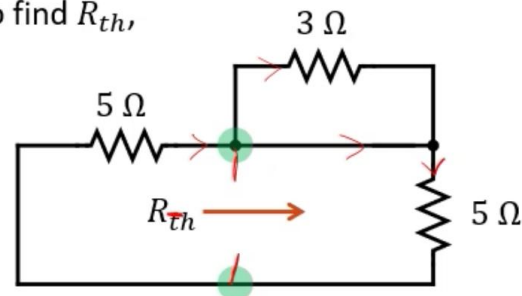

$$R_{th} = 2.5 \Omega$$

Maximum power transferred to load resistor ' $R$ ' will be,

$$P_{max} = \frac{V_{th}^2}{4R_{th}} = \frac{5.5^2}{4 \times 2.5} = 3.025 \text{ W}$$





KOMAL...



Prateek Jain [...]



AISHW...




TANAY ...



ARNAV...



UDITA ...

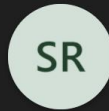


SHAUR...



SRISHT...




KASHY...

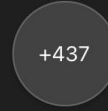


+437



SG

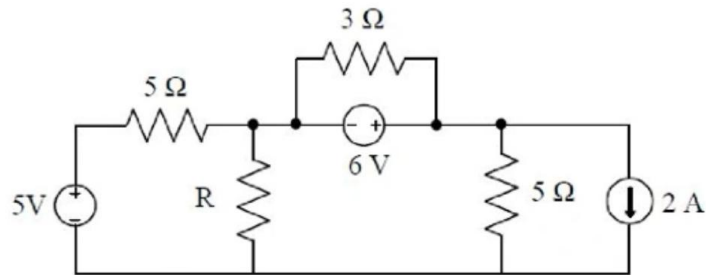

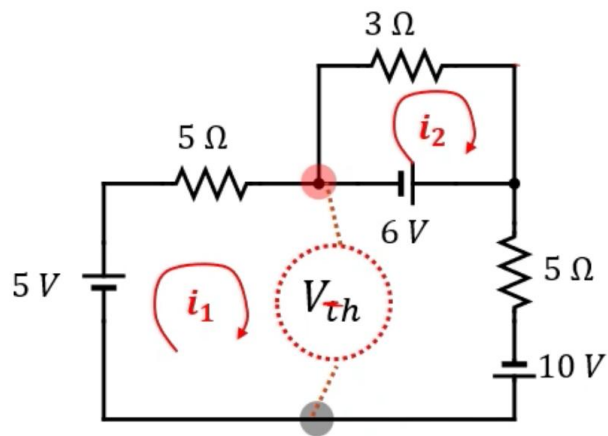To find  $V_{th}$  across load resistance  $R$ ,



$$5 - (5)(i_1) + 6 - 5(i_1) + 10 = 0$$

$$i_1 = 2.1 \text{ A}$$

$$-3i_2 - 6 = 0$$


$$i_2 = -2 \text{ A}$$

Applying KVL,

$$5 - 5(2.1) - V_{th} = 0$$

$$V_{th} = -5.5 \text{ V}$$

To find  $R_{th}$ ,

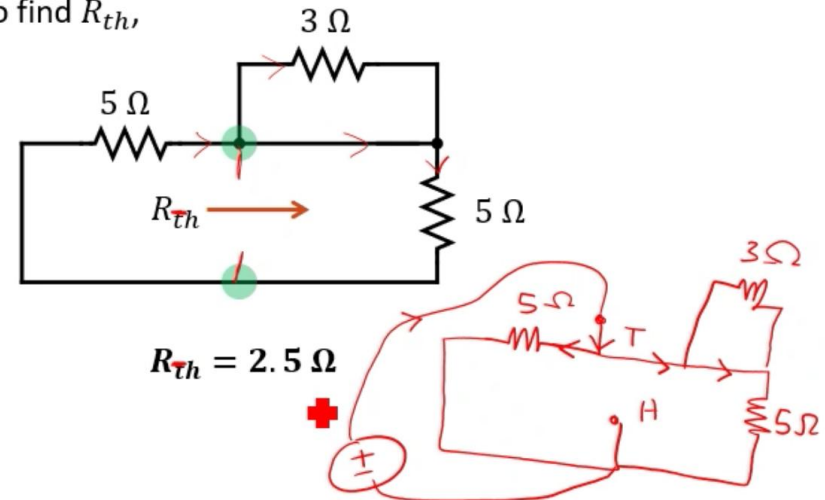

$$R_{th} = 2.5 \Omega$$

Maximum power transferred to load resistor ' $R$ ' will be,

$$P_{max} = \frac{V_{th}^2}{4R_{th}} = \frac{5.5^2}{4 \times 2.5} = 3.025 \text{ W}$$

## Self-Practice 6: Thevenin's and MPTT



Determine the value of the load resistance to be connected across terminals **A & B** such that maximum power is transferred to it. Also, find the **maximum power** transferred.

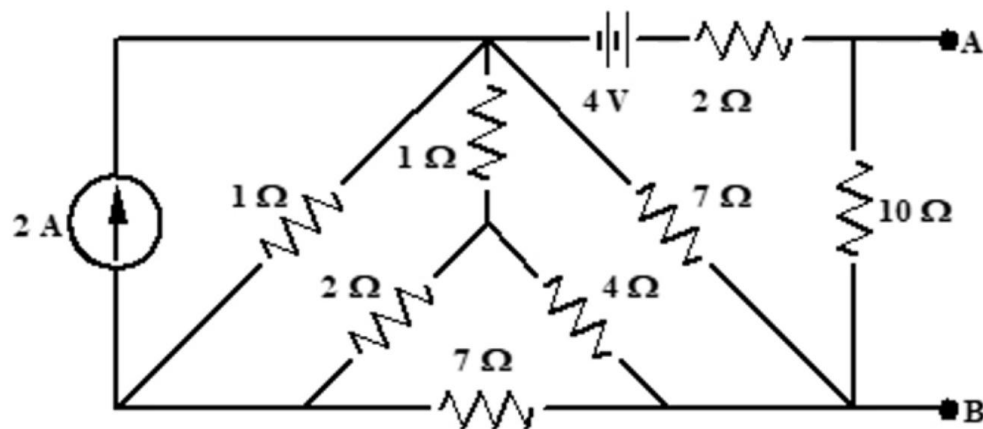


Fig. 1A

# Miscellaneous 1

Two purely resistive incandescent bulbs have the following ratings:

**Bulb 1: 120 V, 60 W**

**Bulb 2: 240 V, 480 W**


- a) Both of them are connected in series across a voltage source.
  - i. Which bulb will glow brighter and why?
  - ii. What is the maximum voltage that can be applied so that none of the bulbs fuse?
- b) Now both of them are connected in parallel across a voltage source.
  - i. Which bulb will glow brighter and why?
  - ii. What is the maximum voltage that can be applied so that none of the bulbs fuse?

Ans: (a) – (i) Bulb 1 will glow brighter as  $P_1 > P_2$ , (ii) Max. voltage = 180 V  
(b) – (i) Bulb 2 will glow brighter as  $P_2 > P_1$ , (ii) Max. voltage = 120 V
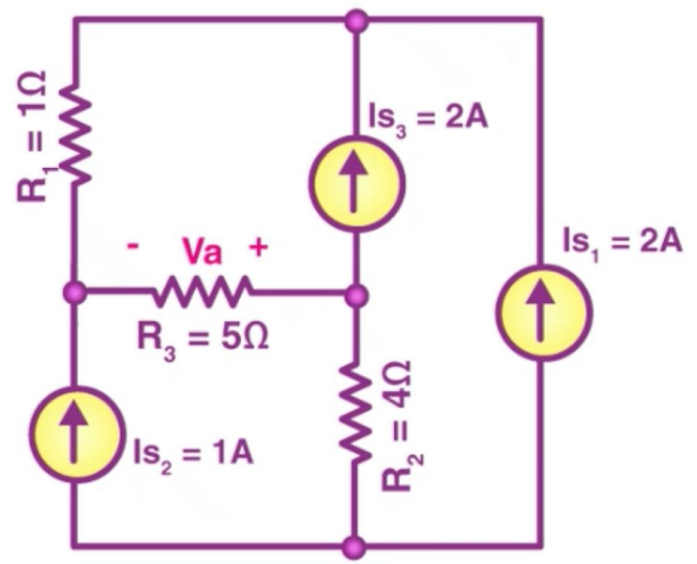
# Miscellaneous 2



Find  $V_a$  using nodal analysis and verify using mesh analysis



# Self-Practice 6: Thevenin's and MPTT



Determine the value of the load resistance to be connected across terminals **A & B** such that maximum power is transferred to it. Also, find the **maximum power** transferred.

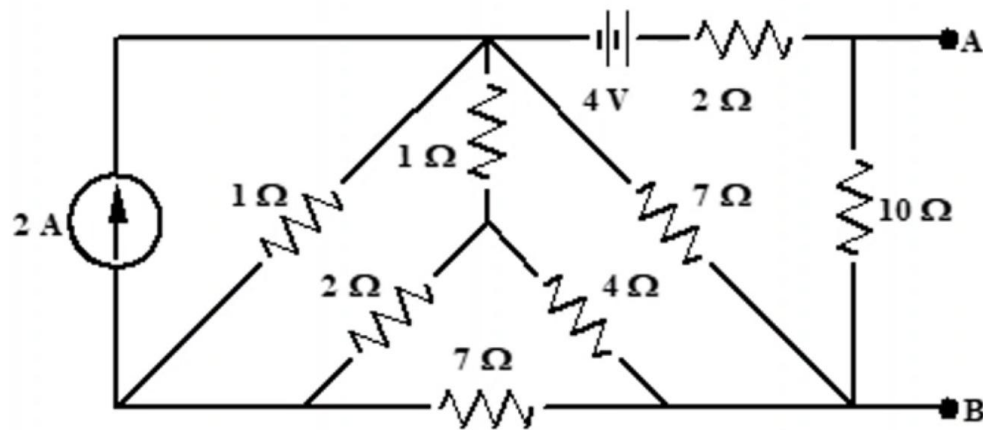


Fig. 1A

Ans: 2.923 Ω and 0.9098 W





Vedavyasa Ka...



Prateek Jain [...]

SN

SHASH...

TS

TANAY ...

AJ

ARNAV...

UG

UDITA ...

SR

SHAUR...

SS

SRISHT...

KP

KASHY...

+426

SG

# Assessment



## Brief Overview

Component	Marks	Details	
Internal	50	In-Semester Test 1	15
		In-Semester Test 2	15
		Weekly assignments via LMS Brightspace	20
External	50	End Semester Examination	