



MANIPAL INSTITUTE OF TECHNOLOGY

MANIPAL

(A constituent institution of MAHE, Manipal)




Basic Electrical Technology

TUTORIAL 1 - DC CIRCUITS


NETWORK REDUCTION | NETWORK ANALYSIS | NETWORK THEOREMS

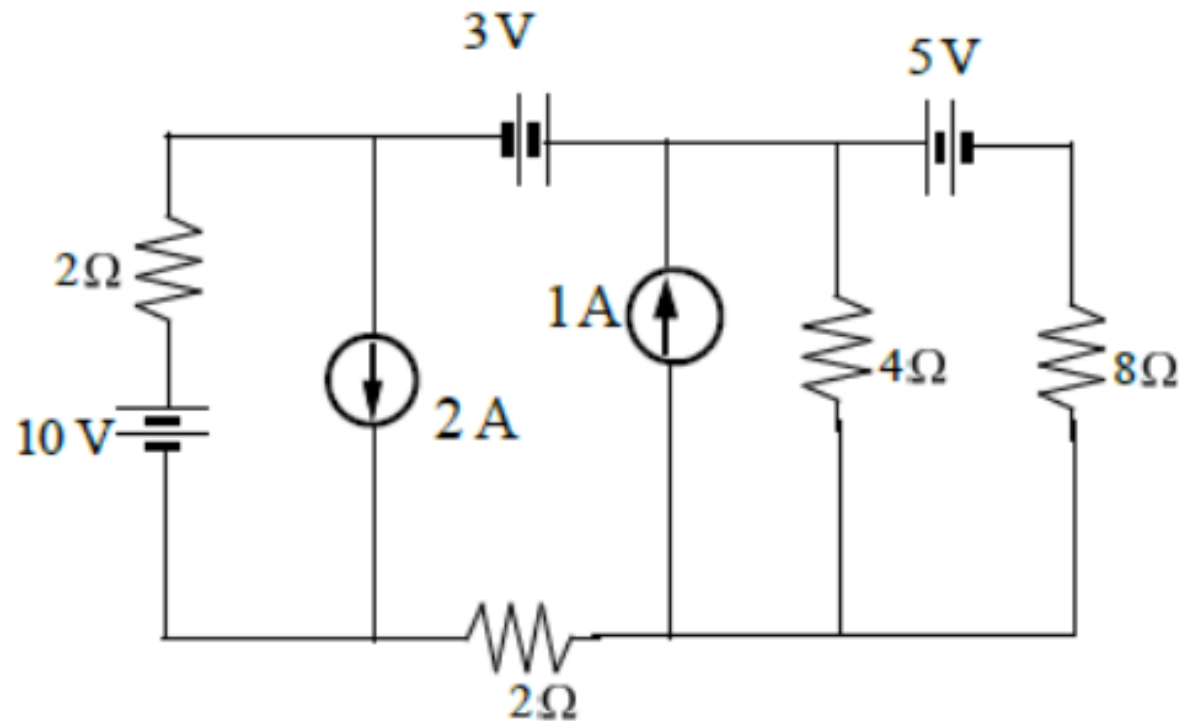Problem 1: Source Conversion

In the circuit shown, find the current through $8\ \Omega$ resistor by **source transformation** method.




Ans: 150 mA

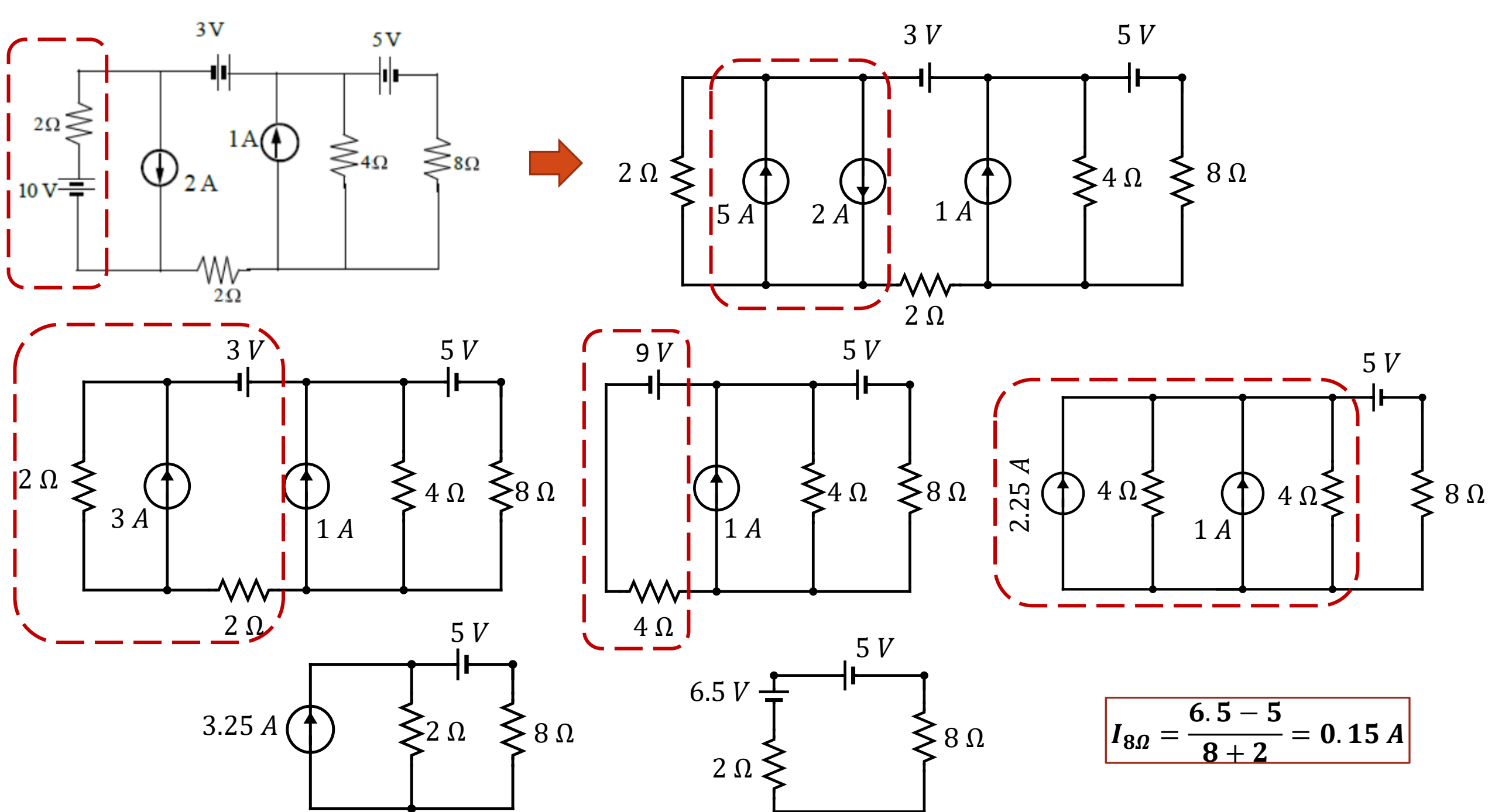

Self-Practice 1: Source Conversion

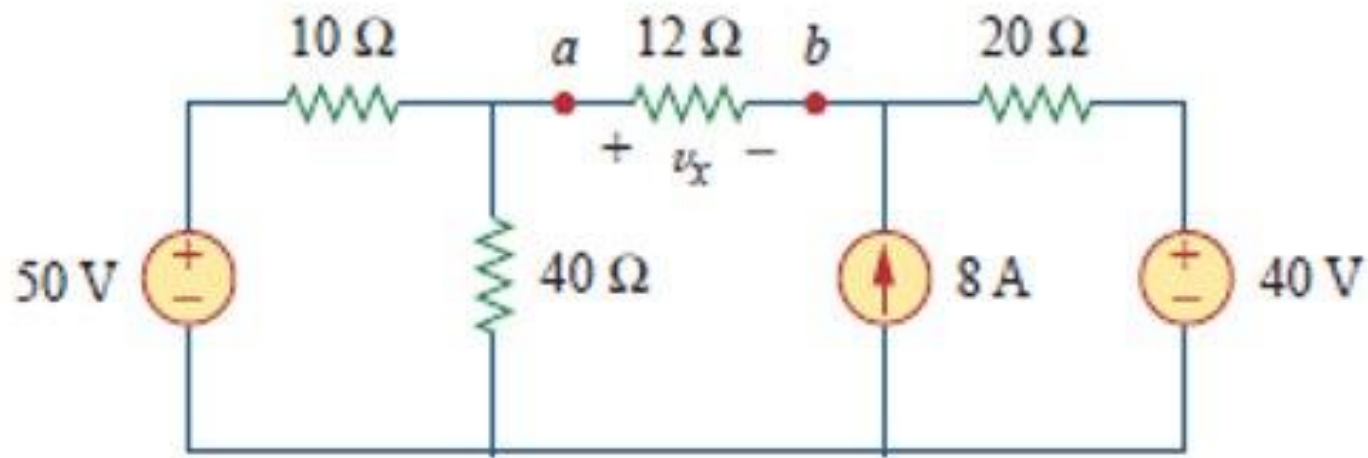
Find the voltage across $12\ \Omega$ resistor (labeled V_x) by the **source transformation** method.







Ans: -48 V

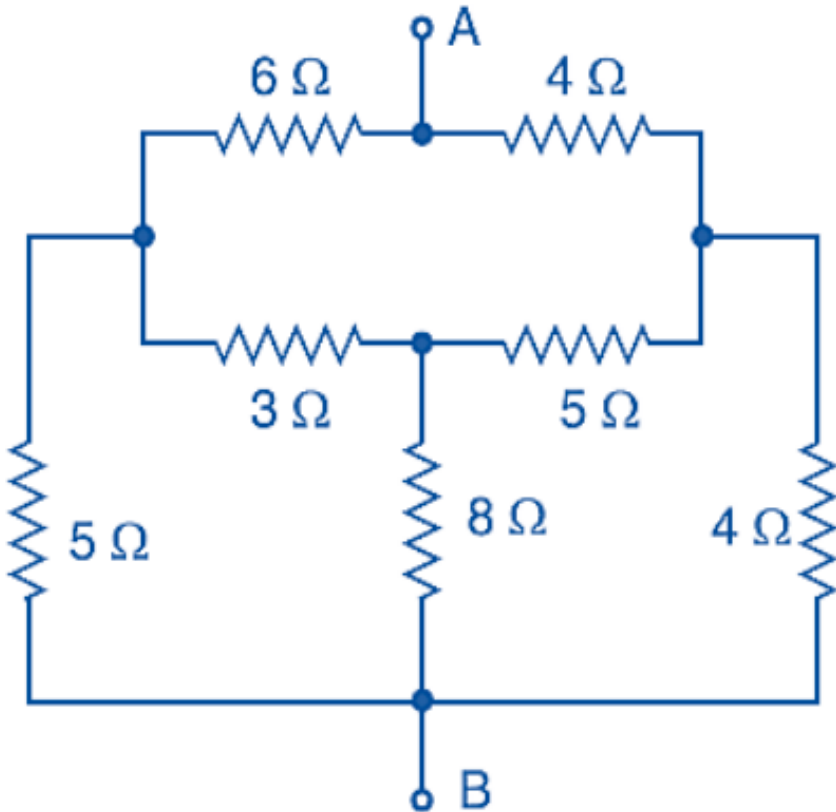Problem 2: Star-Delta Transformation

Determine the equivalent resistance across terminals **A** & **B**.




Ans: $4.23\ \Omega$

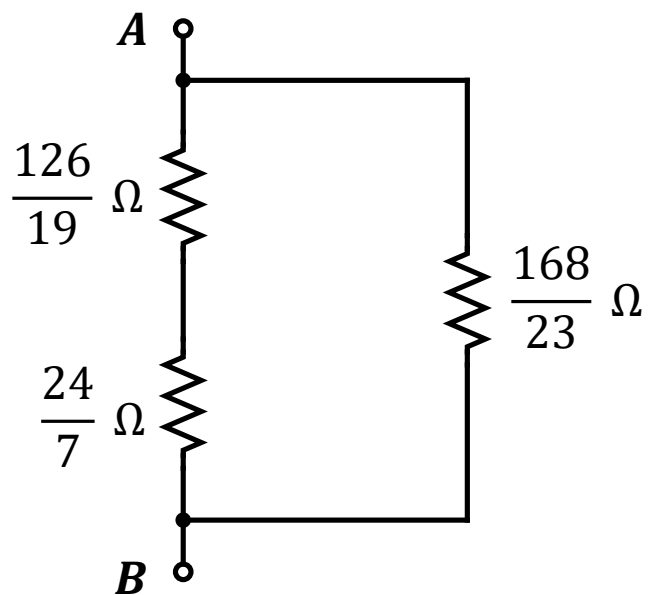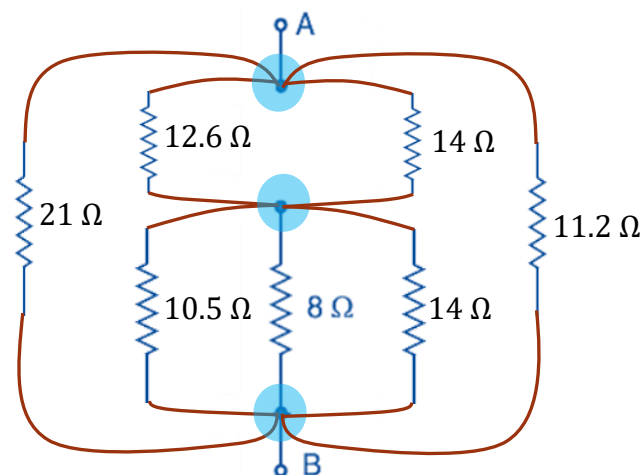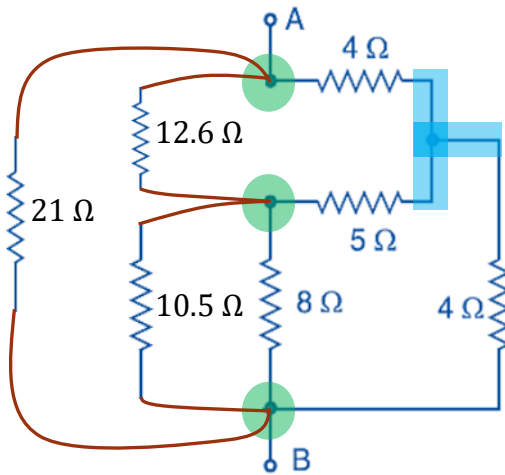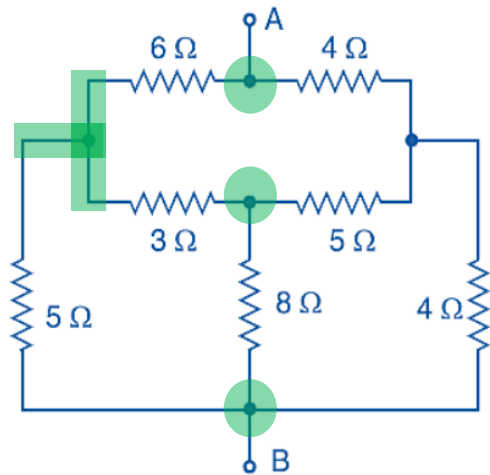

$$R_{AB} = 4.2317\ \Omega$$

Self-Practice 2: Star-Delta Transformation

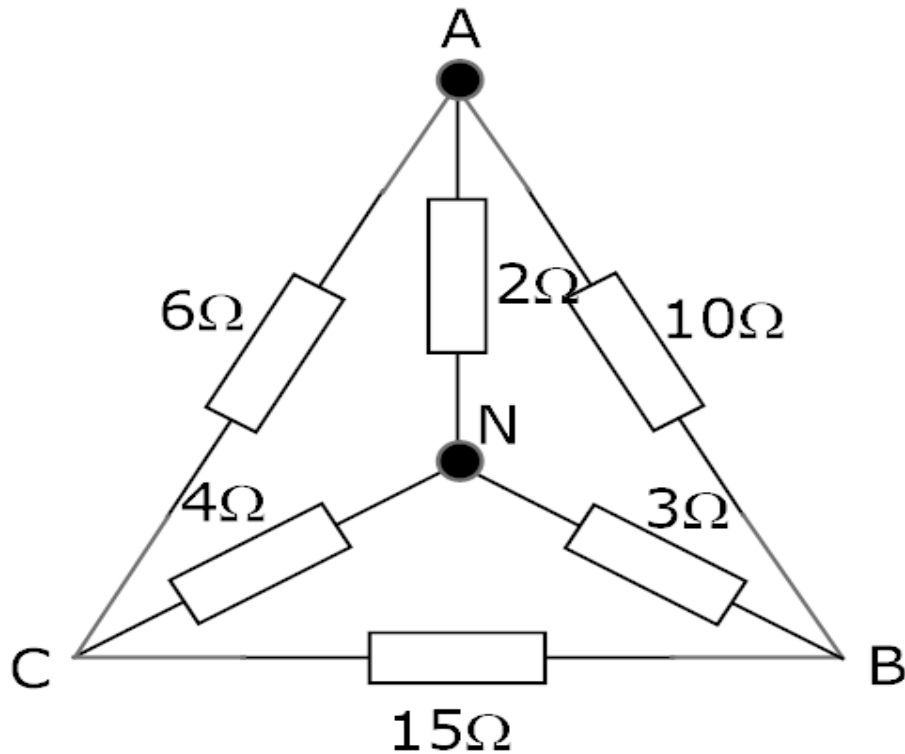Calculate the equivalent resistance across the terminals **A** and **N** of the given network.




Ans: $R_{AN} = 1.4741 \Omega$


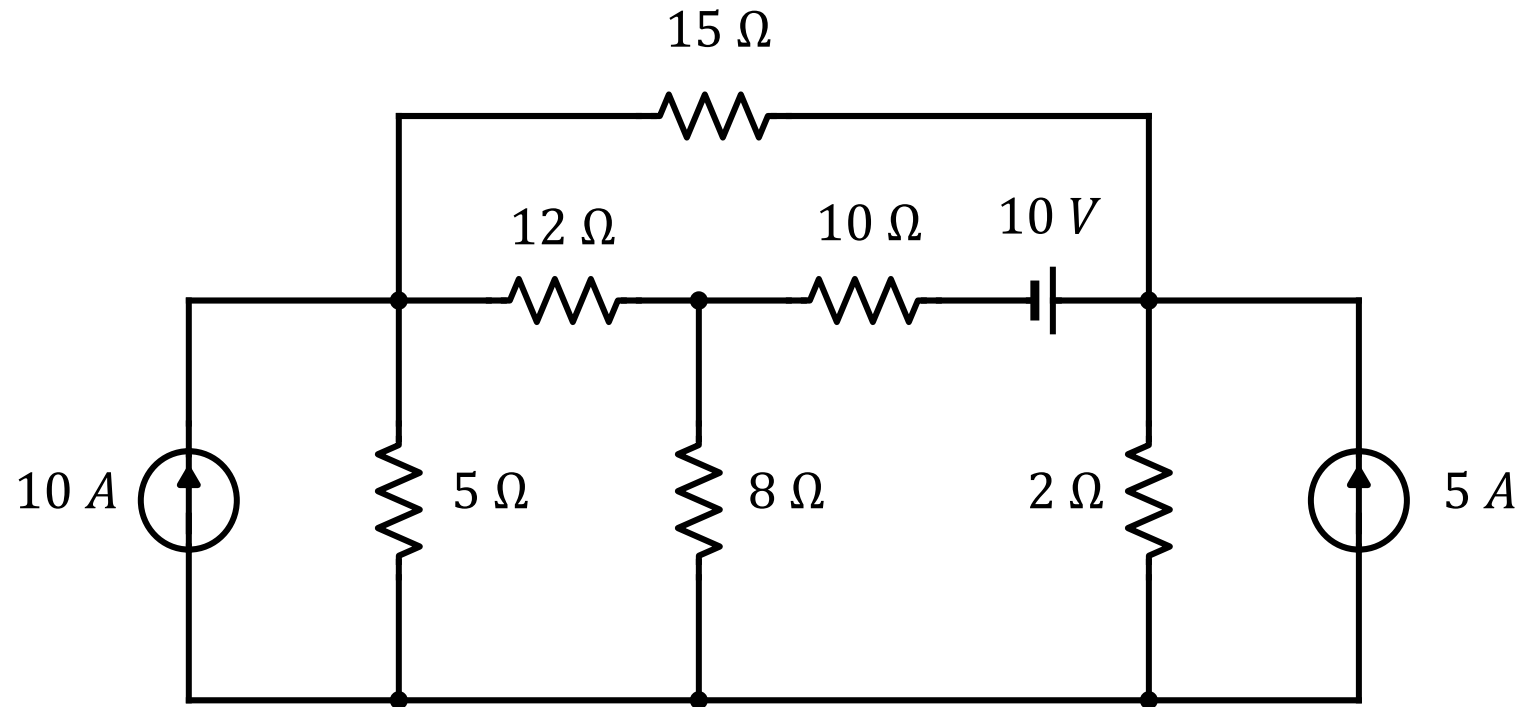
Problem 3: Mesh Current Analysis



Find the power dissipated in $8\ \Omega$ resistor using mesh current analysis in the circuit shown.



Ans: 13.47 W

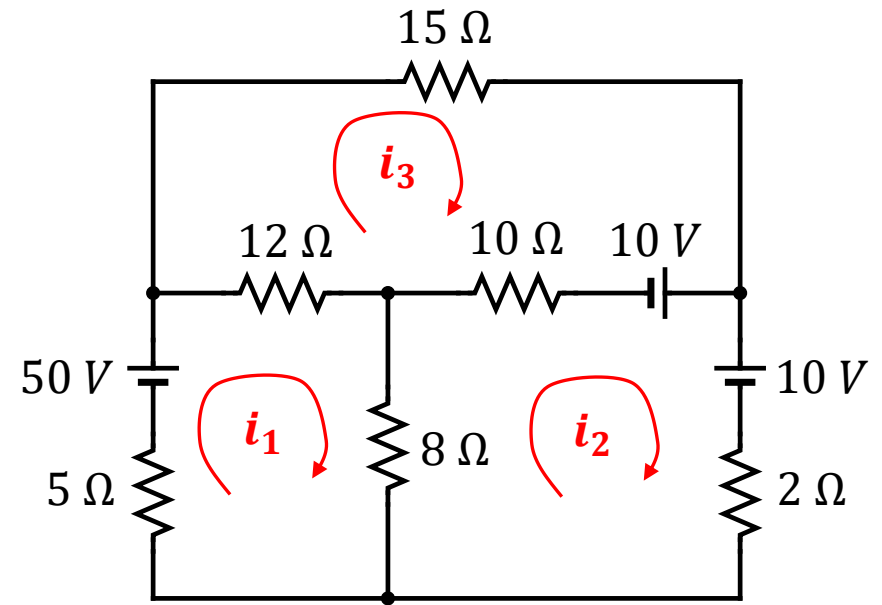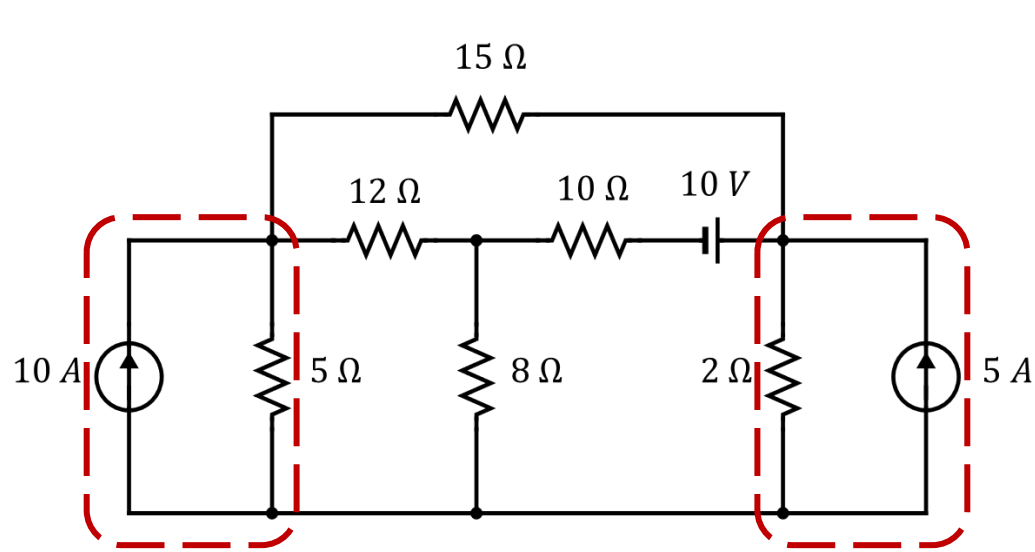

$$\begin{bmatrix} 25 & -8 & -12 \\ -8 & 20 & -10 \\ -12 & -10 & 37 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} = \begin{bmatrix} 50 \\ 0 \\ -10 \end{bmatrix}$$

$$i_1 = 3.2608 \text{ A}$$

$$i_2 = 1.9633 \text{ A}$$

$$i_3 = 1.3179 \text{ A}$$


$$I_{8\Omega} = i_1 - i_2 = 1.2975 \text{ A}$$

$$P_{8\Omega} = I_{8\Omega}^2 \times 8 = 13.4680 \text{ W}$$

Self-Practice 3: Mesh Current Analysis

Find the power supplied by **8 V** and **4 A** sources in the circuit.


Hint: Supermesh

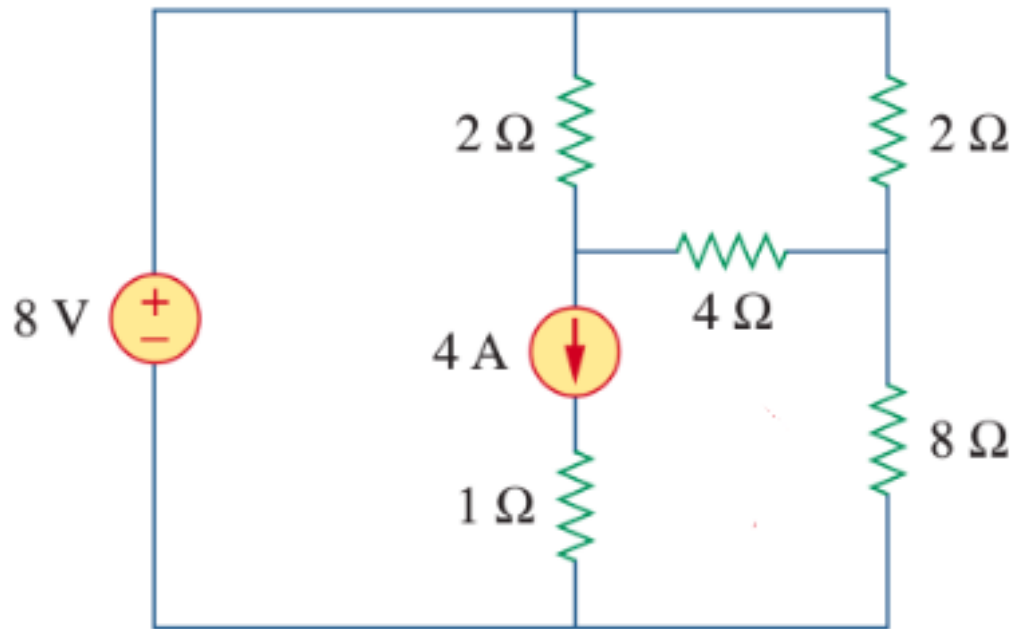



Ans:

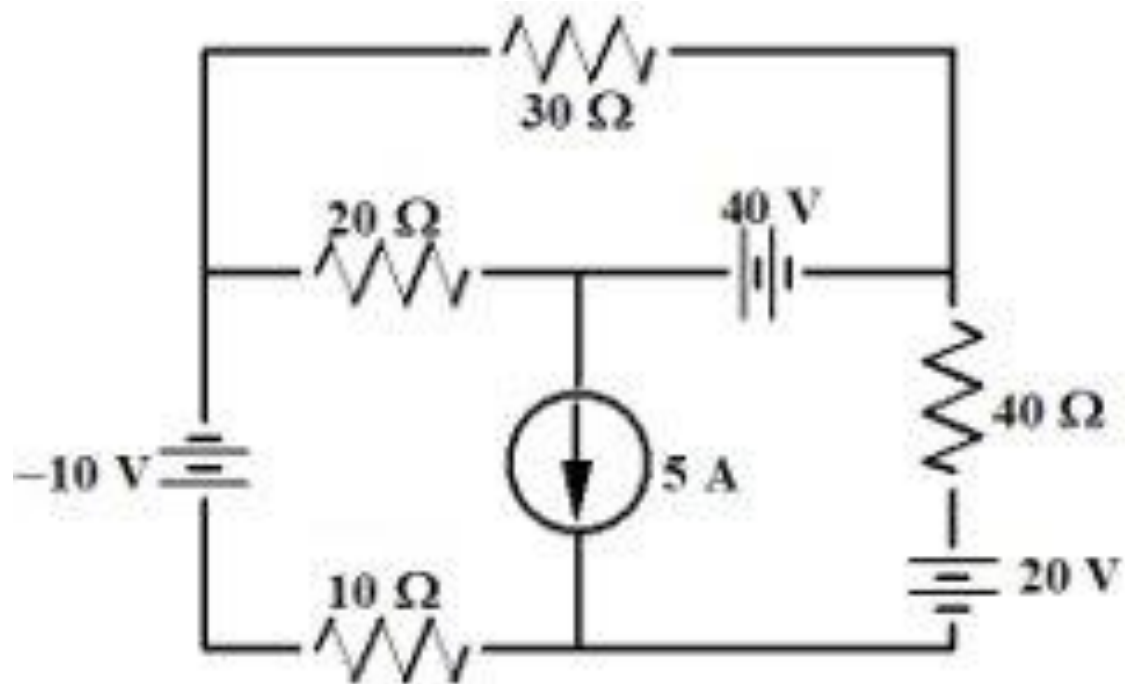Problem 4: Node Voltage Analysis

Find the current through **40 V** battery. Is the battery charging or discharging?



Ans: 4.19 A, Discharging

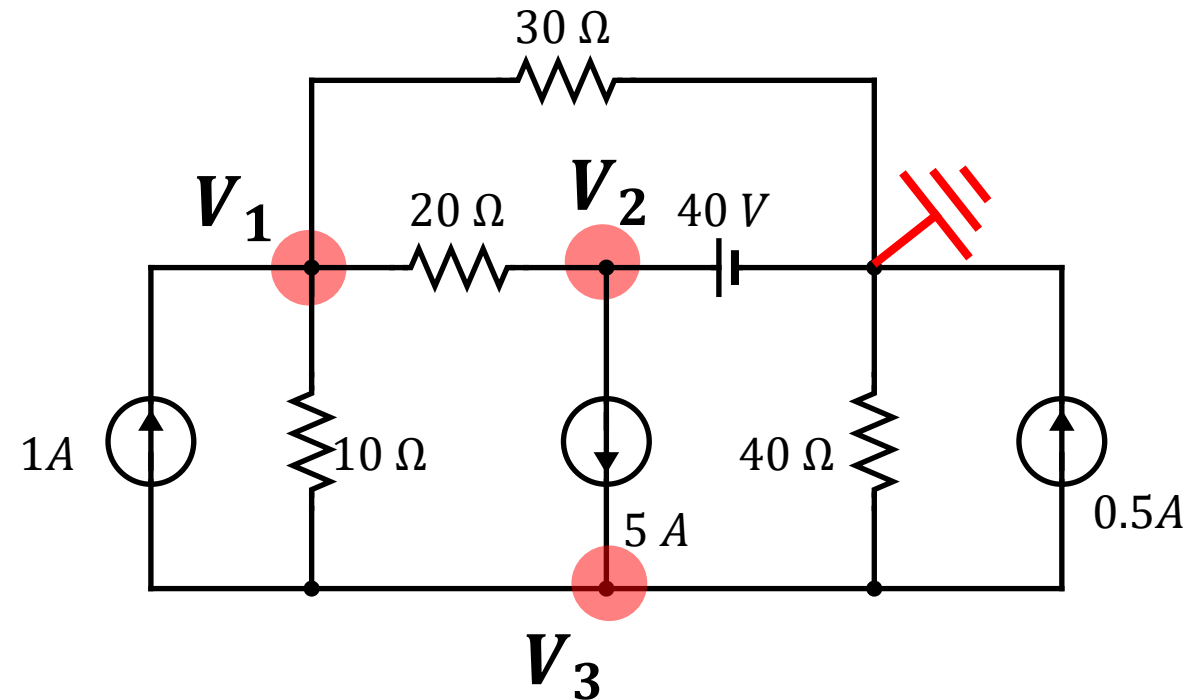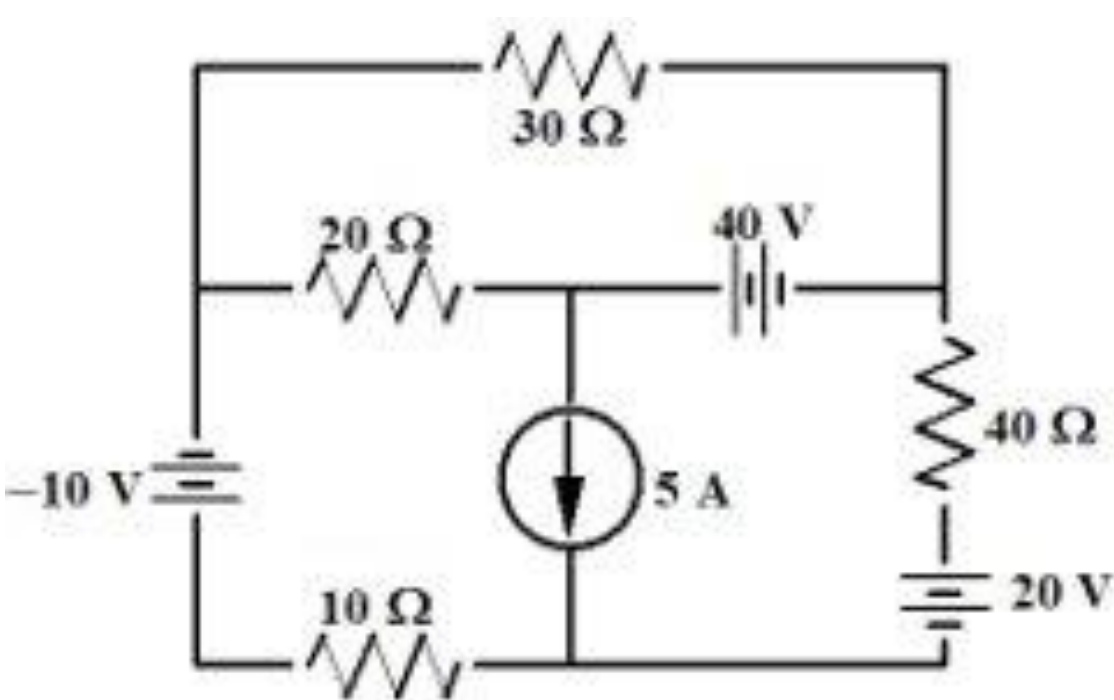


$$V_2 = 40 \text{ V}$$

$$\frac{V_1 - V_2}{20} + \frac{V_1 - V_3}{10} + \frac{V_1}{30} - 1 = 0$$

$$\frac{V_3 - V_1}{10} + \frac{V_3}{40} - 5 + 1 + 0.5 = 0$$

$$V_1 = 56.1290 \text{ V}$$

$$V_3 = 72.9032 \text{ V}$$

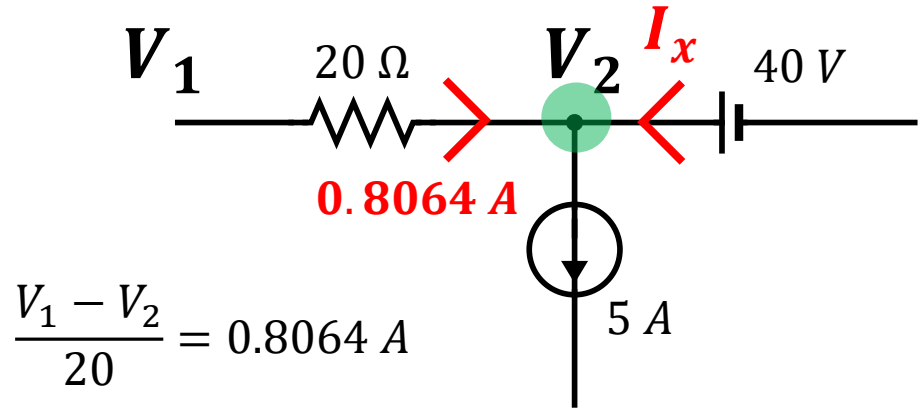

$$\frac{V_1 - V_2}{20} = 0.8064 \text{ A}$$


$$0.8064 + I_x = 5$$

$$I_x = 4.1936 \text{ A}$$

40 V battery is **discharging**


Self-Practice 4: Node Voltage Analysis

Find the voltage of **all nodes** using node voltage analysis.

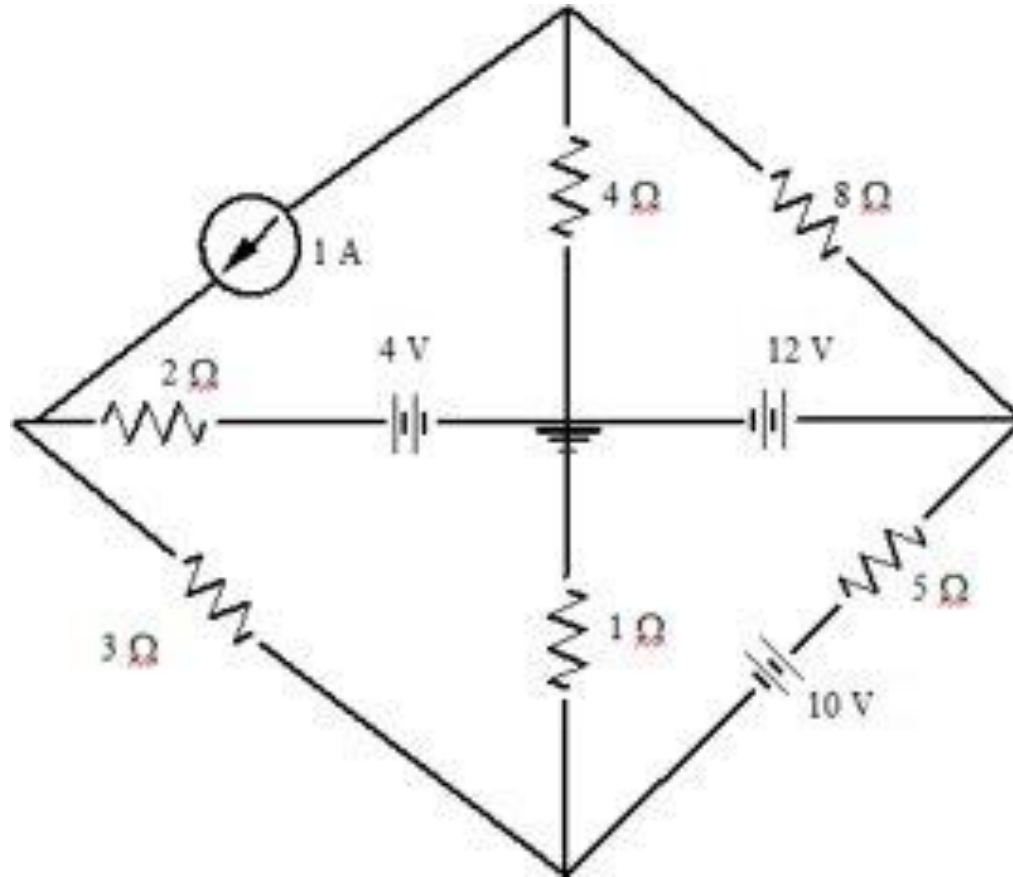

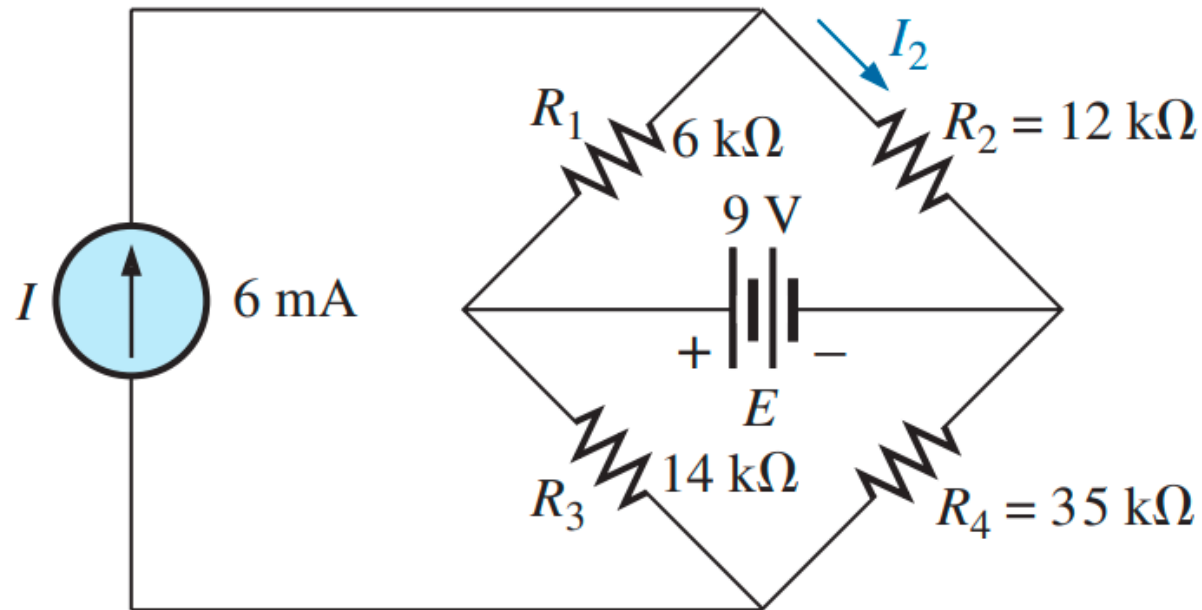Problem 5: Superposition Principle

Using the principle of superposition, find the current I_2 through **12 k Ω** resistor.




Ans:

Due to source I : 2 mA

Due to source 9 V: 0.5 mA


Total: 2.5 mA

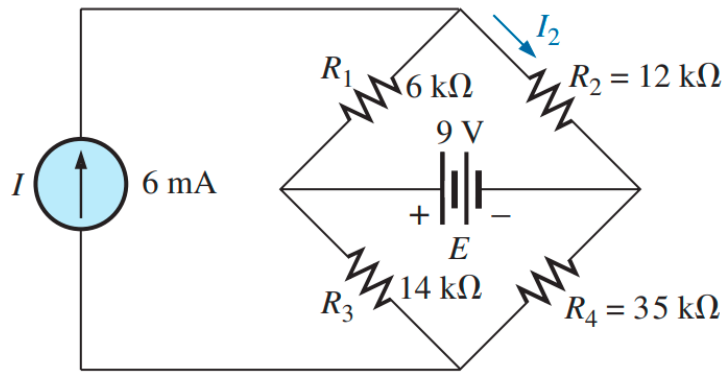

$$I_2 = I_2|_{6\text{ mA}} + I_2|_{9\text{ V}}$$


$$I_2 = 0.5\text{ mA} + 2\text{ mA} = 2.5\text{ mA}$$

Response I_2 due to 6 mA current source,

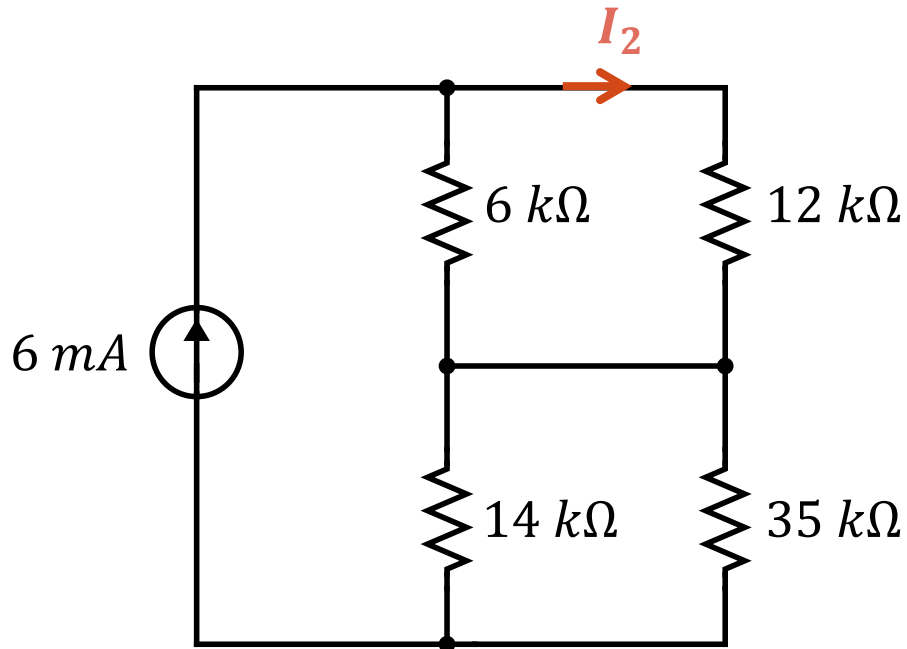

$$I_2|_{6\text{ mA}} = \frac{6 \times 10^{-3} \times 6 \times 10^3}{18 \times 10^3} = 2\text{ mA}$$


Response I_2 due to 9 V voltage source,

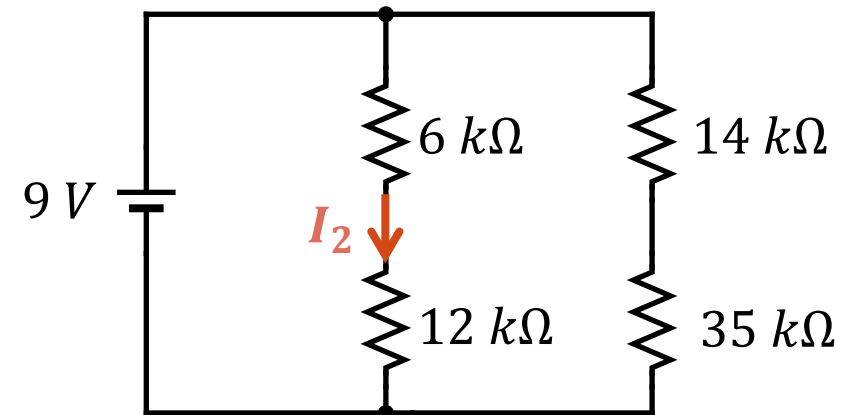

$$I_2|_{9\text{ V}} = \frac{9}{18 \times 10^3} = 0.5\text{ mA}$$

Self-Practice 5: Superposition Principle

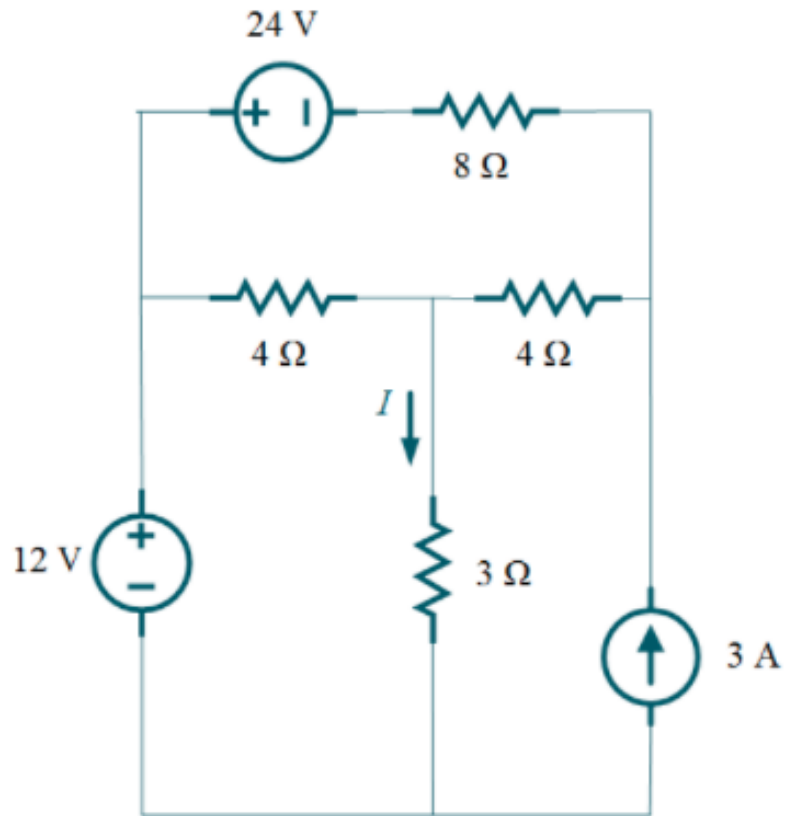Find the current I using **superposition** theorem.



Ans:

Due to source 24 V: - 1 A


Due to source 12 V: 2 A

Due to source 3 A: 1 A


Total: 2 A

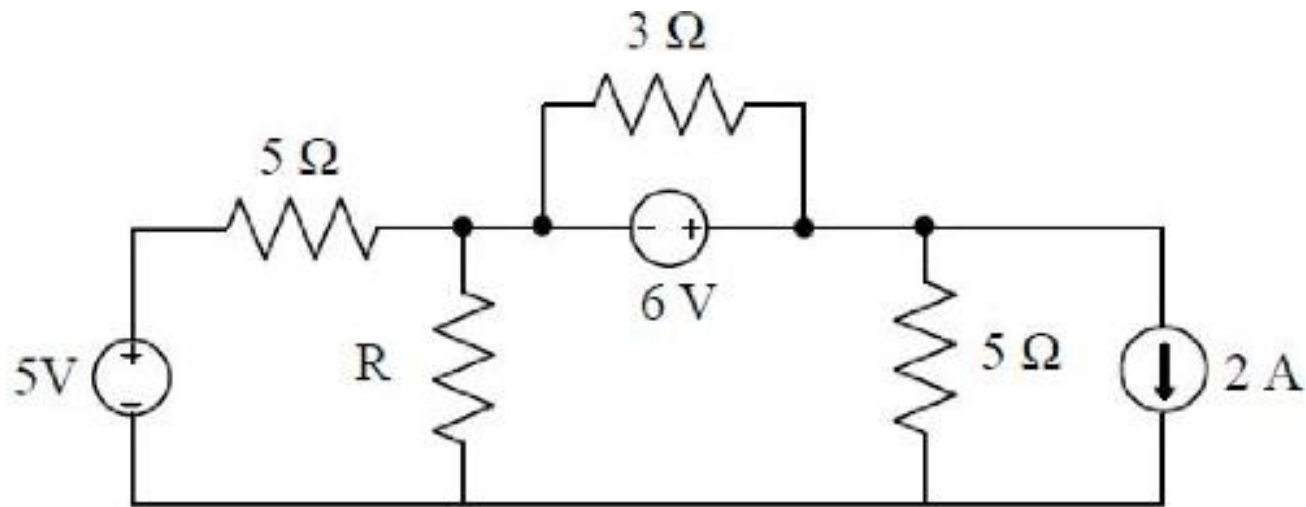Problem 6: Thevenin's & MPTT


In the circuit shown, find the **maximum power** transferred to the resistor **R**.



Ans: 3.025 W

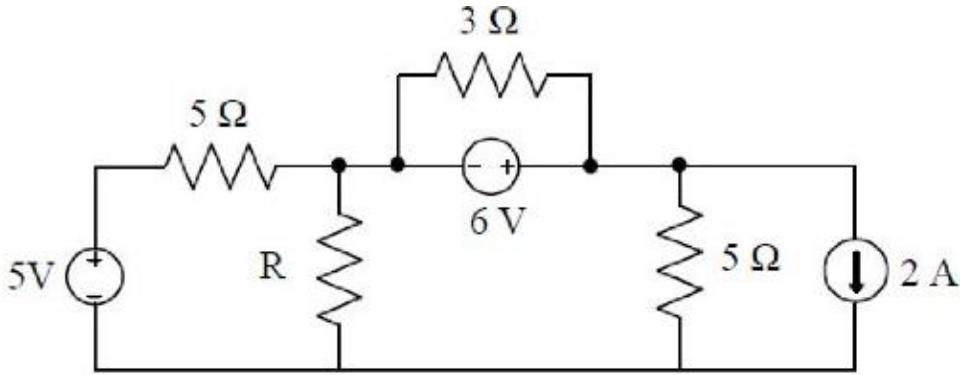

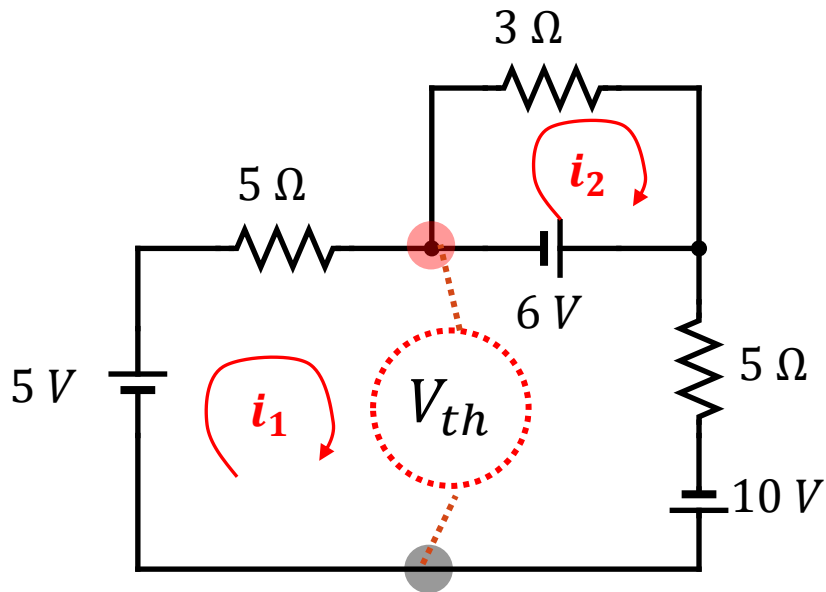To find V_{th} across load resistance R ,




$$5 - (5)(i_1) + 6 - 5(i_1) + 10 = 0$$

$$i_1 = 2.1 \text{ A}$$

$$-3i_2 - 6 = 0$$

$$i_2 = -2 \text{ A}$$

To find R_{th} ,

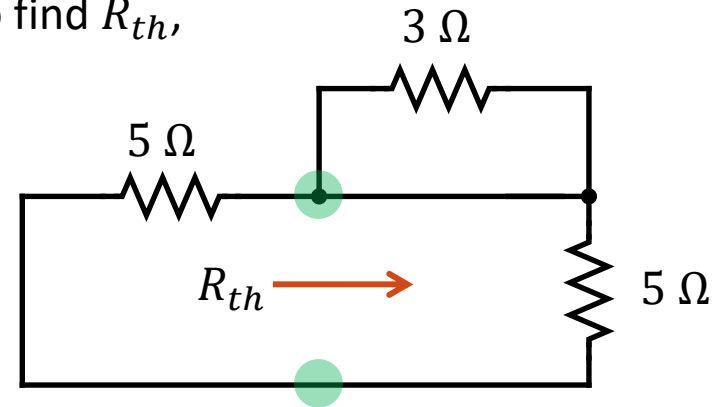

$$R_{th} = 2.5 \Omega$$

Applying KVL,

$$5 - 5(2.1) - V_{th} = 0$$

$$V_{th} = -5.5 \text{ V}$$

Maximum power transferred to load resistor ' R ' will be,

$$P_{max} = \frac{V_{th}^2}{4R_{th}} = \frac{5.5^2}{4 \times 2.5} = 3.025 \text{ W}$$

Self-Practice 6: Thevenin's and MPTT

Determine the value of the load resistance to be connected across terminals **A & B** such that maximum power is transferred to it. Also, find the **maximum power** transferred.

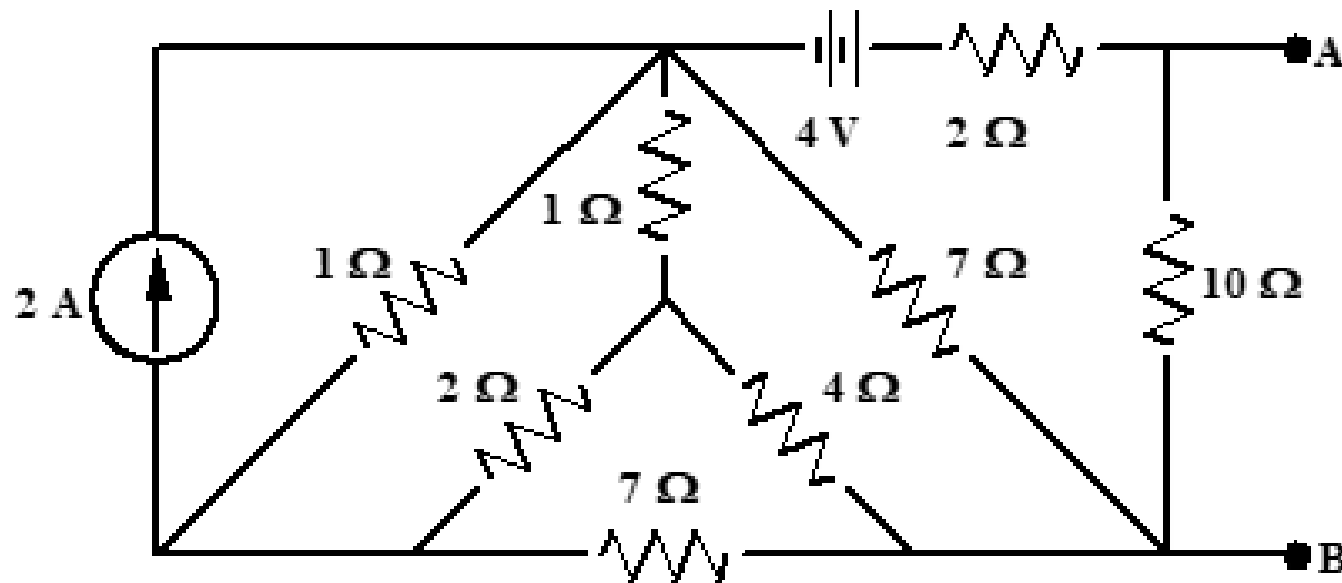


Fig. 1A

Ans: 2.923 Ω and 0.9098 W

Miscellaneous 1



Two purely resistive incandescent bulbs have the following ratings:

Bulb 1: 120 V, 60 W

Bulb 2: 240 V, 480 W


- a) Both of them are connected in series across a voltage source.
 - i. Which bulb will glow brighter and why?
 - ii. What is the maximum voltage that can be applied so that none of the bulbs fuse?
- b) Now both of them are connected in parallel across a voltage source.
 - i. Which bulb will glow brighter and why?
 - ii. What is the maximum voltage that can be applied so that none of the bulbs fuse?

Ans: (a) – (i) Bulb 1 will glow brighter as $P_1 > P_2$, (ii) Max. voltage = 180 V
(b) – (i) Bulb 2 will glow brighter as $P_2 > P_1$, (ii) Max. voltage = 120 V

Miscellaneous 2



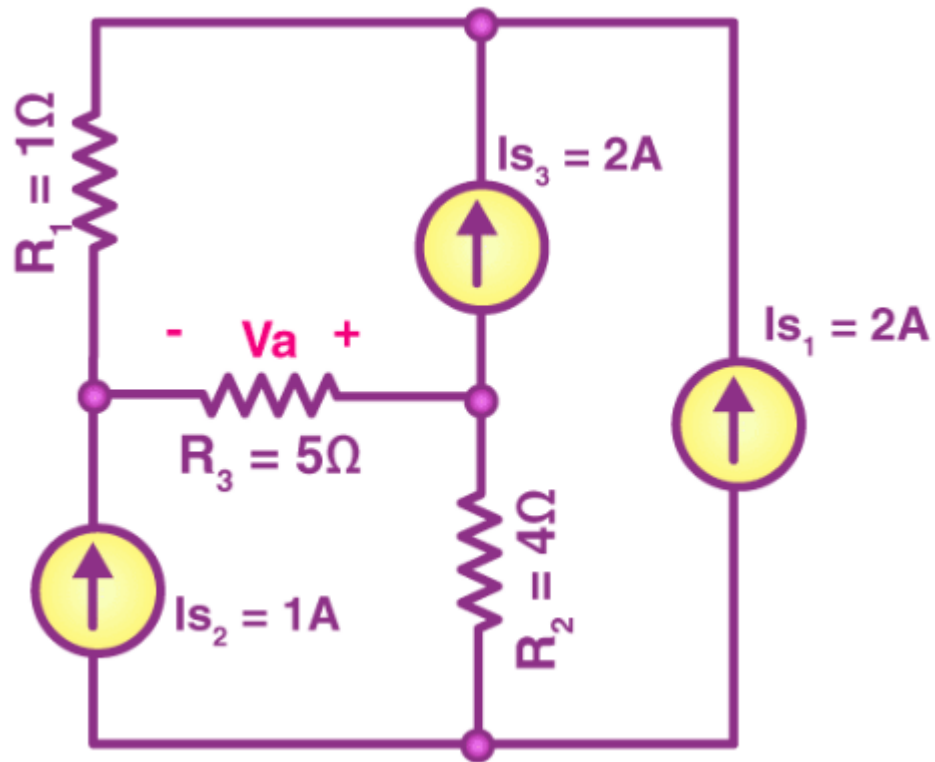Find V_a using nodal analysis and verify using mesh analysis



Ans: - 25 V